

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

ELECTRICAL ENGINEERING DEPARTMENT

Dr. Ibrahim O. Habiballah

EE-463 -131

Key Solutions

Quiz 1 ser#: I.D.: Name:

Q.1 An inductive load consisting of R and X in parallel feeding from a 2400-V rms supply absorbs 288 kW at a lagging power factor of 0.8. Determine R and X.

- a. $R = 26.7 \text{ Ohm}$; $X = 20.0 \text{ Ohm}$
- b. $R = 20.0 \text{ Ohm}$; $X = 26.7 \text{ Ohm}$**
- c. $R = 0.05 \text{ Ohm}$; $X = 0.0375 \text{ Ohm}$
- d. $R = 0.0375 \text{ Ohm}$; $X = 0.05 \text{ Ohm}$

Q.2 A 40-MVA, 20-kV/400-kV, single-phase transformer has the following series impedances: $Z_1 = 0.9 + j1.8 \text{ Ohm}$ (referred to the low-voltage side) and $Z_2 = 128 + j288 \text{ Ohm}$ (referred to the high-voltage side). Using the transformer rating as base, determine the per unit equivalent impedance of the transformer referred to the low-voltage side. Compute the per unit equivalent impedance using the ohmic value referred to the high-voltage side.

- a. $1.22 + j 2.52$; $488 + j 1008$
- b. $0.122 + j 0.252$; $4.88 + j 100.8$
- c. $0.122 + j 0.252$; $0.122 + j 0.252$**
- d. $4.88 + j 100.8$; $4.88 + j 100.8$