

KING FAHD UNIVERSITY OF PETROLEUM AND MINERALS
Electrical Engineering Department

EE 466-03 Major Examination 1

Term 062

Course	EE 466
Date	March 27, 2007
Time	18:30-19:45
Place	59-2017

Student Name: _____

Student Id # _____

Student Sequence #-----


Section Number **03**

Question #	Score
Q 1	/30
Q 2	/45
Q 3	/25

Mohamed


Q2

a)

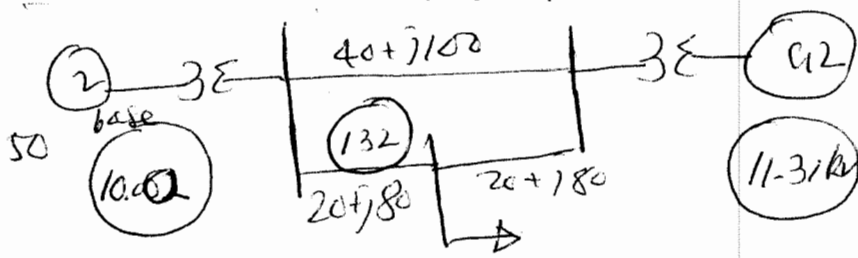

Line base = 132 kV;
 $V_{L1} \text{ base} = \frac{132(12.2)}{167} = 10.0 \text{ kV}$
 $V_{L2} \text{ base} = \frac{132(13.8)}{162} = 11.32$
 $X_{g1} = 0.15 \left(\frac{100}{50} \right) \frac{12.2^2}{10^2} = 0.4463$; $X_{g2} = 0.15 \frac{100}{20} \frac{13.8^2}{11.32^2} = 1.1166$
 $X_{T1} = 0.1 \left(\frac{100}{80} \right) \frac{12.2^2}{10^2} = 0.18596 = 0.1 + \frac{100}{80} \frac{161^2}{132^2}$
 $X_{T2} = 0.1 \left(\frac{100}{40} \right) \frac{13.8^2}{11.31^2} = 0.3719 \mu$
 $Z_{\text{base line}} = 132^2 / 100 = 174.24 \Omega$; $Z_{4/100} = \frac{20 + j80}{174.24} = 0.2296 + j0.9183$
 $Z_{20/100} = 0.1148 + j0.4591$
 Load (Parallel); $R = \frac{V^2}{P} = \frac{117^2}{40} = 592.9$, $r = \frac{592.9}{174.24} = 3.402 \mu$
 $X = \frac{V^2}{Q} = \frac{117^2}{30} = 790.53$; $X = 4.537$


Q2(b)

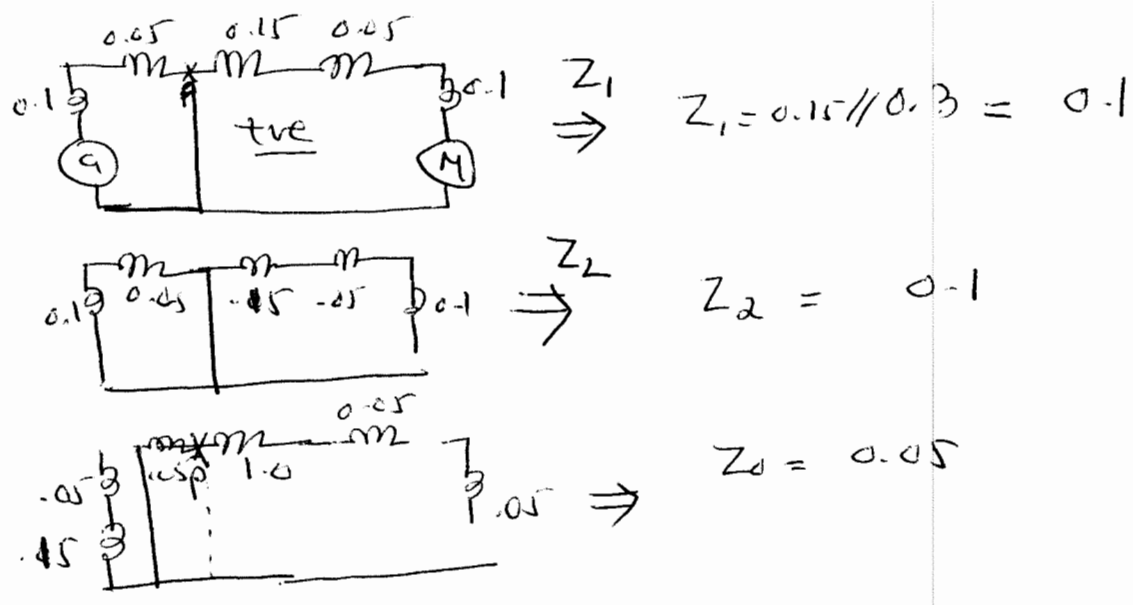

Line-ground = $C_1 = C_2 = C_0 = \frac{V_0}{Z_1 + Z_2 + Z_0} = j(0.1 + 0.1 + 0.05)$
 $I_F = 3C_1 = -12.0 \mu A$

Q1 4)

No charge or per unit reactances

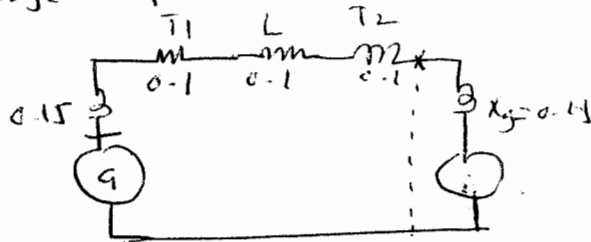

$$V_g = 10.6 \text{ kV} \\ = \frac{10.6}{11} = 0.9636 \text{ pu}$$

$$Z_f = 0.15 // (0.45) = 0.1125$$

$$I_f = V_g / Z_f = 8.565 \text{ pu}$$


$$I_{base} = \frac{25 \times 10^3}{\sqrt{3}(11)} = 1312.2 \text{ A}$$

$$I_f(\text{A}) = 1312.2 * (8.565) = 11,239 \text{ A} \angle -90^\circ$$

$$I_{fn} = \frac{8.565(0.45)}{0.6} = 6.4237 = 8429.24 \text{ A}$$

$$I_{fg} = \frac{8.565(0.11)}{0.6} = 2.14125 = 2809.74$$

5) b)

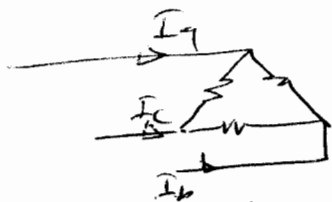

$$I_A + I_B + I_C = 0$$

$$10/30 + 15/60 + I_C = 0$$

$$I_C = 18/117^\circ$$

$$\begin{bmatrix} I_0 \\ I_1 \\ I_2 \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} 10/30 \\ 15/60 \\ 18/117 \end{bmatrix}$$

$$= \begin{bmatrix} 0 \\ 10.35 + j9.3 \\ -1.7 - j4.3 \end{bmatrix} = \begin{bmatrix} 0 \\ 14 \angle 42^\circ \\ 4.65 \angle 288^\circ \end{bmatrix}$$

$$\begin{bmatrix} I_{B0} \\ I_{B1} \\ I_{B2} \end{bmatrix} = \begin{bmatrix} 0 \\ 14 \angle 28^\circ \\ 4.65 \angle 8^\circ \end{bmatrix}$$

Q2