

EE 205 Dr. A. Zidouri

Electric Circuits II

# More about Mutual Inductance

## Lecture #32

EE 205 Dr. A. Zidouri

The material to be covered in this lecture is as follows:

- Mutual Inductance in Terms of Self Inductance
- Mesh Current Analysis of magnetically coupled Circuits
- Procedure for Determining Dot Markings
- Energy Calculation

EE 205 Dr. A. Zidouri

After finishing this lecture you should be able to:

- Analyze Circuits with Mutual Inductance
- Determine the Coefficient of Coupling
- Determine the Dot Markings of neighboring Coils
- Perform Energy Calculations in Magnetically Coupled Circuits

## Mutual Inductance in Terms of Self Inductance

We have seen that

$$L_1 = N_1^2 p_1$$

$$L_2 = N_2^2 p_2$$

Therefore  $L_1 L_2 = N_1^2 N_2^2 p_1 p_2 = N_1^2 N_2^2 (p_{11} p_{21})(p_{22} p_{12})$

But for linear system,

$$p_{21} = p_{12} \Rightarrow$$

$$L_1 L_2 = N_1^2 N_2^2 p_1^2 \left(1 + \frac{p_{11}}{p_{12}}\right) \left(1 + \frac{p_{22}}{p_{12}}\right)$$

$$= M^2 \left(1 + \frac{p_{11}}{p_{12}}\right) \left(1 + \frac{p_{22}}{p_{12}}\right)$$

Replacing the positive quantity  $\left(1 + \frac{p_{11}}{p_{12}}\right) \left(1 + \frac{p_{22}}{p_{12}}\right)$  by  $\frac{1}{k^2}$  gives a more meaningful expression

$$M^2 = k^2 L_1 L_2 \quad \text{or} \quad M = k \sqrt{L_1 L_2}$$

## Mutual Inductance in Terms of Self Inductance (Cont.)

$k$  is called the **Coefficient of Coupling** and must lie between 0 and 1:

$$0 \leq k \leq 1$$

When  $\Phi_{12} = \Phi_{21} = 0 \Rightarrow p_{12} = 0$

$$\Rightarrow \frac{1}{k^2} = \infty, \text{ or } k = 0$$

If no flux linkage between the coils, obviously  $M = 0$  and  $k = 0$ , when  $\Phi_{11} = \Phi_{22} = 0$ ,  
which presents the Ideal State.

## Mesh Current Analysis

- To solve the following example 32-1, Let us reproduce the Mesh Current Equations that describe the following Circuit seen in Lec31:

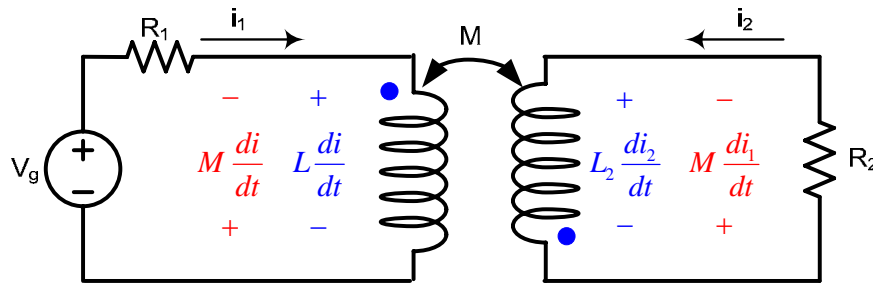


Fig.31-5 (c) The Self and Mutually Induced Voltages appearing across the coils shown in Fig.31-5 (a)

$$-v_g + R_1 i_1 + L_1 \frac{di_1}{dt} - M \frac{di_2}{dt} = 0 \quad (\text{Mesh 1})$$

$$R_2 i_2 + L_2 \frac{di_2}{dt} - M \frac{di_1}{dt} = 0 \quad (\text{Mesh 2})$$

### Example 32-1

- Write a Set of Mesh-Current Equations that describe the Circuit in the following Figure:
- What is the Coefficient of Coupling of the Magnetically Coupled Coils?

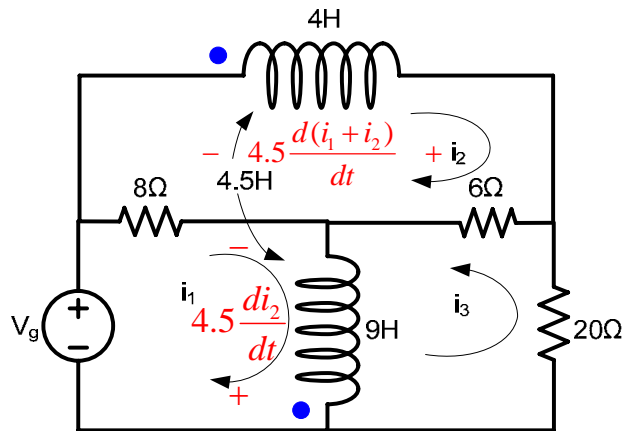


Fig.32-1 Circuit for Example 32-1

$$-v_g + 8(i_1 - i_2) + 9 \frac{d(i_1 + i_3)}{dt} - 4.5 \frac{di_2}{dt} = 0 \quad (\text{Mesh 1})$$

$$6(i_2 + i_3) + 8(i_2 - i_1) + 4 \frac{di_2}{dt} - 4.5 \frac{d(i_2 + i_3)}{dt} = 0 \quad (\text{Mesh 2})$$

$$20i_3 + 6(i_2 + i_3) + 4 \frac{di_2}{dt} + 9 \frac{d(i_1 + i_3)}{dt} - 4.5 \frac{di_2}{dt} = 0 \quad (\text{Mesh 3})$$

$$k = \frac{M}{\sqrt{L_1 L_2}} = \frac{4.5}{\sqrt{4 \times 9}} = \frac{4.5}{6} = 0.75$$

## Procedure for Determining Dot Markings

The following six steps applied to the following figure determine a set of **Dot Markings**.

- 1) Arbitrarily Select one Terminal, (Say Terminal D) of one coil and mark it with a **Dot**
- 2) Assign a **current** into the dotted terminal and label it  $i_D$
- 3) Use the Right-Hand rule to determine the **direction** of the magnetic field established by  $i_D$  inside the coupled coils and label this as  $\Phi_D$
- 4) Arbitrarily **pick one terminal** of the second coil (Say Terminal A) and **Assign a current** into it (Show this as  $i_A$ )
- 5) Use the Right-Hand rule to determine the **direction** of the magnetic field established by  $i_D$  inside the coupled coils and label this as  $\Phi_A$
- 6) **Compare the directions** of the two fluxes  $\Phi_D$  and  $\Phi_A$ . If the fluxes have the same reference direction, place a **Dot** on the terminal of the second coil where the test current ( $i_A$ ) enters.

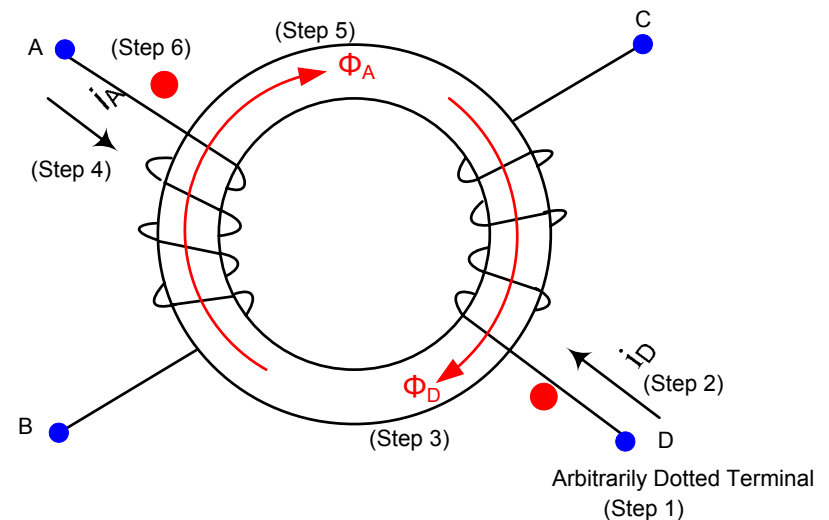


Fig.32-2 Set of Coils Showing Steps for Determining a Set of Dot Markings

In this example the fluxes  $\Phi_D$  and  $\Phi_A$  have the same reference direction, therefore a **Dot** goes on terminal A.



### Example 32-2

- The polarity markings on two coils are to be determined experimentally. The experimental setup is shown in Fig.32-3. When the switch is opened, the dc Voltmeter kicks upscale. According to the polarity and dot marking shown, where should we place the other dot?

**Answer:**

- ✓ The lower terminal of the unmarked coil has the same instantaneous polarity as the dotted terminal.
- ✓ Therefore, place a dot on the lower terminal of the unmarked coil.

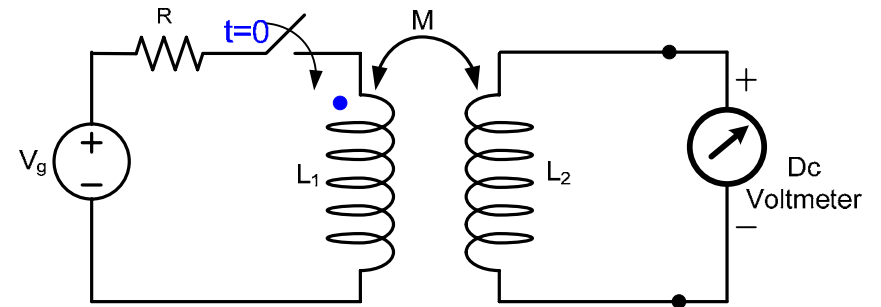


Fig.32-3 (a) Circuit For Example 32-2

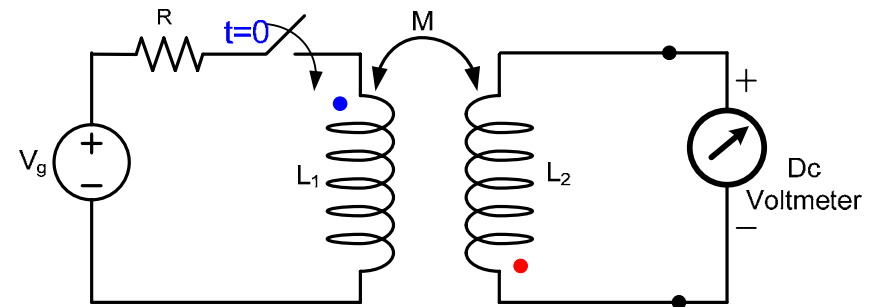


Fig.32-3 (b) Circuit For Example 32-2

## Energy Calculations

For linear magnetic coupling

①  $M_{12} = M_{21}$

②  $M = k\sqrt{L_1 L_2}$

Consider the following Circuit

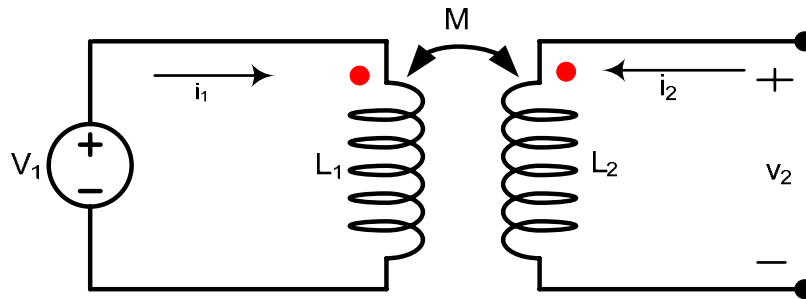


Fig.32-4 Circuit used for Energy Calculations

### Case 1:

Increase  $i_1$  from 0 to  $I_1$ , hold  $i_1 = I_1$  and  $i_2 = 0$

$$\int_0^{W_1} dw = L_1 \int_0^{I_1} di_1$$

$$W_1 = \frac{1}{2} L_1 I_1^2$$

### Case 2:

Now we hold  $i_1 = I_1$  and Increase  $i_2$  from 0 to  $I_2$

$$p = I_1 M_{12} \frac{di_2}{dt} + i_2 v_2$$

## Energy Calculations (cont)

The total energy stored in the pair of coils when  $i_2 = I_2$

$$\int_{W_1}^W dw = \int_0^{I_2} I_1 M_{12} di_2 + \int_0^{I_2} L_2 i_2 di_2$$

$$W = W_1 + \frac{1}{2} L_2 I_2^2 + M_{12} I_1 I_2$$

$$W = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 + M_{12} I_1 I_2$$

If we reverse the procedure – That is, if we first increase  $i_2$  from zero to  $I_2$  and increase  $i_1$  from zero to  $I_1$  – The total energy stored is:

$$W = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 + M_{21} I_1 I_2$$

At any instant of time, the total energy stored in the coupled coils is:

$$w(t) = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 + M i_1 i_2 \quad \text{Assuming that both coil currents entered polarity marked terminals}$$

In general:

$$w(t) = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 \pm M i_1 i_2$$

### Example 32-3

Consider the circuit in Fig.32-5. Determine the coupling coefficient. Calculate the energy stored in the coupled inductors at time  $t = 1\text{s}$  if  $v = 60 \cos(4t + 30^\circ)\text{V}$ .

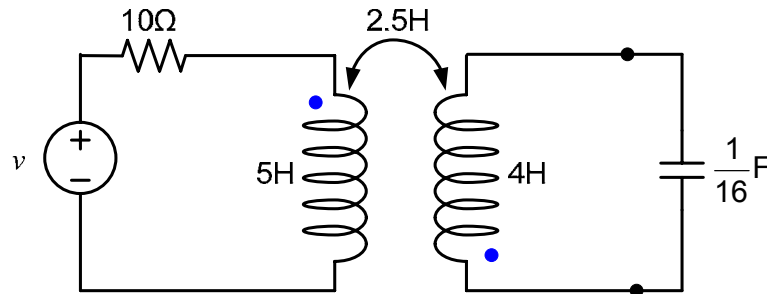


Fig.32-5 Circuit For Example 32-3

### Solution:

The coupling coefficient is

$$k = \frac{M}{\sqrt{L_1 L_2}} = \frac{2.5}{\sqrt{20}} = 0.56$$

- Means that the inductors are tightly coupled.
- To find the energy stored, we need to obtain the frequency domain equivalent of the circuit

$$60 \cos(4t + 30^\circ)\text{V} \Rightarrow 60 \angle 30^\circ, \omega = 4 \text{ rad/s}$$

$$5\text{H} \Rightarrow j\omega L_1 = j20\Omega$$

$$2.5\text{H} \Rightarrow j\omega M = j10\Omega$$

$$4\text{H} \Rightarrow j\omega L_2 = j16\Omega$$

$$\frac{1}{16}\text{F} \Rightarrow \frac{1}{j\omega C} = -j4\Omega$$

The frequency domain equivalent is shown in Fig.32-6 below:

### Solution (Cont):

We now apply mesh analysis

$$(10 + j20)I_1 + j10I_2 = 60\angle 30^\circ$$

$$j10I_1 + (j16 - j4)I_2 = 0$$

Or

$$I_1 = -1.2I_2$$

This yields

$$I_2(-12 - j14) = 60\angle 30^\circ \Rightarrow I_2 = 3.254\angle 160.6^\circ \text{ A}$$

$$I_1 = -1.2I_2 = 3.905\angle -19.4^\circ \text{ A}$$

In the time domain

$$i_1 = 3.905 \cos(4t - 19.4^\circ),$$

$$i_2 = 3.254 \cos(4t + 160.6^\circ)$$

At time  $t=1\text{s}$ ,  $4t= 4\text{rad}=229.2^\circ$ ,

$$i_1 = 3.905 \cos(229.2^\circ - 19.4^\circ) = -3.389\text{A},$$

$$i_2 = 3.254 \cos(229.2^\circ + 160.6^\circ) = 2.824\text{A}$$

**Solution (Cont):**

The total energy stored in the coupled inductors is

$$w = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 + M i_1 i_2$$

$$w = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 + M i_1 i_2$$

$$= \frac{1}{2} (5)(-3.389)^2 + \frac{1}{2} (4)(2.824)^2 + 2.5(-3.389)(2.824) = 20.73J$$

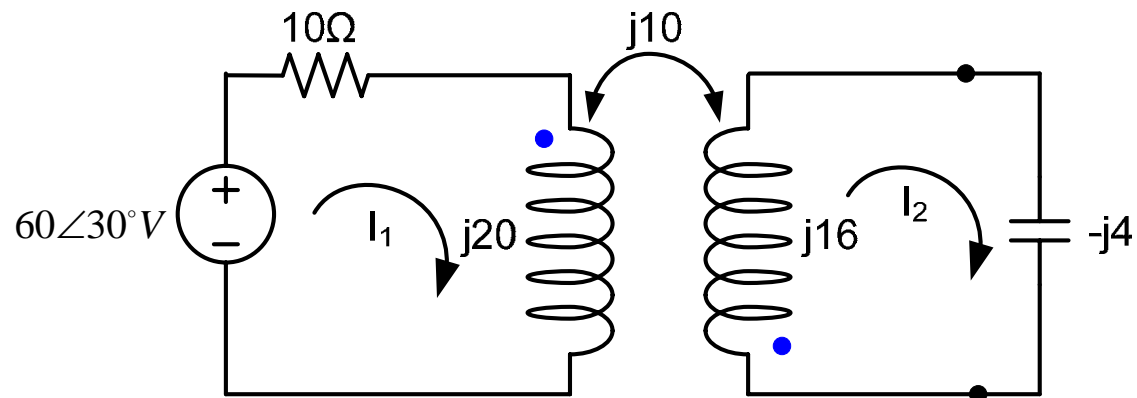


Fig.32-6 Frequency domain Equivalent Circuit For Example 32-3

### Self Test:

- ❖ When  $k$  equals zero, two inductors in series combine by  
a) addition      b) subtraction      c) product-over-sum      d) multiplication  
answer: a
- ❖ Two parallel inductors with no mutual inductance combine by  
a) addition      b) subtraction      c) product-over-sum      d) multiplication  
answer: c
- ❖ If  $N=200$  and a rate of change of flux is  $0.4 \text{ Wb/s}$ . The voltage induced in the inductor is?  
a) 50      b) 80      c) 200      d) 500  
answer: b
- ❖ Two inductors are wound on a ferromagnetic core. The first Inductor has  $N_1=200$  and a rate of change of flux is  $0.4 \text{ Wb/s}$ . If the second Inductor has  $N_2=125$  turns and the coefficient of coupling is unity, how much voltage is induced in the second inductor?  
a) 50      b) 80      c) 200      d) 500  
answer: a
- ❖ The self-inductances of the coils in Fig.32-4 are  $L_1= 18 \text{ mH}$  and  $L_2 = 32 \text{ mH}$ . If the coefficient of coupling is  $0.85$ , calculate the energy stored in the system in millijoules when  
a)  $i_1 = 6 \text{ A}$ ,  $i_2 = 9 \text{ A}$ ;    b)  $i_1 = -6 \text{ A}$ ,  $i_2 = -9 \text{ A}$ ;    c)  $i_1 = -6 \text{ A}$ ,  $i_2 = 9 \text{ A}$ ;    d)  $i_1 = 6 \text{ A}$ ,  $i_2 = -9 \text{ A}$ .  
What conclusion do you draw?  
answer:  
a)  $2721.60 \text{ mJ}$ ;      b)  $2721.60 \text{ mJ}$ ;    c)  $518.40 \text{ mJ}$ ;    d)  $518.40 \text{ mJ}$ .  
Same answer when both current are entering or both leaving, and same answer when one is leaving and one is entering.