

### Problem 10-1

$$R = 10 \Omega, \alpha = \pi/3, V_s = 120 \text{ V}, V_m = \sqrt{2} \times 120 = 169.7 \text{ V}$$

$$\text{From Eq. (10-1), } V_{dc} = 0.2387 V_m \text{ and } I_{dc} = 0.2387 V_m/R$$

$$\text{From Eq. (10-4), } V_{rms} = 0.4485 V_m \text{ and } I_{rms} = 0.4485 V_m/R$$

$$\text{From Eq. (3-1), } P_{dc} = V_{dc} I_{dc} = (0.2387 V_m)^2/R$$

$$\text{From Eq. (3-2), } P_{ac} = V_{rms} I_{rms} = (0.4485 V_m)^2/R$$

(a) From Eq. (3-3) the rectification efficiency,

$$\eta = (0.2387 V_m)^2 / (0.4485 V_m)^2 = 28.32 \%$$

(b) From Eq. (3-5) the form factor is,  $FF = 0.4485 V_m / (0.2387 V_m) = 1.879$   
or 187.9 %

(c) From Eq. (3-7) the ripple factor,  $RF = [1.879^2 - 1]^{1/2} = 1.591$  or 159.1%

(d) The rms voltage of transformer secondary is  $V_s = V_m / \sqrt{2} = 0.707 V_m$

The rms value of the transformer secondary current is the same as that of the load,  $I_s = 0.4485 V_m/R$

$$\text{Volt-Amp (VA) of transformer, } VA = V_s I_s = 0.707 V_m \times 0.4485 V_m/R$$

$$\text{From Eq. (3-8) } TUF = 0.2387^2 / (0.707 \times 0.4485) = 0.1797 \text{ and } 1/TUF = 5.56$$

(e) The peak inverse voltage,  $PIV = V_m = 169.7 \text{ V}$

### Problem 10-2

$$R = 10 \Omega, V_s = 120 \text{ V}, V_n = 0.25 \text{ pu}, V_m = \sqrt{2} \times 120 = 169.7 \text{ V}$$

(a) From Eq. (10-3),  $0.25 = 0.5 (1 + \cos \alpha)$  or  $\alpha = 120^\circ$

(b) From Eq. (10-1),  $V_{dc} = 0.0796 V_m = 13.5 \text{ V}$ ,  $I_{dc} = 13.5/10 = 1.35 \text{ A}$

From Eq. (10-4),  $V_{rms} = 0.221 V_m = 37.5 \text{ V}$ ,  $I_{rms} = 37.5/10 = 3.75 \text{ A}$

### Problem 10-7

$$V_s = 120 \text{ V}, f = 60 \text{ Hz}, \alpha = \pi/3, V_m = \sqrt{2} \times 120 = 169.7 \text{ V}$$

$$\text{From Eq. (10-9), } I_1 = (2 \sqrt{2} I_a / \pi) = 0.9003 I_a$$

$$I_s = I_a$$

(a)  $HF = [(I_s/I_1)^2 - 1]^{1/2} = 0.4834$  or 48.34 %

(b) From Eq. (10-10),  $\phi_1 = -\pi/3$  and  $DF = \cos(-\pi/3) = 0.5$

(c)  $PF = (I_1/I_s) DF = (2\sqrt{2}/\pi) \times 0.5 = 0.45$  (lagging)

### Problem 10-8

$$R = 10 \Omega, V_s = 120 \text{ V}, V_n = 0.25 \text{ pu}, V_m = \sqrt{2} \times 120 = 169.7 \text{ V}$$

(a) From Eq. (10-6),  $0.25 = \cos \alpha$  or  $\alpha = 75.5^\circ$

(b) From Eq. (10-5),  $V_{dc} = 0.1591 V_m = 27 \text{ V}$ ,  $I_{dc} = 27/10 = 2.7 \text{ A}$

From Eq. (10-7),  $V_{rms} = 0.70 V_m = 120 \text{ V}$ ,  $I_{rms} = 120/10 = 12 \text{ A}$

(c)  $I_{av} = I_{dc} = 1.35 \text{ A}$ ,  $I_R = I_{rms} = 12/\sqrt{2} = 8.49 \text{ A}$

(d) Assuming that the harmonics are negligible, the output power,  $P_o = 12^2 \times 10 = 1440 \text{ W}$

The rms voltage of transformer secondary is  $V_s = 120 \text{ V}$

The rms value of the transformer secondary current is the same as that of the load,  $I_s = I_{rms} = 12 \text{ A}$

Volt-Amp (VA) of transformer,  $VA = V_s I_s = 120 \times 12 = 1440$

$pf = 1440/1440 = 1.0$

### Problem 10-22

$$\alpha = 2\pi/3$$

From Eq. (10-29),  $I_1 = (\sqrt{6}/\pi) I_a = 0.7797 I_a$

$$I_s = \left[ \frac{2}{2\pi} \int_{\pi/6+\alpha}^{5\pi/6+\alpha} I_a^2 d\theta \right]^{1/2} = I_a \sqrt{\frac{2}{3}} = 0.8165 I_a$$

(a)  $HF = [(I_s/I_1)^2 - 1]^{1/2} = [(\pi/3)^2 - 1]^{1/2} = 0.3108$  or 31.08 %

(b) From Eq. (10-28),  $DF = \cos(-\alpha) = 0.5$

$PF = (I_1/I_s) \times DF = (3/\pi) DF = 0.478$  (lagging)

### Problem 10-23

$$V_L = 220 \text{ V}, f = 60 \text{ Hz}, R = 10 \Omega, V_s = 220/\sqrt{3} = 127 \text{ V},$$

$$V_m = \sqrt{2} V_s = 179.6 \text{ V}, V_n = 0.25 \Omega$$

$$V_{dm} = 3 \sqrt{3} V_m / \pi = 3 \sqrt{3} \times 179.6 / \pi = 297 \text{ V}$$

$$V_{dc} = 0.25 \times 297 = 74.26 \text{ V}$$

(a) From Eq. (10-26),  $0.25 = \cos \alpha$ , or  $\alpha = 75.5^\circ$

(b)  $I_{dc} = V_{dc} / R = 74.26 / 10 = 7.426 \text{ A}$

From Eq. (10-27),

$$V_{rms} = 6 \times 179.6 [(1/4) + (3 \sqrt{3} / 8\pi) \cos (2 \times 75.5)]^{1/2} = 115.6 \text{ V}$$

$$I_{rms} = 115.6 / 10 = 11.56 \text{ A}$$

(c)  $I_{DT} = I_{dc} / 3 = 7.426 / 3 = 2.48 \text{ A}$

$$I_{RT} = I_{rms} \sqrt{(2/6)} = 11.56 \sqrt{(2/6)} = 6.67 \text{ A}$$

(d) From Eq. (3-3)

$$\eta = 74.26 \times 7.426 / (115.6 \times 11.56) = 0.4123 \text{ or } 41.23 \%$$

(e)  $I_s = I_{rms} \sqrt{(4/6)} = 9.44 \text{ A}$ ,

$$VI = 3 V_s I_s = 3 \times 127 \times 9.44 = 3597 \text{ W}$$

From Eq. (3-8),  $TUF = 74.26 \times 7.426 / 3597 = 0.1533$

(f) The output power,  $P_o = I_{rms}^2 R = 11.562^2 \times 10 = 1337 \text{ W}$

$$\text{pf} = 1337 / 3597 = 0.3717 \text{ (lagging)}$$