

بسم الله الرحمن الرحيم

King Fahd University of Petroleum and Minerals
Department of Electrical Engineering

Semester I 2005/2006

EE303 Electronics II

Quiz (4)

ATTEMPT ALL QUESTIONS
TIME ALLOWED 10 Minutes

Assuming **ideal** transistors, can the circuit shown oscillate? Justify your answer.
An answer without justification can not carry any credit

