

بسم الله الرحمن الرحيم

King Fahd University of Petroleum and Minerals
Department of Electrical Engineering

Semester II 2006/2007

Electronic Circuits II (EE303)

Quiz (3)

ATTEMPT ALL QUESTIONS
TIME ALLOWED 10 MINUTES

Assuming ideal operational amplifier, sketch the transfer function of the circuit shown in Figure. SHOW THE MOST IMPORTANT POINTS.

