

3.8 a)

$$5 // 20 = \frac{100}{25} = 4 \Omega \quad (5 // 20 + 9 // 18 + 10 = 20 \Omega)$$

$$9 // 18 = \frac{162}{27} = 6 \Omega \quad (20 // 30 = \frac{600}{50} = 12 \Omega)$$

$$R_{ab} = 5 + 12 + 3 = 20 \Omega$$

3.12

$$60 // 30 = 20 \Omega$$

$$i_{30 \Omega} = \frac{25(75)}{125} = 15 \text{ A}$$

$$V_o = 15(20) = 300 \text{ V}$$

$$V_o + 30i_{30} = 750 \text{ V}$$

$$V_g - 12(25) = 750$$

$$\therefore V_g = 1050 \text{ V}$$

3.15 a)

$$V_{9 \Omega} = 1(9) = 9 \text{ V} \quad (i_{2 \Omega} = \frac{9}{2+1} = 3 \text{ A})$$

$$i_{4 \Omega} = 1 + 3 = 4 \text{ A} \quad (V_{25 \Omega} = 4(4) + 9 = 25 \text{ V})$$

$$i_{25 \Omega} = \frac{25}{25} = 1 \text{ A} \quad (i_{3 \Omega} = i_{25 \Omega} + i_{9 \Omega} + i_{20 \Omega} = 1 + 1 + 3 = 5 \text{ A})$$

$$V_{40 \Omega} = V_{25 \Omega} - V_{3 \Omega} = 25 - (-5)(3) = 40 \text{ V}$$

$$i_{40 \Omega} = \frac{40}{40} = 1 \text{ A} \quad (i_{5 // 20 \Omega} = i_{40 \Omega} + i_{25 \Omega} + i_{4 \Omega} = 1 + 1 + 4 = 6 \text{ A})$$

$$V_{5 // 20 \Omega} = 4(6) = 24 \text{ V} \quad (V_{32 \Omega} = V_{40 \Omega} + V_{5 // 20 \Omega} = 40 + 24 = 64 \text{ V})$$


$$i_{32 \Omega} = \frac{64}{32} = 2 \text{ A} \quad (i_{10 \Omega} = i_{32 \Omega} + i_{5 // 20 \Omega} = 2 + 6 = 8 \text{ A})$$

$$V_g = 10(8) + V_{32 \Omega} = 80 + 64 = 144 \text{ V}$$

$$b) P_{20 \Omega} = (24)^2 / 20 = 28.8 \text{ W}$$

3.51 (continued)

3/3

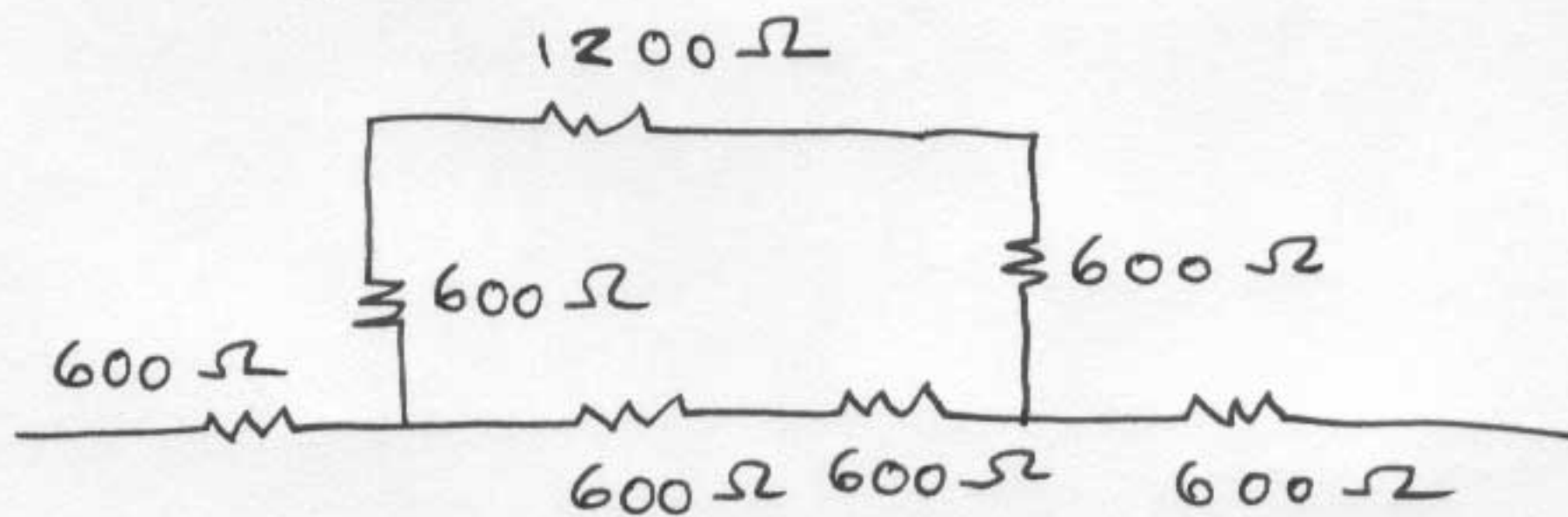

Now the $2400\ \Omega$ is in parallel with $1200\ \Omega$.

This combination reduces to:

$$1200 // 2400 = \frac{1200(2400)}{1200+2400} = 800\ \Omega$$

$$\therefore R_{ab} = 600 + 800 + 600 = 2000 = 2\text{K}\ \Omega.$$

3.46

2/3

Note the bridge structure is balanced, because
 $15 \times 5 = 25 \times 3$.

\therefore There is no current in the $5k\Omega$ resistor.

This means the equivalent resistance of the circuit is:

$$R_{eq} = 0.375 + \frac{15(25)}{40} + \frac{(3)(5)}{8} = 11,625 \Omega$$

The source current is $\frac{60}{11,625} = 5.16 \text{ mA}$, from left to right through the 375Ω resistor.

The current down through the $3k\Omega$ resistor is:

$$i_{3k} = 5.16 \times \frac{5}{8} = 3.23 \text{ mA}$$

$$\therefore P_{3k} = (3.23 \times 10^{-3})^2 (3000) = 31.2 \text{ mW}$$

3.51 The top of the pyramid can be replaced by a resistor equal to:

$$R_1 = \frac{3.6(1.8)}{5.4} = 1.2 \text{ k}\Omega$$

The lowest left + right deltas can be replaced by wyes. Each resistance in the wye equals 600Ω . Thus the circuit can be reduced to: