

King Fahd University of Petroleum & Minerals
Electrical Engineering Department

EE204 Fundamentals of Electric Circuits

Semester 092

Final Exam

7:30 AM June 13, 2010 Sunday

Time : 2 hours and 30 minutes

Student Name	
Student ID	
Serial #	
Section # (or circle your instructor's name)	DR. M ABDUL HALEEM DR. AHMED MASOUD DR. HAMMI OUALID DR. AL-SAYYED AL-AKHDAR DR. AHMED YAMANI DR. K QURESHI
Lab Section number or Lab Instructor's Name	

Problem 1	10	
	10	
Problem 2	10	
	10	
Problem 3	10	
	10	
Problem 4	10	
Problem 5	10	
Problem 6	10	
	10	
Total	100	

Solve all problems


Put your final results in the provided text boxes

Organize and clearly show the steps of your work and results.

Problem 1:


a) For the given circuit find:

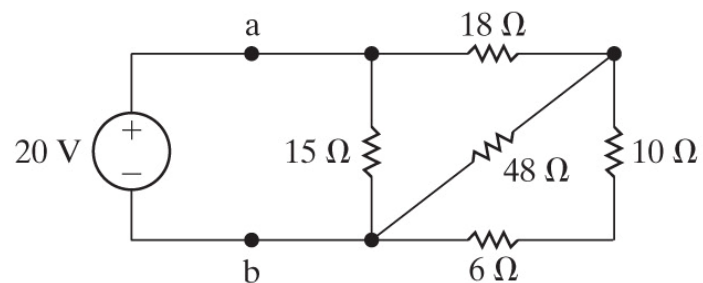1. The equivalent resistance R_{ab} as seen by the voltage source .
2. The power delivered by the voltage source.



$R_{ab} =$
$P_{20V} =$

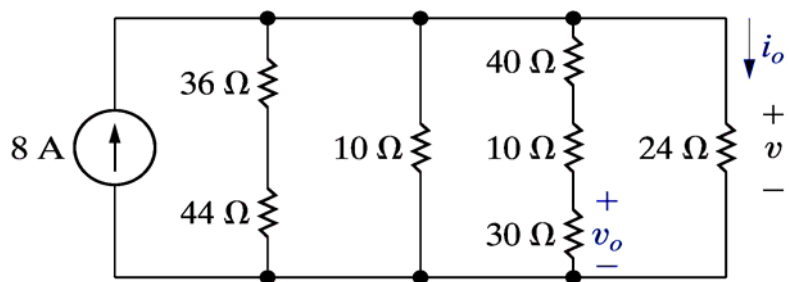
- b) For the circuit shown,
1. Use current division to find the current i_o
 2. Use voltage division of v to find the voltage v_o .



$i_o =$
$v_o =$


Problem 2:

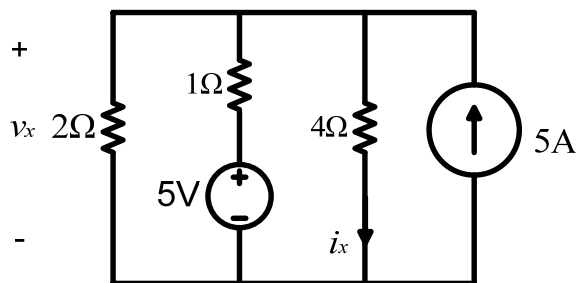a) Determine the voltage v_x and the current i_x in the circuit shown using node-equation method.



$v_x =$
$i_x =$

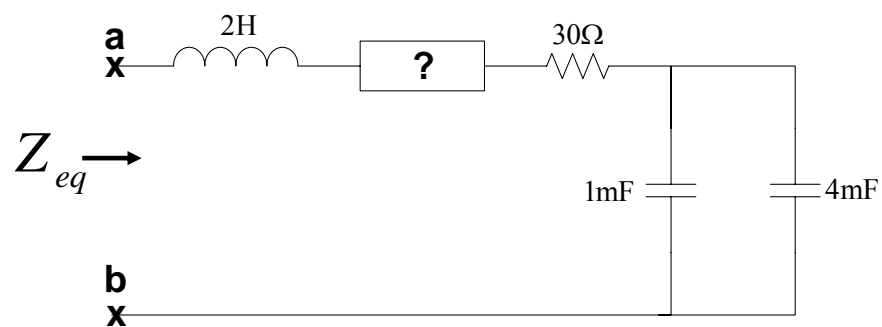b) In the circuit shown $\omega = 50 \text{ rad/s}$, and the equivalent impedance $Z_{eq} = 30 + j76 \Omega$. Find the type of the missing element indicated by the question mark (is it a resistor, a capacitor or an inductor) and its value.




Answer:

Problem 3:


a) For the following circuit,

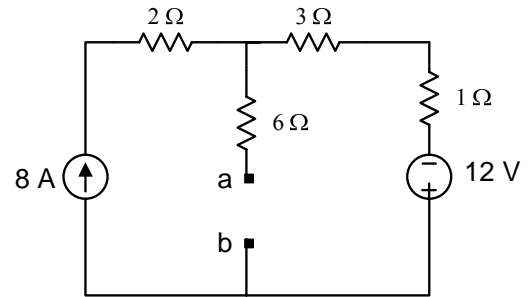1. Find the resistor to be connected between terminals a-b that gets the maximum power transfer.
2. Calculate the maximum power absorbed by the resistor found in part 1.



$R_{TH} =$
$P_{max} =$

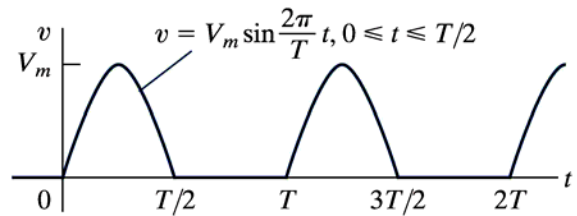b) Calculate the effective (RMS) value for the periodic voltage waveform shown.




$V_{rms} =$

Problem 4:

For the circuit shown

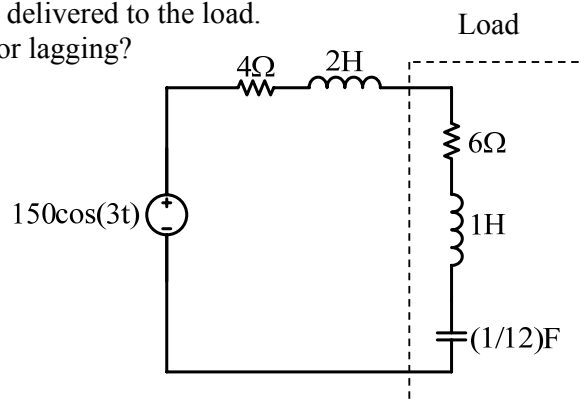
1. Calculate the average power and the reactive power delivered to the load.
2. Calculate the power factor of the load. Is it leading or lagging?



$P_{av} =$
$Q =$
$pf =$

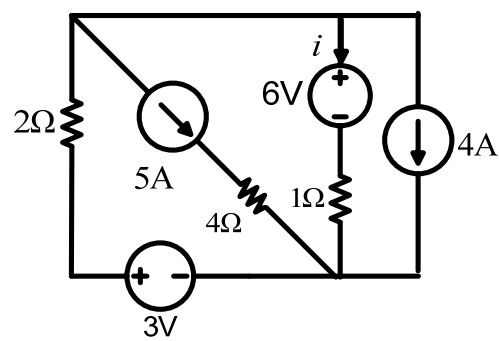Problem 5:

Find the current i in the circuit shown using superposition principle.




$i =$

Problem 6:

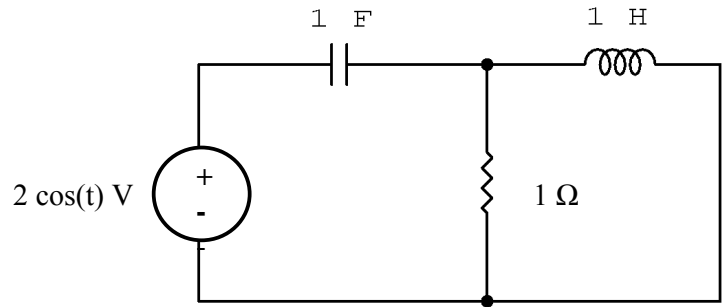a) For the following circuit **use mesh-currents equation method** to:

- 1- compute the power dissipated by the 1Ω resistor
- 2- compute the power factor at the voltage source.
- 3- compute the complex power absorbed by the circuit connected to the source.




$$P_{1\Omega} =$$

$$pf =$$

$$\hat{P} =$$

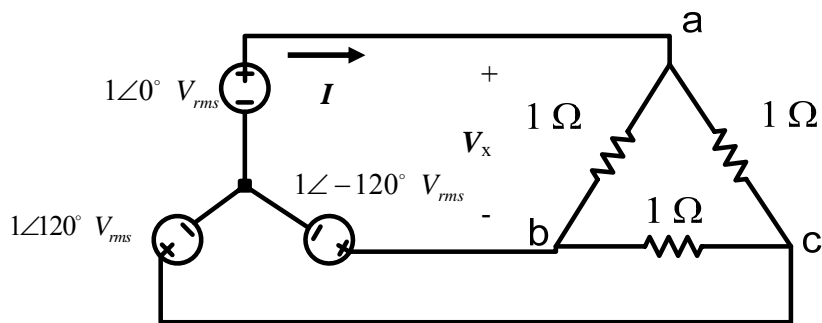b) Compute I and V_x in the three-phase circuit shown.



$$I =$$

$$V =$$