



King Fahd University of Petroleum & Minerals  
Electrical Engineering Department

**EE204 : Electric Circuits**

Semester 101

First Major Exam

Time : 1 hr 30 min

Section No. \_\_\_\_\_

Student Name \_\_\_\_\_

Student ID \_\_\_\_\_


Q#1	10	
Q#2	10	
Q#3	10	
TOTAL	30	

**Problem I:**

**Part 1: (5 points)**

Consider the circuit shown above:


1. Calculate the current  $i_F$ . (1 point)
  2. Calculate the voltage  $V_G$ . (1 point)
  3. Calculate the voltage  $V_I$ . (1 point)
  4. Calculate the power associated with the element B. (2 points)
- 

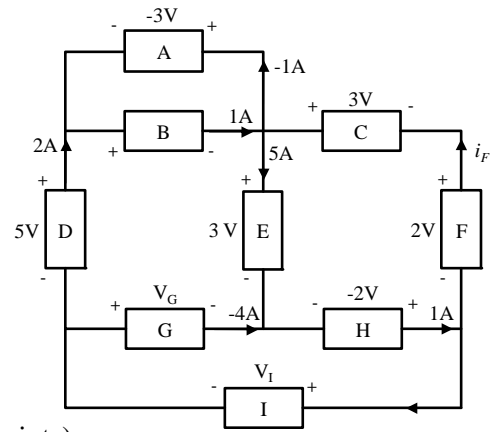

Problem I:

Part 2: (5 points)


For the circuit shown below, use KVL, KCL, Ohms law along with series /parallel reduction to compute the current  $I$  and the voltage  $V$ .

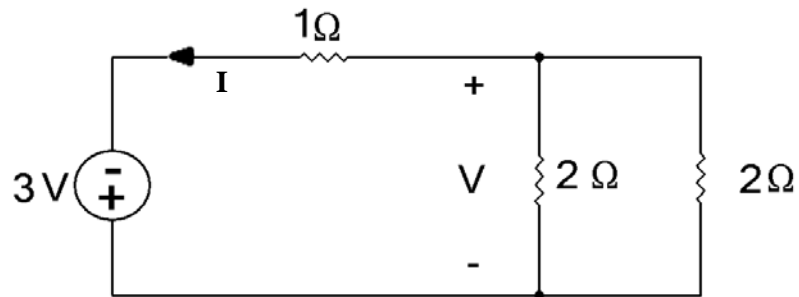

Problem II:

Part 1: (5 points)

Using circuit reduction technique, find the value of current  $I_x$ .

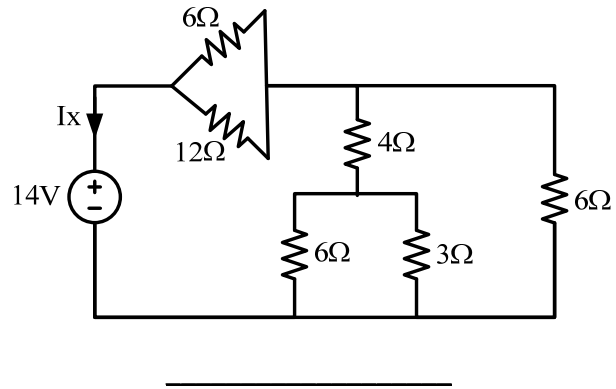

Problem II:

Part 2: (5 points)

If the current in a circuit is


$$i = \begin{cases} 25 \text{ A} & 0 \leq t \leq 2 \\ -25 \text{ A} & 2 \leq t \leq 6 \\ 25 \text{ A} & 6 \leq t \leq 8 \end{cases}$$

- Sketch the current as a function of  $t$
  - Find the charge  $Q(t)$  flowing in the circuit as a function of  $t$
  - Sketch  $Q(t)$ .
-

Problem III:

Part 1: (5 points) Use current divider rule to find:

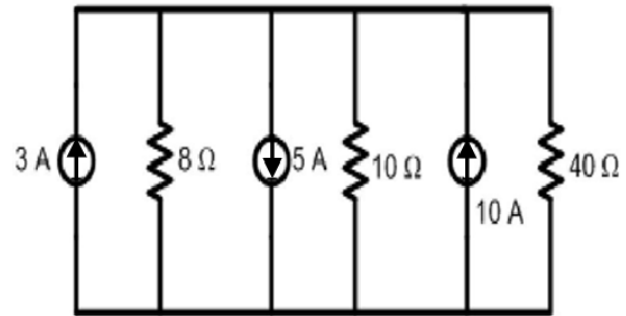
1. Current flowing down in the 10 Ohms resistor.
2. The power associated with the 10 A current source
3. State whether this power is been absorbed or delivered.



---

Problem III:

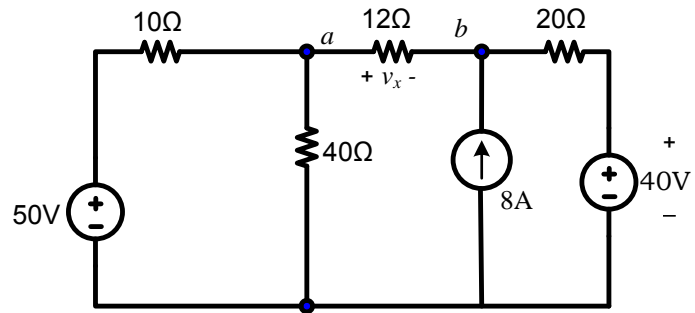Part 2: ( 5 points) Apply source transformations to reduce the circuit shown to a single loop, then find  $v_x$ .



\_\_\_\_\_