



King Fahd University of Petroleum & Minerals
Electrical Engineering Department
Fall 2011 (111)

EE 203 – Final Exam
Monday, January 16, 2011
7:00-10:00 PM

Name	
ID	

	Dr. W. Mesbah	Dr. O. Hammi
Section	1 and 2	3 and 4

Problem	1 (out of 10)	2 (out of 10)	3 (out of 10)	4 (out of 10)	5 (out of 10)	6 (out of 10)	Total (out of 60)
Grade							

Important:

- **Final answers must be written in the specified boxes. The steps should be included.**

Problem 1 – Part A

For the circuit shown in Figure 1-A, the voltage drop across each conducting diode is 0.7V.

a) Find the output voltage V_o .[2 points]

 


Figure 1-A

$V_o =$

b) Find the current I_{D1} .[1 point]

$I_{D1} =$

c) Find the current I_{D2} .[1 point]

$I_{D2} =$

Problem 1 – Part B

For the circuit shown in Figure 1-B, the Zener diode has a voltage drop of 9.1V at 9mA, $r_z=30\Omega$, and $I_{zk}=0.3\text{mA}$.

- a) Find the output voltage V_o with no load connected.
[2 points]

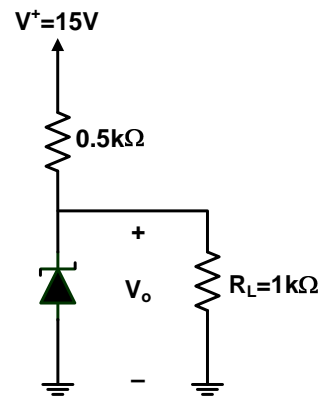


Figure 1-B

$V_o =$

- b) Find the output line regulation with no load connected.[2 points]

- c) For what range of values of R_L , the diode still operates in the breakdown region. (For this part, assume $r_z=0\Omega$).[2 points]

Problem 2

For the amplifier shown in Figure 2, assume that the NMOS has $V_t=1V$, $\mu_n C_{ox} W/L=1mA/V^2$, and $\lambda=0.01V^{-1}$.


 


Figure 2

 

- a) Sketch the DC circuit in the designated box. **[1 point]**
- b) Neglecting the effect of λ (**only in this part**), calculate the DC values I_{DS} and V_{DS} . **[2 points]**

$I_{DS} =$


$V_{DS} =$

- c) Calculate the small-signal parameters g_m and r_0 . **[2 points]**

$g_m =$

$r_0 =$

 d) Draw the small-signal AC circuit using the **π model** of the transistor. [2 points]



e) Use the small-signal ac circuit to write the expressions of R_{out} , R_{in} , and the gain v_o/v_i (for the gain calculation **ONLY**, assume $R_G = \infty$). [3 points]

$R_{out} =$

$R_{in} =$

$v_o/v_i =$

Problem 3:

Consider the circuit shown in Figure 3. The BJT transistor has $\beta=100$. Neglect the Early effect.


 


Figure 3

 - a) Draw the small signal equivalent circuit using the transistor's **T model**. [2 points]



- b) Find the expressions of the input resistance R_{in} and the output resistance R_{out} of the amplifier. [2 points]

$R_{in} =$

$R_{out} =$

c) Calculate the values of the input resistance R_{in} and the output resistance R_{out} of the amplifier. [2 points]

$R_{in} =$

$R_{out} =$

d) Find the expression of the voltage gain v_{out}/v_{sig} in terms of R_{in} and/or R_{out} . (Do not replace R_{in} and/or R_{out} by the expression found in question b)) [2 points]

$$v_{out}/v_{sig} =$$

e) If the voltage v_{be} should not exceed 5mV. What is the maximum input voltage v_{sig_max} .
[2 points]

$$v_{in_max} =$$

Problem 4:

Consider the circuit of Figure 4. The transistors Q_1 and Q_2 have $k'_n W/L = 2.5 \text{ mA/V}^2$, $V_t = 1 \text{ V}$, and $\lambda = 0$. The DC current through R_{ss} is 1 mA .


 


Figure 4

 

- a) Sketch the DC circuit in the designated box. [2 points]

- b) Find the required value of the DC voltage V_{CM} . [2 points]

$V_{CM} =$

c) Find the value of R_D that results in a differential gain A_d of -8 V/V. [2 points]

$R_D =$

d) Determine the DC voltage at the drain of Q_1 . [2 points]


$V_D =$

e) Calculate the single-ended common mode gain (for an ac input signal). [2 points]

$A_{CM} =$

Problem 5 – Part A:

Consider the voltage transfer function of the CMOS shown in Figure 5-A. Indicate, **on the same figure**, the mode of operation of the NMOS and PMOS transistors in each region of the voltage transfer characteristic. Clearly show the limits of each region. [5 points]

 

Problem 5 – Part B:

a) What is the minimum number of transistors required to implement the following logic function using CMOS gates. [2 points]

$$Y = \overline{A}BC + ABC + AB\overline{C} + \overline{A}B\overline{C} + \overline{A}\overline{B}C$$

Minimum number =

b) If “p” represent W/L of the PMOS of the basic inverter, design the PUN and the sizing of each transistor (show the sizes on the PUN circuit) for the function:

$Y = \overline{B}C + B(A + \overline{A}\overline{C})$. (Do not simplify or change the equation. You do not have to plot the inverters). [3 points]



Problem 6:

Consider the ECL circuit shown in Figure 6. The transistors used have $V_{BE}=0.7\text{V}$ at $I_E=1\text{mA}$. The current $I_{tot}=4\text{mA}$ all the time. Neglect the base currents when collector currents are present. Assume that $\beta_{Q2}=\beta_{Q3}=100$. Consider only the **OR** output at the emitter of Q_2 .

 


Figure 6

- a) If we define the voltages V_{IL} and V_{IH} when the current in one branch is **95%** of I_{tot} . Calculate the voltages V_{IL} and V_{IH} for the OR output. **[4 points]**

$V_{IL} =$
$V_{IH} =$

b) Calculate the voltages V_{OL} and V_{OH} for the OR output. **[4 points]**

$V_{OL} =$

$V_{OH} =$

c) Calculate the noise margins N_{ML} and N_{MH} for the OR output. **[2 points]**

$N_{ML} =$

$N_{MH} =$