



King Fahd University of Petroleum & Minerals
Electrical Engineering Department
Winter 2012 (112)

EE 203 – Final Exam
Tuesday, May 22, 2012
7:30-10:30 AM

Name					
ID					
	Dr. M. Al-Gahtani	Dr. H. Al-Zaher	Dr. O. Hammi	Dr. W. Mesbah	Dr. H. Ragheb
Section	3 and 6	5	1, 4 and 8	7	2

Problem		Grade
Part A (28 points)		
Part B (42 points)	Problem 1 (14 points)	
	Problem 2 (14 points)	
	Problem 3 (14 points)	
Total (70 points)		

Note: Part 1 is made of multiple choices questions, only one answer is correct. Clearly fill the box beside the right answer (■). Unclear or multiple answers will be considered as wrong.

Part A: Multiple Choices Questions


[2 points each]

In each of the questions below, clearly fill the box beside the correct answer.

Question 1:

For the OPAMP circuit shown below, where $R_1 = 2\text{ k}\Omega$, $R_2 = R_3 = R_4 = 1\text{ k}\Omega$ and $R_a = 2\text{ k}\Omega$ and $R_b = 3\text{ k}\Omega$. The output voltage V_o is given by:

- $V_o = 3V_1 + 6V_2 - 3V_3$.
- $V_o = 6V_1 - 6V_2 - 3V_3$.
- $V_o = 3V_1 + 6V_2 + 3V_3$.
- $V_o = 3V_1 - 6V_2 + 3V_3$.

 

Question 2:

The voltage drop across a reverse biased diode is about:

- 0.0 V
- 0.2 V
- 0.7 V
- unknown

Question 3:


In a forward biased pn junction:

- The electrons flow from the p side to the n side.
- The electrons flow from the n side to the p side.
- The electrons remain in the n region.
- The electrons remain in the p region.

Question 4:

The voltage regulator shown in the figure below, uses a Zener diode having a resistance $r_z=2\Omega$, Find the change in the output voltage (V_o) when the input voltage (V^+) changes by 1.3V.


- $\Delta V_o = 1.2 \text{ mV}$
- $\Delta V_o = 102 \text{ mV}$
- $\Delta V_o = 65 \text{ mV}$
- $\Delta V_o = 110 \text{ mV}$

 

Question 5:

The circuit shown in the figure below has an ideal opamp and an ideal diode. If a sinusoidal input voltage source is applied, the circuit will work as:


- Half wave rectifier.
- Full wave rectifier.
- Inverting amplifier.
- Difference amplifier.

 

Question 6:

For the MOS circuit shown below, the two transistors are identical and have the following parameters: $V_t = 1\text{V}$, $k'_n \frac{W}{L} = 2 \text{ mA/V}^2$, and $\lambda = 0$. The voltage V_1 and the current I_1 are:

- $V_1 = 1.5 \text{ V}$ and $I_1 = 250 \mu\text{A}$.
- $V_1 = 1.2 \text{ V}$ and $I_1 = 40 \mu\text{A}$.
- $V_1 = 3 \text{ V}$ and $I_1 = 0 \mu\text{A}$.
- $V_1 = -1.5 \text{ V}$ and $I_1 = 200 \mu\text{A}$.

 

Question 7:

The MOSFET can be used as a constant current source when it operates in:

- The pinch-off (saturation) region.
- The linear region.
- The triode region.
- The cut-off region.

Question 8:

The phase shift between the input and output signals in common-emitter amplifiers is:

- 0° .
- 90° .
- 180° .
- 270° .

Question 9:

A receiver requires an output amplifier stage having high input resistance and low output resistance. Which of the following amplifier configurations can be used?

- Common source amplifier.
- Common source amplifier with R_s .
- Common gate amplifier.
- Common drain amplifier.

Question 10:

The BJT can be used as an amplifier if:


- The EB junction is reverse biased and CB junction is forward biased.
- The EB junction is forward biased and CB junction is reverse biased.
- The EB junction is forward biased and CB junction is forward biased.
- The EB junction is reverse biased and CB junction is reverse biased.

Question 11:

For the circuit shown in the figure below, $V_{BE}=0.7V$, the transistor is in the active mode and has $\beta=50$.

The emitter current I_E is given by:

- $I_E = 2.5 \text{ mA}$
- $I_E = 2.65 \text{ mA}$
- $I_E = 2.30 \text{ mA}$
- $I_E = 2.33 \text{ mA}$

 

Question 12:

MOSFET in digital circuits mostly work in:

- Triode and pinch off (saturation) region.
- Triode and cut off region.
- Cut off and pinch off (saturation) region.
- Active and pinch off (saturation) region.

Question 13:


In CMOS logic circuits, V_{IL} is defined as:

- The maximum input voltage that can be considered as high input.
- The minimum input voltage that can be considered as low input.
- The maximum input voltage that can be considered as low input.
- The minimum input voltage that can be considered as high input.

 Question 14:

For the circuit shown in the figure below, the output Y is given by:

- $Y = A \cdot (B + C)$
- $Y = \bar{A} \cdot (\bar{B} + \bar{C})$
- $Y = \bar{A} + (\bar{B} \cdot \bar{C})$
- $\bar{Y} = \bar{A} \cdot (\bar{B} + \bar{C})$




Part B: Problems

Problem 1:

[14points]

Given a MOSFET with the following parameters, $V_t = 2\text{V}$, $k'_n \frac{W}{L} = 5 \text{ mA/V}^2$, and $\lambda = 0$ (no channel length modulation effect), the available DC voltage source is $V_{DD} = 15\text{V}$. It is required to design the common source amplifier shown in the figure below. The biasing point is set to $V_{DS} = \frac{V_{DD}}{2}$ and $I_D = 2.5 \text{ mA}$. The amplifier also must provide a voltage gain $\frac{v_o}{v_{sig}} = -10 \text{ V/V}$.

Find the values of the resistors R_D , R_S and R_2 .

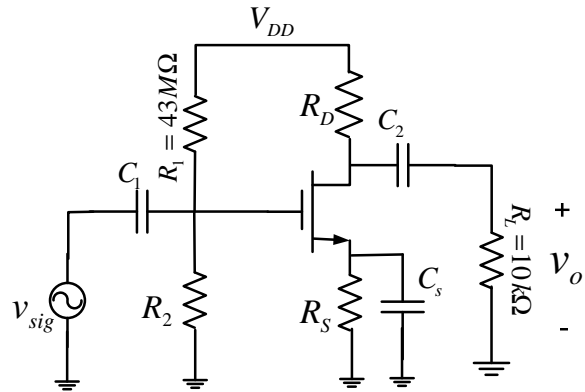


Problem 2:

[14 points]

The transistor in the circuit below is biased in the active region and has $V_{BE}=0.7V$, and $\beta=100$. Neglect the effect of Early voltage.

1. Calculate the value of the input resistance R_{in} .
2. Calculate the value of the output resistance R_{out} .
3. What is the value of the gain (v_o/v_{sig})?
4. Suggest a way to increase the gain (no need for calculations).

 


Problem 3:

[14 points]

Problem 3 - A:

[6 points]

1. Which logic gate has the voltage transfer characteristic shown below?
2. Clearly label V_{OL} , V_{OH} , V_{IL} , and V_{IH} in the figure.
3. Express the noise margins as a function of the voltages V_{OL} , V_{OH} , V_{IL} , and V_{IH} ?

 

Problem 3 - B:**[6 points]**

1. Sketch the complete CMOS logic circuit using **minimum number of transistors** that realize the function below. (Assume that the available inputs are A, B and C).

$$Y = \overline{\overline{B} + A \cdot C}$$

2. What is total number of transistors needed?
3. Find the transistor sizing for the circuit of question 1 in terms of the size of the inverter's transistors.

Problem 3 – C:**[2 points]**

1. Draw the **complete circuit (transistors)** using pass transistor logic (transmission gate) to realize the following function:

$$M = CA + \overline{CB}$$

