

King Fahd University of Petroleum & Minerals

Electrical Engineering Department
EE 204 Fundamentals of Electric Circuits
Second Semester (122)

Exam II
Saturday, 13 March 2013
6:30 PM – 8:00 PM

Name: _____

SHOW YOUR WORK FOR ALL QUESTIONS

ID: _____

Section: _____

Serial No.: _____

Instructors

Dr. HARB
Dr. AL-MUHAINI
Dr. HAMMI
Dr. ALAKHDHAR
Dr. HUSSEIN

Problem	Score	Out of
1		10
2		10
3		10
4		10
5		10
Total		50


Good Luck!!

Problem 1:

Reduce the circuit connected to the load R_L between terminals a b to its Thevenin's equivalent circuit.


What is the value of v_L for maximum power transfer to the load R_L .

Note that: Your steps and figures should be described clearly in order to get full mark.

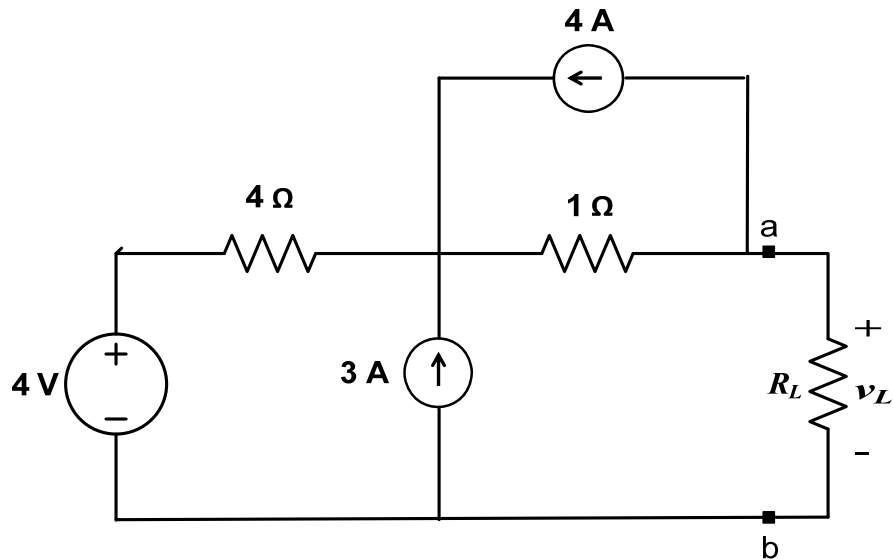

Problem 2:


Use the principle of superposition to solve for the voltage v in the circuit shown.

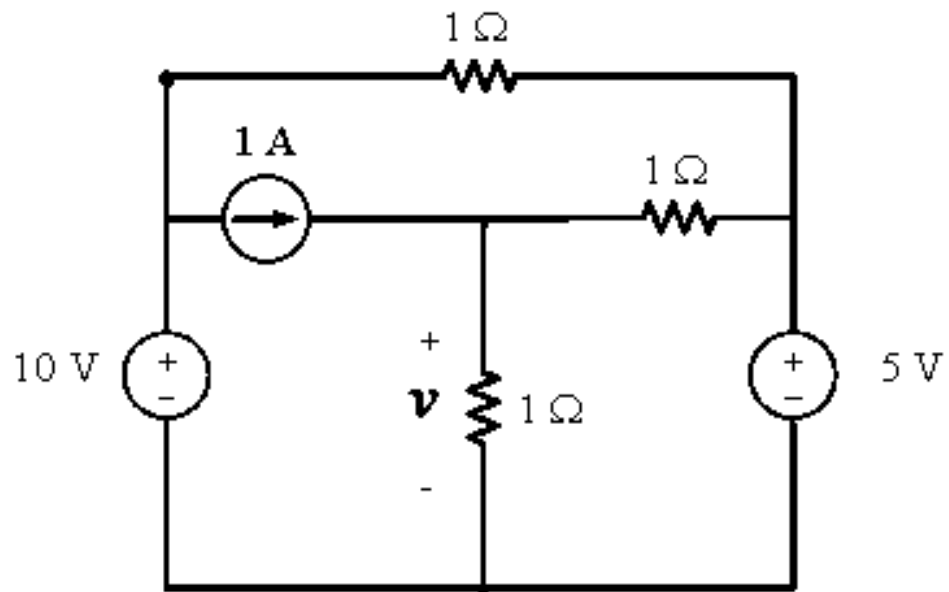

Problem 3:


For the circuit show

- Write the mesh equations for i_1 , i_2 , i_3 , and i_4 .
- Solve for i_1 , i_2 , i_3 , and i_4 .
- Calculate the power supplied by the 3 A current source.

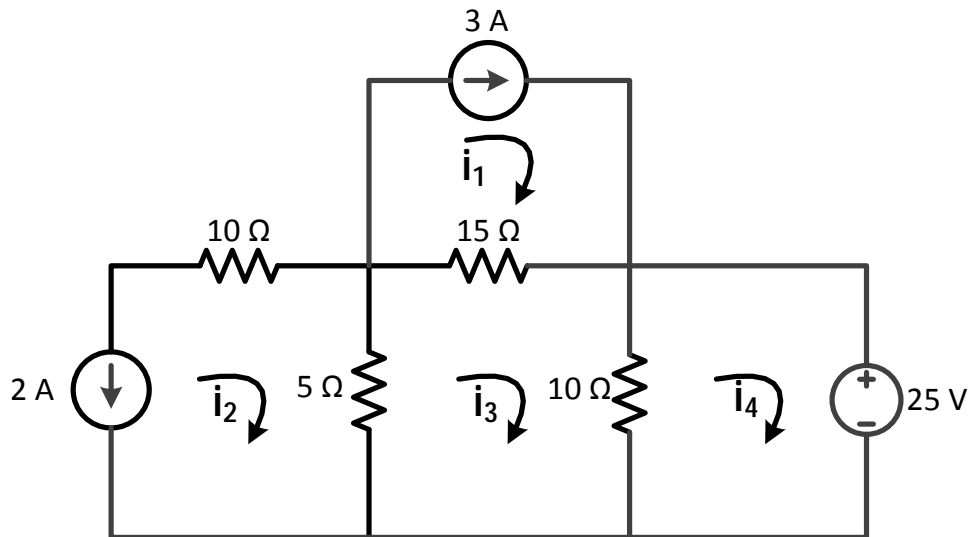

Problem 4:



Write the node voltage equations for the circuit below. (Do not solve the equations)

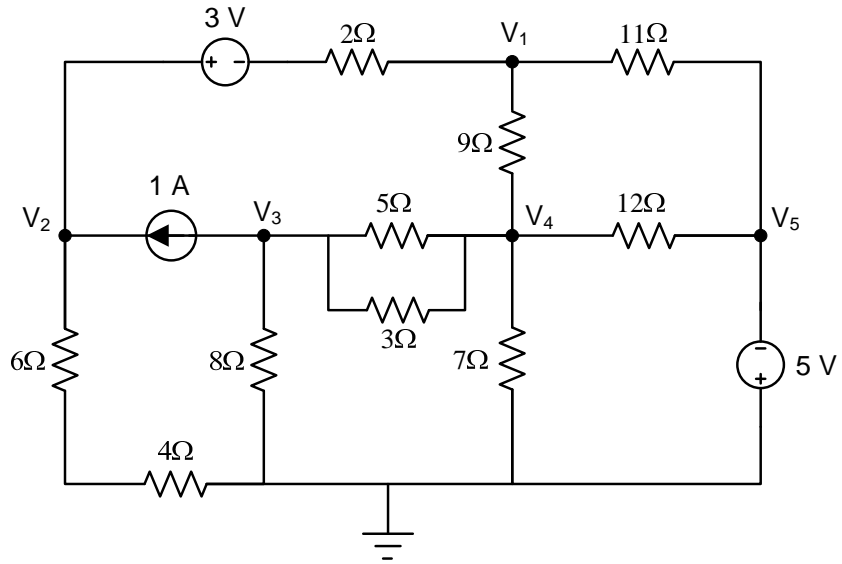

Problem 5:

a) For the shown circuit:

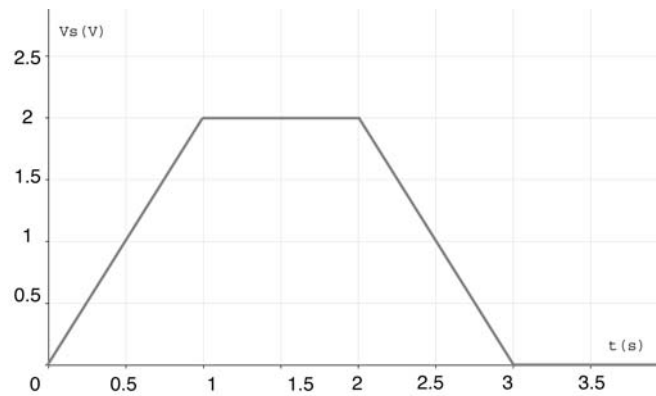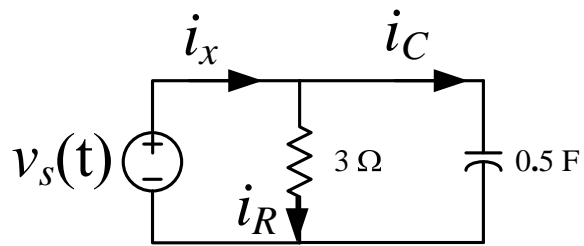- i. Draw $i_R(t)$ against time from $t=0$ to 3.5 s
- ii. Draw $i_C(t)$ against time from $t=0$ to 3.5 s
- iii. Determine $i_x(t)$ at $t = 1.5$ s
- iv. Determine the energy $W(t)$ stored in the capacitor at $t = 1.5$ s



b) Find the equivalent capacitance between terminals a and b for the following circuit

