

Question # 1: (3 Marks)

Consider the half-wave rectifier circuit shown below, let V_s be a sinusoid with 100V peak amplitude, and $R = 500\Omega$. Find the required turns ratio N_2/N_1 of the transformer to have an average output voltage of 10V. (use constant-voltage-drop model with $V_D = 0.7V$).

- a) Sketch the waveform of V_o .
- b) Find the peak current in the diode.
- c) Find the PIV of the diode.

0.75
 0.5
 0.75

$N_2/N_1 = ??$


$V_{oav} = 10V = \frac{V_{opeak}}{\pi} \Rightarrow$

$V_{opeak} = 31.4V$


$V_{ipeak} = V_{opeak} + V_D = 31.4 + 0.7 = 32.1V$

$\frac{N_2}{N_1} = \frac{V_{ipeak}}{V_{speak}} \approx \frac{1}{3}$

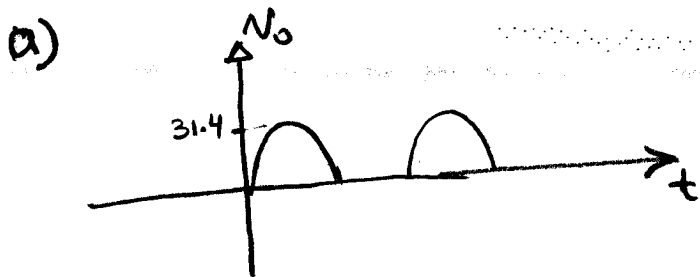b) $I_{Peak} = \frac{V_{opeak}}{R} = \frac{31.4}{500} = 62.8mA$




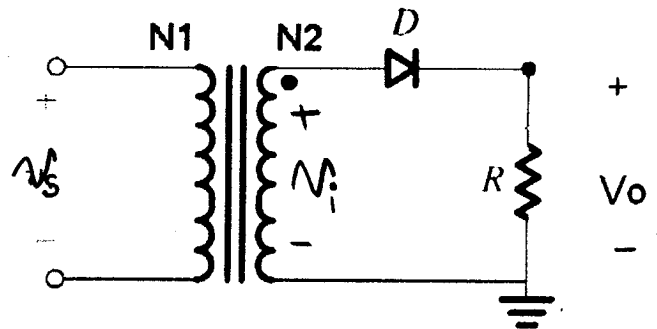
c) $\times PIV = V_{ipeak} \approx 32.1V$



Question # 2:

a). Assuming constant voltage drop model with $V_{D0}=0.7V$ for the diodes shown below, use thevenin's theorem to simplify the circuit and thus find the values of labeled voltage and current. (4 Marks)

By thevenin

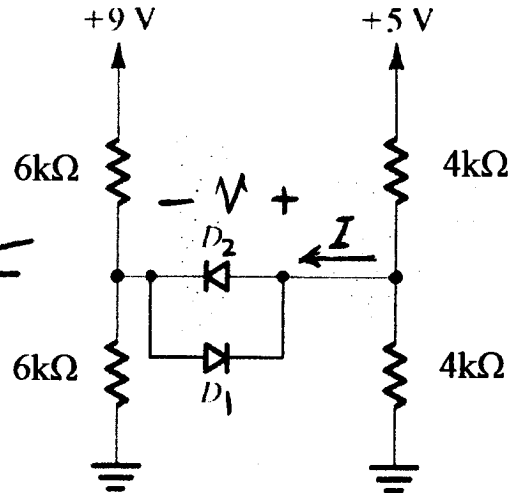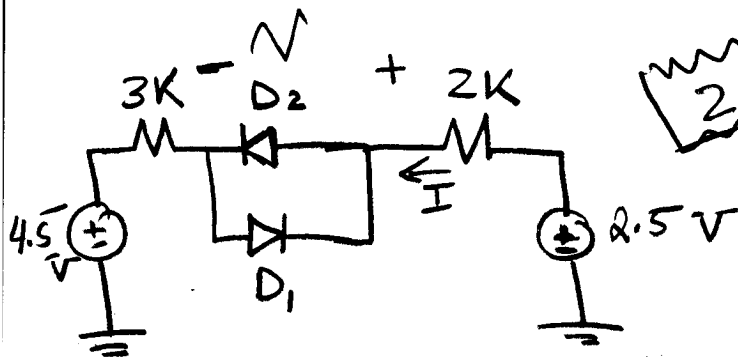


$\Rightarrow D_1$ on & D_2 off

By KVL:



$$I = \frac{2.5 + 0.7 - 4.5}{3k + 2k} = -0.26 \text{ mA}$$

$$V = -0.7$$

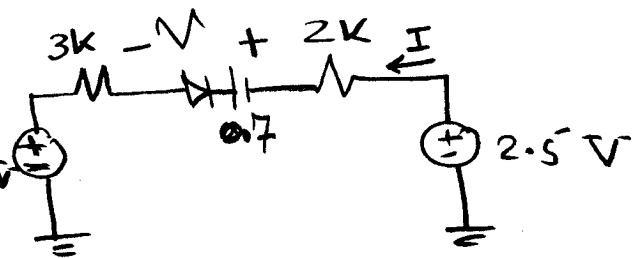

b). Design a limiter circuit using only one diode and one resistor to realize the transfer characteristics shown below, (assuming piecewise linear model $V_{D0}=0.7V$ & $r_d=20\Omega$). (3 Marks)

$$R = 200\Omega$$

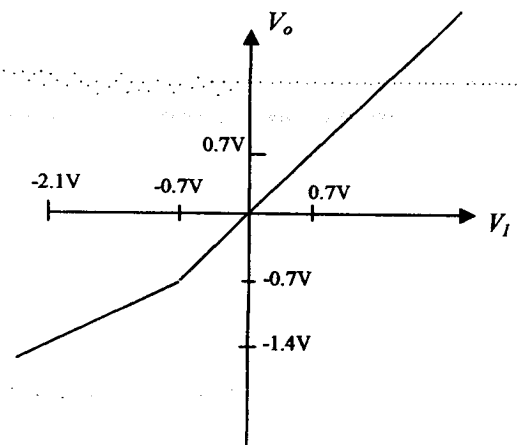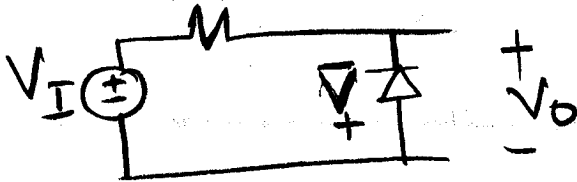

Question # 3: (5)

For the circuit shown below, the enhancement NMOS transistor parameters are: $V_t = 1.5V$, and $K_n'(W/L) = 2mA/V^2$.

Design R_S so that $V_S = 1V$;

Calculate drain current I_D , and voltage V_D .

Analysis 3.

$$I_D = \frac{1}{2} K_n' \frac{W}{L} (V_{GS} - V_t)^2$$

$$I_D = 1m (V_{GS} - 1.5)^2 \quad (1)$$

$$V_G = 9 \times \frac{3}{6+3} = 3V$$

$$V_{GS} = V_G - V_S = 3 - 1 = 2V$$


From (1) $I_D = 1m \times (2 - 1.5)^2$

$$= \underline{\underline{0.25mA}}$$

$$R_S = \frac{V_S}{I_D} = \frac{1}{0.25m} = \underline{\underline{4k\Omega}}$$

By KVL
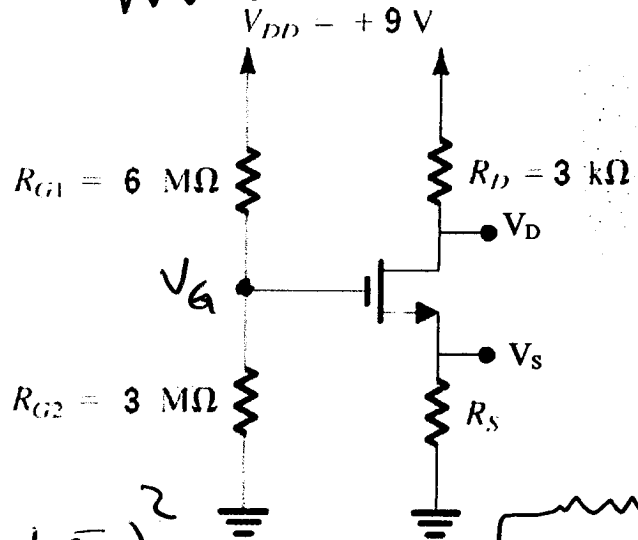
$$V_D = 9 - I_D R_D = 9 - 3k \times 0.25 = \underline{\underline{8.25V}}$$



0.75

0.5

0.75