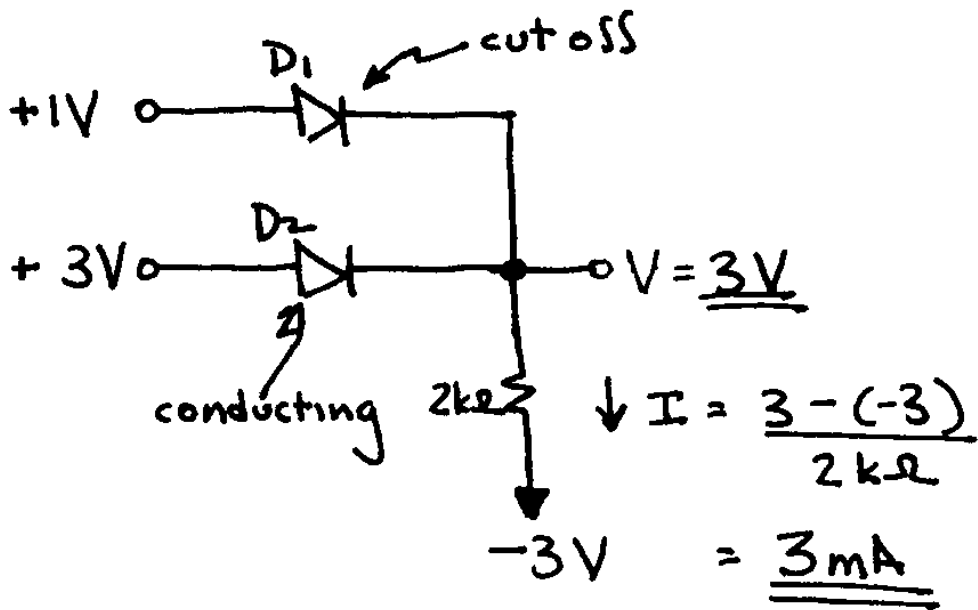



# HW1

3.3

(a)




(b)

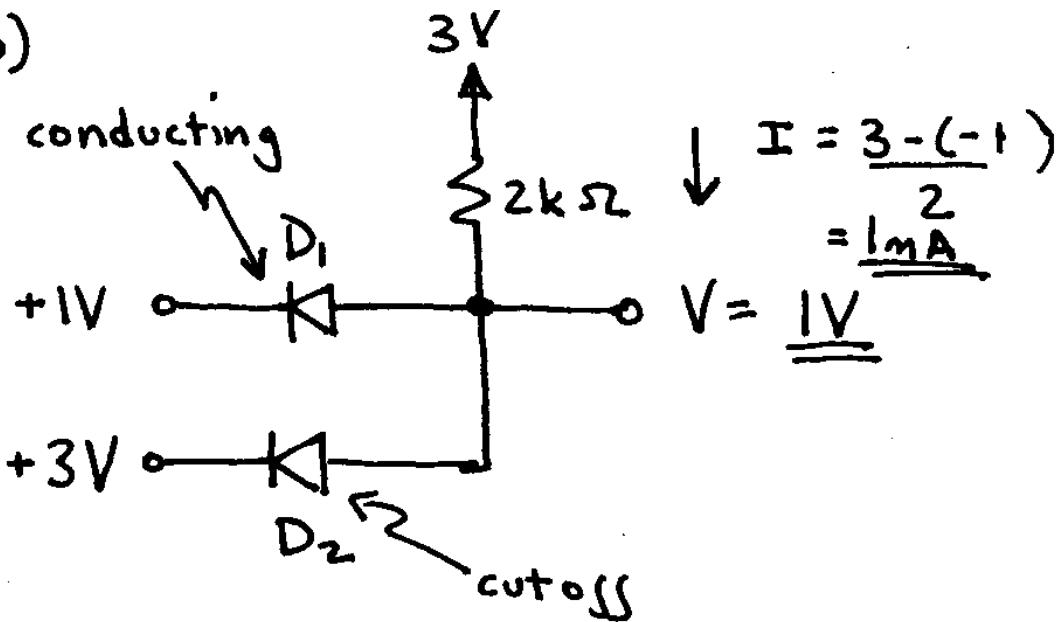

3.10

(a)

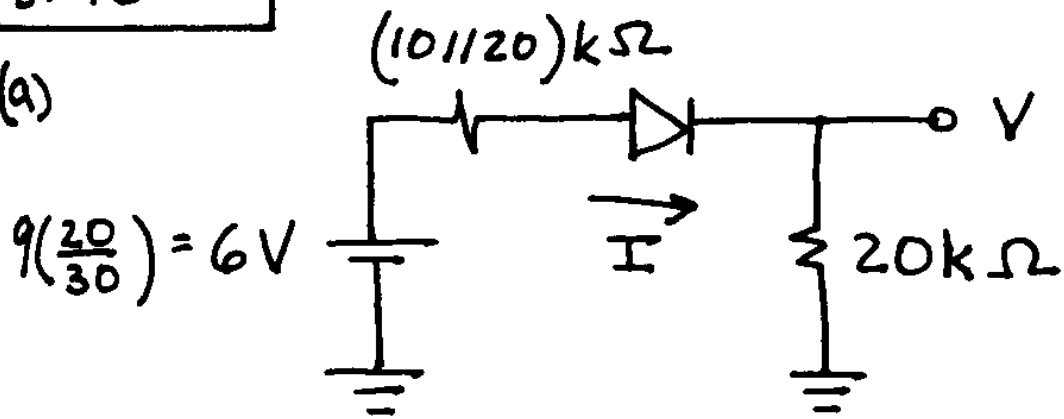


$$9\left(\frac{20}{30}\right) = 6V$$

$$I = \frac{6}{(10||20) + 20} = \underline{\underline{0.225mA}}$$

$$V = \frac{20}{(10||20) + 20} \times 6 = \underline{\underline{4.5V}}$$

(b)

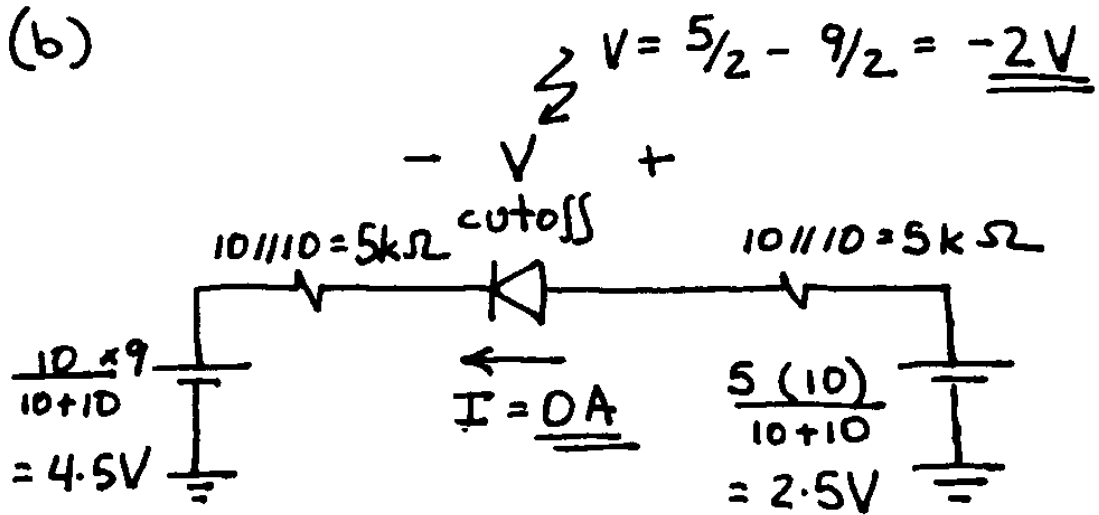


3.11

$$R \gg \frac{120\sqrt{2}}{50} \gg \underline{\underline{3.4\text{ k}\Omega}}$$

The largest reverse voltage appearing across the diode is equal to the peak input voltage

$$120\sqrt{2} = \underline{\underline{169.7\text{ V}}}$$

3.26

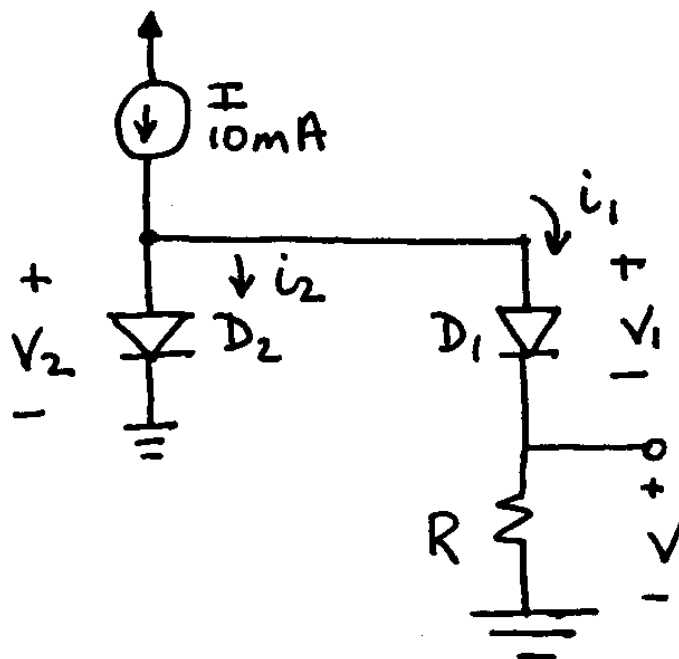

Given for each diode

$$i = I_s e^{V/nV_T} \Rightarrow 10 \times 10^{-3} = I_s e^{0.7/n \times 0.025} \quad \textcircled{1}$$

$$100 \times 10^{-3} = I_s e^{0.8/n \times 0.025} \quad \textcircled{2}$$

$$\textcircled{2}/\textcircled{1} \quad 10 = e^{0.1/n(0.025)}$$

$$n = 1.737$$

$$V = V_2 - V_1 = nV_T \ln(i_2/i_1) = 80 \text{ mV}$$

$$1.737 (25 \times 10^{-3}) \ln\left(\frac{0.01 - i_1}{i_1}\right) = 80$$

$$i_1 = 1.4 \text{ mA}$$

$$R = 80/i_1 = 80/1.4 = \underline{\underline{57.1 \Omega}}$$