


Q1 (35 points)

a) Assuming ideal Op-amp,

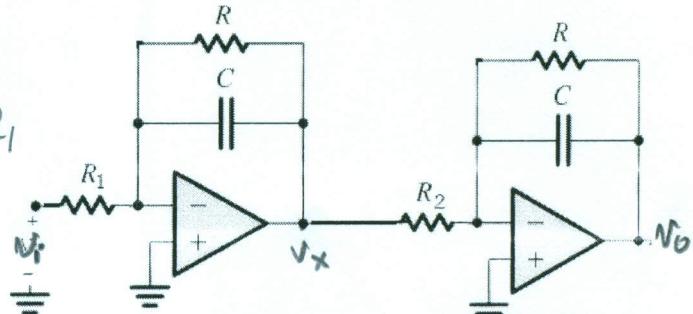1. Drive the transfer function V_o/V_i and identify the circuit function.
2. Select the resistors and the capacitors to provide a 3dB corner frequency = 10k rad/s and filter gain = 20 dB.

$$N_x = N_i \left(-\frac{R}{sCR_1 + R_1} \right) = -\frac{R}{sCR_1 + R_1}$$

$$\frac{N_o}{N_i} = \left(-\frac{R}{sCR_1 + R_1} \right) \left(-\frac{R}{sCR_2 + R_2} \right)$$



$$= \frac{R^2}{s^2 C^2 R^2 R_1 R_2 + 2sCR_1 R_2 + R_1 R_2} = \frac{\frac{1}{C^2 R_1 R_2}}{s^2 + 2s\frac{1}{CR} + \frac{1}{C^2 R^2}}$$
10

ω^{nd} order low pass filter - Active opamp-RC 5

$$2. \omega_0 = \frac{1}{CR} \Rightarrow 10K = \frac{1}{RC} \Rightarrow C = 0.1\mu F, R = 1k\Omega$$


$$\text{Gain} = 20 \text{dB} = 10 \log_{10} = \frac{R^2}{R_1 R_2} \Rightarrow R_1 R_2 = 10^5 \Omega \Rightarrow R_1 = 1k\Omega \quad \boxed{5} \quad R_2 = 100\Omega$$

b) Drive the transfer function V_o/V_i and identify the circuit function.

$$\frac{V_o}{N_i} = \frac{Z_P}{Z_P + R} = \frac{1}{1 + Y_P R}$$


$$= \frac{1}{1 + [sC + \frac{1}{sL}]R} = \frac{sL}{sL + s^2 CLR + R}$$
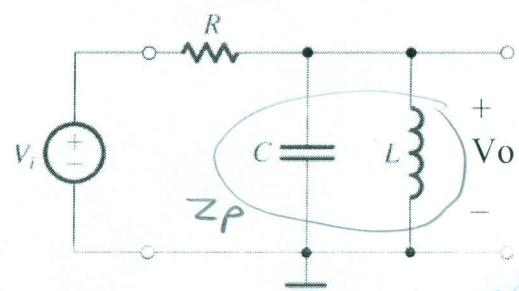
$$= \frac{\frac{1}{CR}}{s^2 + s\frac{1}{CR} + \frac{1}{CL}} \quad \boxed{10} \quad \omega^{nd} \text{ order LCR Band pass filter} \quad \boxed{5}$$



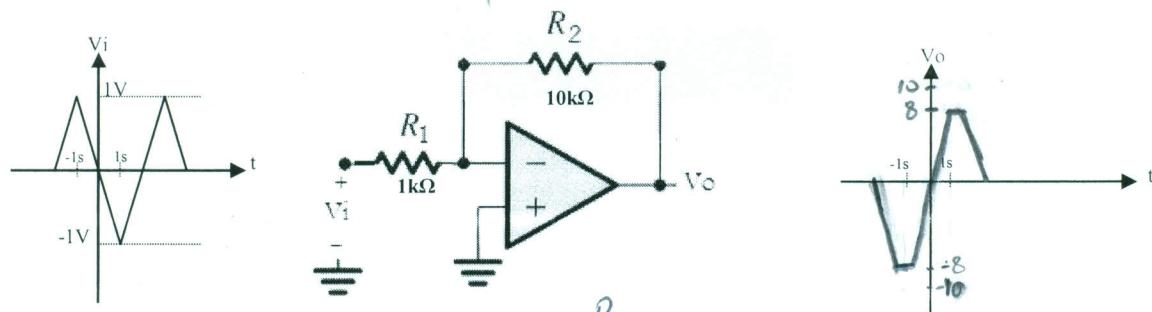Q2 (30 points)


* Consider the circuits shown below, Assuming ideal Op-amp with a saturation output voltage = $\pm 8V$, sketch the output voltages and clearly label the waveforms.



$$\text{Gain} = -\frac{R_2}{R_1} = -10$$


- a. Drive the relation between v_o and v_s for the circuit shown in figure (a), what is the function of this circuit? [7 Points]

$$v_o = -\frac{1}{RC} \int v_s dt$$
7

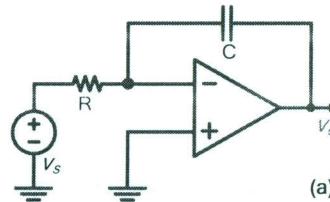

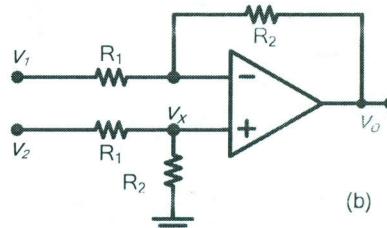- b. Determine v_o as a function of v_1 and v_2 for the circuit shown in figure (b), what is the function of this circuit? [7 Points]


$$v_o = \frac{R_2}{R_1 + R_2} (1 + \frac{R_2}{R_1}) v_2$$



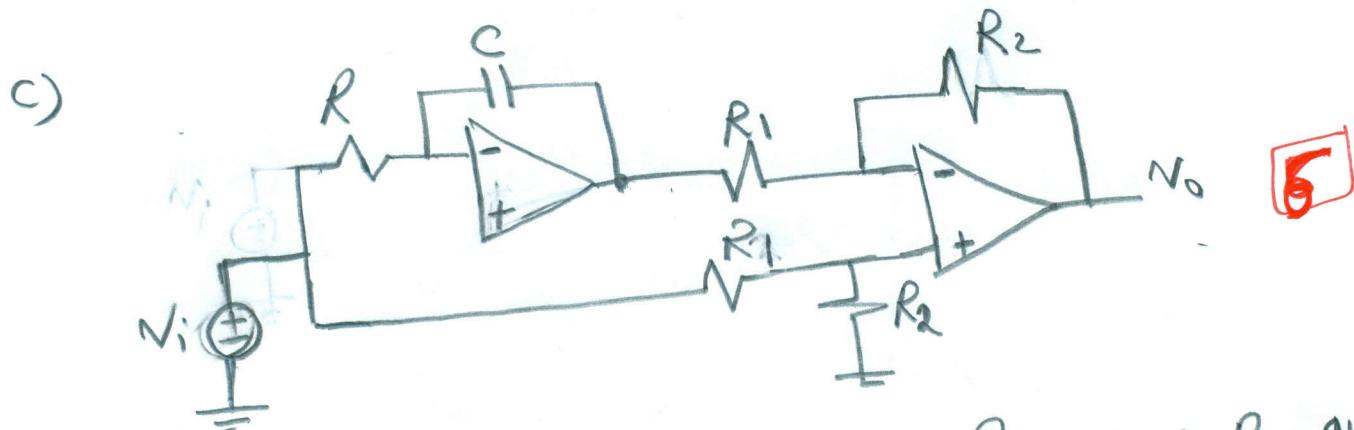- c. Using the circuits in parts (a) and (b); design a circuit to realize the following equation:

$$v_o = 2v_i + 6 \int v_i dt ; [7 \text{ Points}]$$

$$b) v_o = \frac{R_2}{R_1 + R_2} \left(1 + \frac{R_2}{R_1} \right) v_2 - \frac{R_2}{R_1} v_1 = \frac{R_2}{R_1} (v_2 - v_1) \quad \boxed{7}$$



$$v_o = \frac{1}{RC} \left(\frac{R_2}{R_1} \right) \int v_i dt + \frac{R_2}{R_1} v_i \Rightarrow \frac{R_2}{R_1} = 2 \Rightarrow R_2 = 2k \quad R_1 = 1k$$

$$\frac{1}{RC} = 3 \Rightarrow C = 1\mu F, R = 333k \quad \boxed{4}$$

Q3 (35 points)

Consider the circuits shown below and answer the following questions:



- Identify the feedback topology for each circuit. [6 points]
- Drive an expression for the feedback ratio β for each circuit [12 points]
- for figure (a) only Drive an expression for the network A [11 points]
- for figure (a) only Find the closed-loop gain = v_o/v_{sig} [6 points]

i) a) series-series 6

b) series-shunt


ii)

a)

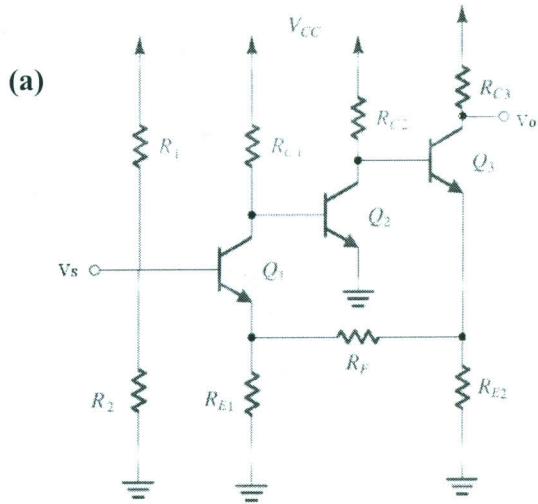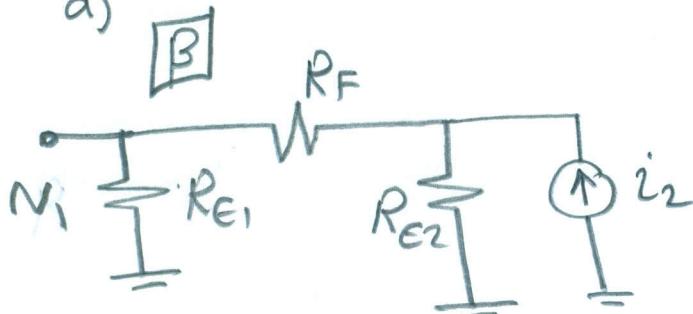


$$\beta = \frac{N_1}{Z_2} = \frac{R_{E2} R_{E1}}{R_{E2} + R_F + R_{E1}} \quad \boxed{6}$$

b)

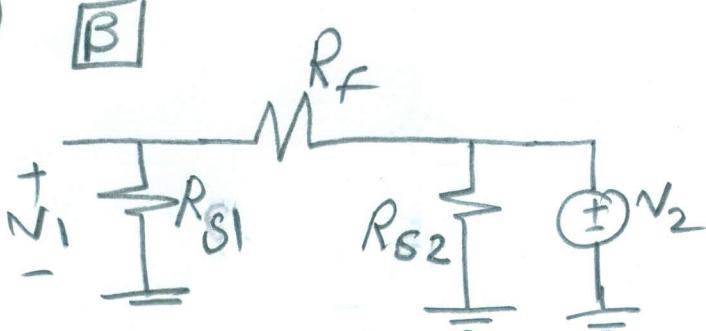


$$\beta = \frac{N_1}{N_2} = \frac{R_{S1}}{R_{S1} + R_F} \quad \boxed{6}$$

iii)

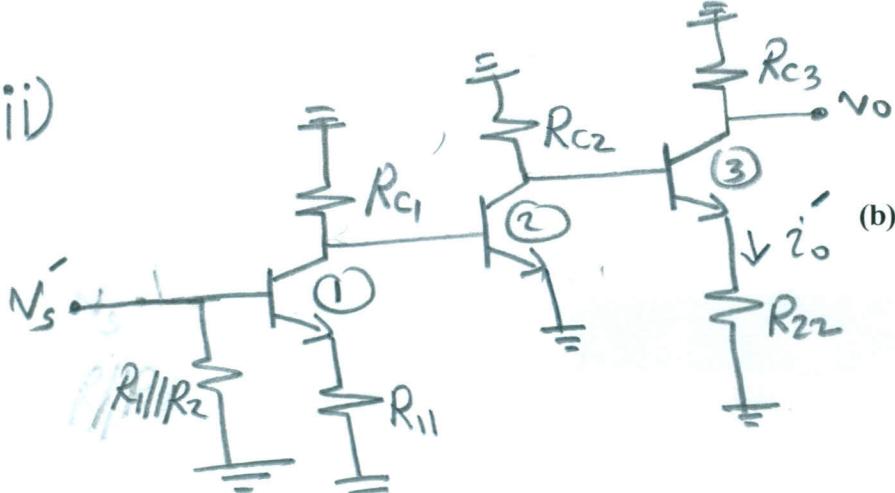

$$R_{11} = R_{E1} / (R_F + R_{E2})$$

$$R_{22} = R_{E2} / (R_F + R_{E1})$$

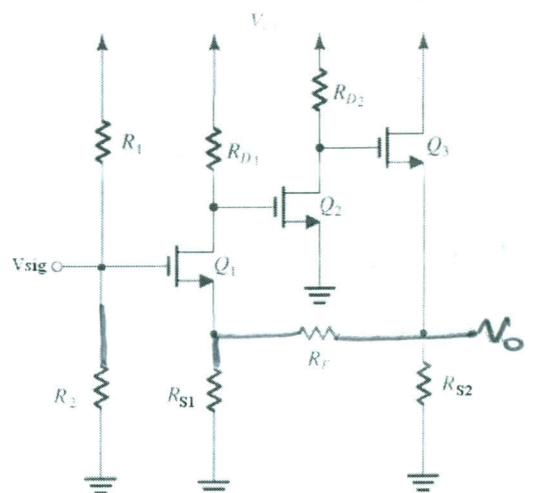

iv) $A_{CL} = \frac{V_o}{V_s} = \frac{A}{1+A\beta}$ 6

$$A = \frac{i'_o}{V_s} = \frac{R_{c1} / (r_{\pi 2})}{R_{11} + r_{e1}} \left(- \frac{R_{c2} / ((\beta+1)(r_{e3} + R_{22}))}{r_{e2}} \right) \frac{1}{r_{e3} + R_{22}}$$
11