

voltage drop across all parallel-connected resistors is the same.

$$\begin{aligned} \text{[a]} \quad R_{\text{eq}} &= \{[(5 \text{ k} + 7 \text{ k}) \parallel 6 \text{ k}] + 3 \text{ k} + 8 \text{ k}\} \parallel 10 \text{ k} = [(12 \text{ k} \parallel 6 \text{ k}) + 11 \text{ k}] \parallel 10 \text{ k} \\ &= (4 \text{ k} + 11 \text{ k}) \parallel 10 \text{ k} = 15 \text{ k} \parallel 10 \text{ k} = 6 \text{ k}\Omega \end{aligned}$$

$$\text{[b]} \quad R_{\text{eq}} = [240 \parallel (180 + 300)] + 140 + 200 = (240 \parallel 480) + 340 = 160 + 340 = 500 \Omega$$

$$\text{[c]} \quad R_{\text{eq}} = (40 + 50 + 60) \parallel (30 + 45) = 150 \parallel 75 = 50 \Omega$$

P 3.6 Always work from the side of the circuit furthest from the source. Remember that the current in all series-connected circuits is the same, and that the voltage drop across all parallel-connected resistors is the same.

$$\text{[a]} \quad R_{\text{eq}} = 12 \parallel 20 \parallel [18 + (28 \parallel 21)] = 12 \parallel 20 \parallel (18 + 12) = 12 \parallel 20 \parallel 30 = 6 \Omega$$

$$\text{[b]} \quad R_{\text{eq}} = 4 + (9 \parallel 18) + [5 \parallel 30 \parallel (20 + 40)] = 4 + 6 + (5 \parallel 30 \parallel 60) = 4 + 6 + 4 = 14 \Omega$$

$$\text{[c]} \quad R_{\text{eq}} = (100 \text{ k} \parallel 300 \text{ k}) + (75 \text{ k} \parallel 50 \text{ k} \parallel 150 \text{ k}) + 25 \text{ k} = 75 \text{ k} + 25 \text{ k} + 25 \text{ k} = 125 \text{ k}\Omega$$

P 3.7 [a] $12 \Omega \parallel 24 \Omega = 8 \Omega$ Therefore, $R_{\text{ab}} = 8 + 2 + 6 = 16 \Omega$

$$\text{[b]} \quad \frac{1}{R_{\text{eq}}} = \frac{1}{24 \text{ k}\Omega} + \frac{1}{30 \text{ k}\Omega} + \frac{1}{20 \text{ k}\Omega} = \frac{15}{120 \text{ k}\Omega} = \frac{1}{8 \text{ k}\Omega}$$

$$R_{\text{eq}} = 8 \text{ k}\Omega; \quad R_{\text{eq}} + 7 = 15 \text{ k}\Omega$$

$$\frac{1}{R_{\text{ab}}} = \frac{1}{15 \text{ k}\Omega} + \frac{1}{30 \text{ k}\Omega} + \frac{1}{15 \text{ k}\Omega} = \frac{5}{30 \text{ k}\Omega} = \frac{1}{6 \text{ k}\Omega}$$

$$R_{\text{ab}} = 6 \text{ k}\Omega$$

P 3.8 [a] $60 \parallel 20 = 1200/80 = 15 \Omega$ $12 \parallel 24 = 288/36 = 8 \Omega$

$$15 + 8 + 7 = 30 \Omega$$

$$30 \parallel 120 = 3600/150 = 24 \Omega$$

$$R_{\text{ab}} = 15 + 24 + 25 = 64 \Omega$$

$$\text{[b]} \quad 35 + 40 = 75 \Omega \quad 75 \parallel 50 = 3750/125 = 30 \Omega$$

$$30 + 20 = 50 \Omega \quad 50 \parallel 75 = 3750/125 = 30 \Omega$$

$$30 + 10 = 40 \Omega \quad 40 \parallel 60 + 9 \parallel 18 = 24 + 6 = 30 \Omega$$

$$30 \parallel 30 = 15 \Omega \quad R_{\text{ab}} = 10 + 15 + 5 = 30 \Omega$$


$$\text{[c]} \quad 50 + 30 = 80 \Omega \quad 80 \parallel 20 = 16 \Omega$$

$$16 + 14 = 30 \Omega \quad 30 + 24 = 54 \Omega$$

$$54 \parallel 27 = 18 \Omega \quad 18 + 12 = 30 \Omega$$

$$30 \parallel 30 = 15 \Omega \quad R_{\text{ab}} = 3 + 15 + 2 = 20 \Omega$$

P 3.17 [a]

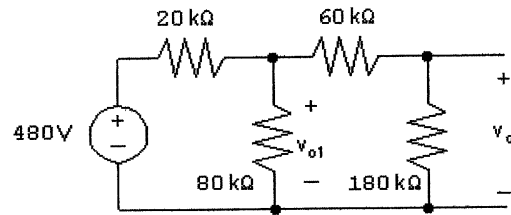


$$180 \text{ k}\Omega + 60 \text{ k}\Omega = 240 \text{ k}\Omega$$

$$80 \text{ k}\Omega \parallel 240 \text{ k}\Omega = 60 \text{ k}\Omega$$

$$v_{o1} = \frac{60,000}{(20,000 + 60,000)}(480) = 360 \text{ V}$$

$$v_o = \frac{180,000}{(240,000)}(v_{o1}) = 270 \text{ V}$$

[b]

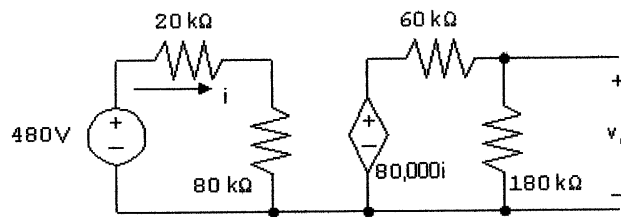

$$i = \frac{480}{100,000} = 4.8 \text{ mA}$$

$$80,000i = 384 \text{ V}$$

$$v_o = \frac{180,000}{240,000}(384) = 288 \text{ V}$$

[c] It removes loading effect of second voltage divider on the first voltage divider. Observe that the open circuit voltage of the first divider is

$$v'_{o1} = \frac{80,000}{(100,000)}(480) = 384 \text{ V}$$

Now note this is the input voltage to the second voltage divider when the current controlled voltage source is used.

$$\text{P 3.18 } \frac{(24)^2}{R_1 + R_2 + R_3} = 80, \quad \text{Therefore, } R_1 + R_2 + R_3 = 7.2 \Omega$$

$$\frac{(R_1 + R_2)24}{(R_1 + R_2 + R_3)} = 12$$

$$\text{Therefore, } 2(R_1 + R_2) = R_1 + R_2 + R_3$$

Thus, $R_1 + R_2 = R_3$; $2R_3 = 7.2$; $R_3 = 3.6 \Omega$

$$\frac{R_2(24)}{R_1 + R_2 + R_3} = 5$$

$$4.8R_2 = R_1 + R_2 + 3.6 = 7.2$$

Thus, $R_2 = 1.5 \Omega$; $R_1 = 7.2 - R_2 - R_3 = 2.1 \Omega$

P 3.19 [a] At no load: $v_o = kv_s = \frac{R_2}{R_1 + R_2}v_s$.

At full load: $v_o = \alpha v_s = \frac{R_e}{R_1 + R_e}v_s$, where $R_e = \frac{R_o R_2}{R_o + R_2}$

Therefore $k = \frac{R_2}{R_1 + R_2}$ and $R_1 = \frac{(1-k)}{k}R_2$

$\alpha = \frac{R_e}{R_1 + R_e}$ and $R_1 = \frac{(1-\alpha)}{\alpha}R_e$

Thus $\left(\frac{1-\alpha}{\alpha}\right) \left[\frac{R_2 R_o}{R_o + R_2}\right] = \frac{(1-k)}{k}R_2$


Solving for R_2 yields $R_2 = \frac{(k-\alpha)}{\alpha(1-k)}R_o$

Also, $R_1 = \frac{(1-k)}{k}R_2 \therefore R_1 = \frac{(k-\alpha)}{\alpha k}R_o$

[b] $R_1 = \left(\frac{0.05}{0.68}\right)R_o = 2.5 \text{ k}\Omega$

$R_2 = \left(\frac{0.05}{0.12}\right)R_o = 14.167 \text{ k}\Omega$

[c]

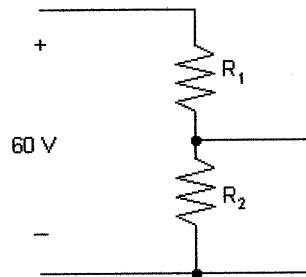


Maximum dissipation in R_2 occurs at no load, therefore,

$$P_{R_2(\max)} = \frac{[(60)(0.85)]^2}{14,167} = 183.6 \text{ mW}$$

Maximum dissipation in R_1 occurs at full load.
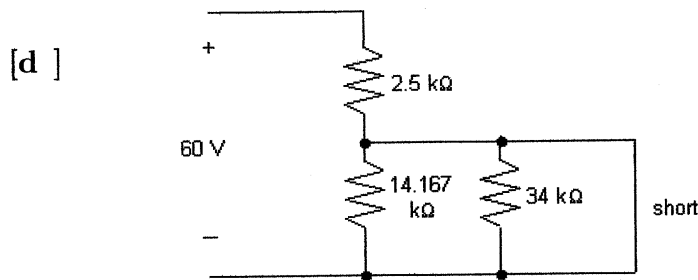
$$P_{R_1(\max)} = \frac{[60 - 0.80(60)]^2}{2500} = 57.60 \text{ mW}$$



$$P_{R_1} = \frac{(60)^2}{2500} = 1.44 \text{ W} = 1440 \text{ mW}$$

$$P_{R_2} = \frac{(0)^2}{14,167} = 0 \text{ W}$$

P 3.20 [a] Let v_o be the voltage across the parallel branches, positive at the upper terminal, then

$$i_g = v_o G_1 + v_o G_2 + \cdots + v_o G_N = v_o (G_1 + G_2 + \cdots + G_N)$$

It follows that
$$v_o = \frac{i_g}{(G_1 + G_2 + \cdots + G_N)}$$

The current in the k^{th} branch is $i_k = v_o G_k$; Thus,

$$i_k = \frac{i_g G_k}{[G_1 + G_2 + \cdots + G_N]}$$

[b]
$$i_{6.25} = \frac{1142(0.16)}{[4 + 0.4 + 1 + 0.16 + 0.1 + 0.05]} = 32 \text{ mA}$$

P 3.21 Begin by using the relationships among the branch currents to express all branch currents in terms of i_4 :

$$i_1 = 4i_2 = 4(8i_3) = 5(32i_4)$$

$$i_2 = 8i_3 = 5(8i_4)$$

$$i_3 = 5i_4$$

Now use KCL at the top node to relate the branch currents to the current supplied by the source.

$$i_1 + i_2 + i_3 + i_4 = 5 \text{ mA}$$

Express the branch currents in terms of i_4 and solve for i_4 :

$$5 \text{ mA} = 160i_4 + 40i_4 + 5i_4 + i_4 = 206i_4 \quad \text{so} \quad i_4 = \frac{0.005}{206} \text{ A}$$

Since the resistors are in parallel, the same voltage, 1 V appears across each of them. We know the current and the voltage for R_4 so we can use Ohm's law to calculate R_4 :

$$R_4 = \frac{v_g}{i_4} = \frac{1 \text{ V}}{(5/206) \text{ mA}} = 41.2 \text{ k}\Omega$$

Calculate i_3 from i_4 and use Ohm's law as above to find R_3 :

$$i_3 = 5i_4 = \frac{25}{206} \text{ A} \quad \therefore R_3 = \frac{v_g}{i_3} = \frac{1 \text{ V}}{(25/206) \text{ mA}} = 8240 \Omega$$


Calculate i_2 from i_4 and use Ohm's law as above to find R_2 :

$$i_2 = 40i_4 = \frac{0.2}{206} \text{ A} \quad \therefore R_2 = \frac{v_g}{i_2} = \frac{1 \text{ V}}{(200/206) \text{ mA}} = 1030 \Omega$$

Calculate i_1 from i_4 and use Ohm's law as above to find R_1 :

$$i_1 = 160i_4 = \frac{0.8}{206} \text{ A} \quad \therefore R_1 = \frac{v_g}{i_1} = \frac{1 \text{ V}}{(800/206) \text{ mA}} = 257.5 \Omega$$

The resulting circuit is shown below:

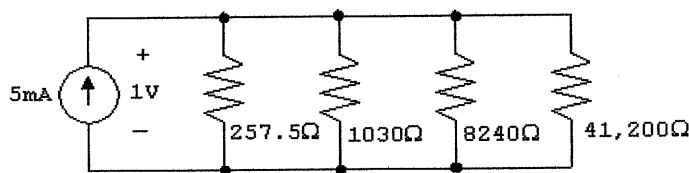

- P 3.22 [a] The equivalent resistance to the right of the 10 kΩ resistor is $3 \text{ k} + 8 \text{ k} + [6 \text{ k} \parallel (5 \text{ k} + 7 \text{ k})] = 15 \text{ k}\Omega$. Therefore,

$$i_{10\text{k}} = \frac{15 \text{ k} \parallel 10 \text{ k}}{10 \text{ k}} (0.002) = \frac{6 \text{ k}}{10 \text{ k}} (0.002) = 1.2 \text{ mA}$$

- [b] The voltage drop across the 10 kΩ resistor can be found using Ohm's law:

$$v_{10\text{k}} = (10,000)i_{10\text{k}} = (10,000)(0.0012) = 12 \text{ V}$$

- [c] The voltage $v_{10\text{k}}$ drops across the 3 kΩ resistor, the 8 kΩ resistor and the equivalent resistance of the 6 kΩ and the parallel branch containing the 5 kΩ and 7 kΩ resistors. Thus, using voltage division,

$$v_{6\text{k}} = \frac{6 \text{ k} \parallel (5 \text{ k} + 7 \text{ k})}{3 \text{ k} + 8 \text{ k} + [6 \text{ k} \parallel (5 \text{ k} + 7 \text{ k})]} (12) = \frac{4}{15} (12) = 3.2 \text{ V}$$

- [d] The voltage $v_{6\text{k}}$ drops across the branch containing the 5 kΩ and 7 kΩ resistors. Thus, using voltage division,

$$v_{5\text{k}} = \frac{5 \text{ k}}{5 \text{ k} + 7 \text{ k}} (3.2) = 1.33 \text{ V}$$