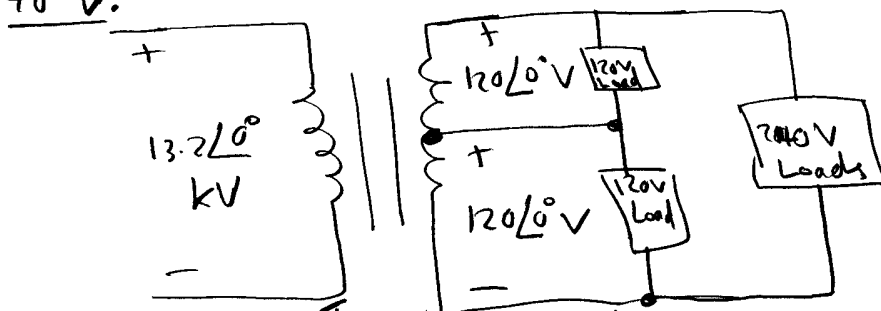


Textbook Sections 6.4 and 6.5  
and 9.10 and 9.11

What is a Transformer?

- A transformer transfer electrical energy between two circuits which are physically separated. For example, in Power distribution, step up and step down transformers are very common. The step down transformer are used to reduce the utility distribution voltage from 13.2 kv to 240 V.




Step down transformer

- In addition, transformers are used in circuits and electronic designs to match impedances and eliminate dc signals from portions of the systems.

How does it work?

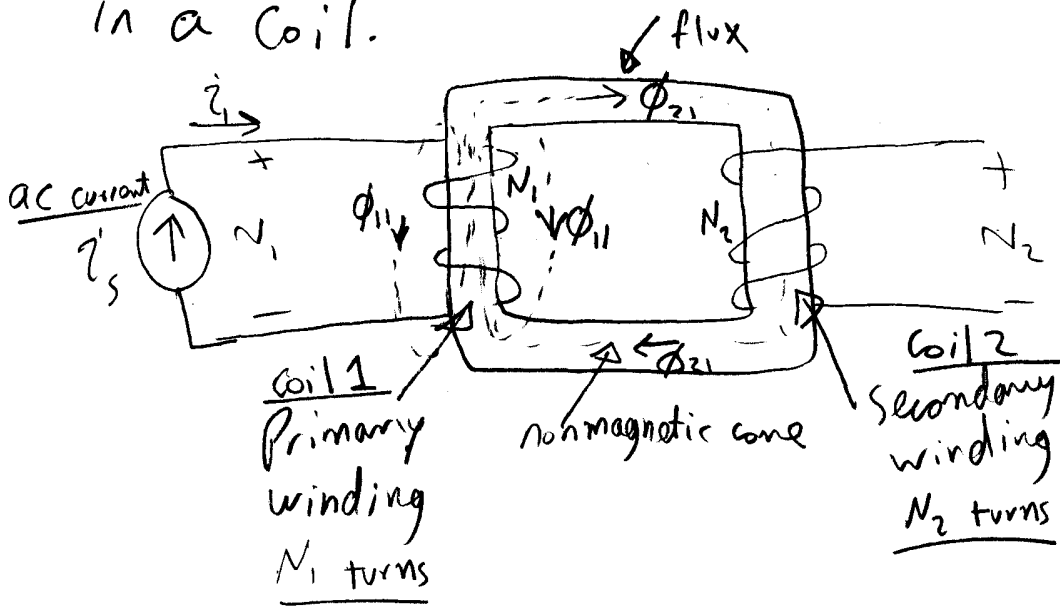It is based on the electromagnetic theory of mutual inductance where a time varying magnetic field will introduce a time varying current in a coil.



What is happening?

- Coil 1 is energized by a time-varying current source that establishes the current  $i_1$  in the  $N_1$  turns.
- Coil 2 is not energized and is open.
- The coils are wound on nonmagnetic core.
- The time-varying current in Coil 1 introduces a flux  $\Phi_1$ .
- Flux  $\Phi_1 = \Phi_{11} + \Phi_{21}$ 
  - $\Phi_{11}$  flux linking Coil 1
  - $\Phi_{21}$  flux linking Coil 2 caused by Coil 1

## Definitions:

- Flux ~~Em~~ strength of magnetic field (webers) (wb)

$$\Phi = \frac{NI}{\mathcal{P}}$$

Permeance  
"Quantity that describes the magnetic properties of a space."

# of Turns

Current

- Flux Linkage  $\lambda = N\Phi$

- So,  $\Phi_1 = \mathcal{P}_1 N_1 i_1$ ;  $\Phi_{11} = \mathcal{P}_{11} N_1 i_1$ ;  $\Phi_{21} = \mathcal{P}_{21} N_1 i_1$

- Note that  $\mathcal{P}_1 = \mathcal{P}_{11} + \mathcal{P}_{21}$

- By using Faraday's Law,

$$v_1 = \frac{d\lambda_1}{dt} = N_1 \frac{d(\Phi_{11} + \Phi_{21})}{dt} = N_1^2 (\mathcal{P}_{11} + \mathcal{P}_{21}) \frac{di_1}{dt} = N_1^2 \mathcal{P}_1 \frac{di_1}{dt}$$

$$\text{Also, } v_2 = \frac{d\lambda_2}{dt} = \frac{d(N_2 \Phi_{21})}{dt} = N_2 \frac{d(\mathcal{P}_{21} N_1 i_1)}{dt} = \underbrace{N_2 N_1 \mathcal{P}_{21}}_{\text{Mutual inductance between coil 1 and 2}} \frac{di_1}{dt}$$

self-inductance of coil 1

Define: Mutual inductance  $M_{21} = N_2 N_1 \mathcal{P}_{21}$   
Similarly  $M_{12} = N_1 N_2 \mathcal{P}_{12}$


For numerical...

What is the relation between Mutual inductance and Self inductance?

$$M = k \sqrt{L_1 L_2} \quad ; \quad 0 \leq k \leq 1$$

↙  
Coefficient  
of Coupling

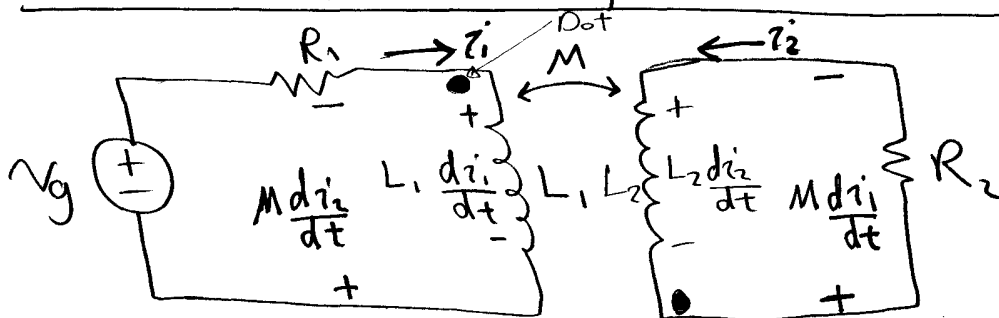Induced Voltage Polarity and Dot Convention:





There are Four voltages

- $L_1 \frac{di_1}{dt}$  } Self inductance
- $L_2 \frac{di_2}{dt}$  }
- $M \frac{di_1}{dt}$  } Mutual Inductance
- $M \frac{di_2}{dt}$  }

Dot Convention:

— When the reference direction of the current enters the dotted terminal of a coil, the reference polarity of the voltage that it induces in the other coil is positive at its dotted terminals.

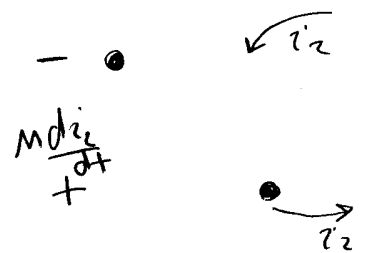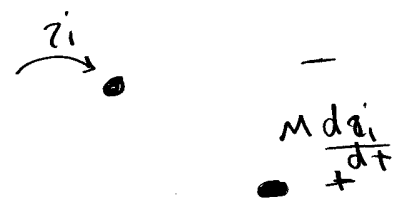— When the reference direction for a current leaves the dotted terminal of a coil, the reference polarity of the voltage that it induces in the other coil is negative



# Mutual Inductance and transformers Ch. 6


P. 5

Thus, the sum of voltages at each loop are:

$$-v_g + i_1 R_1 + L_1 \frac{di_1}{dt} - M \frac{di_2}{dt} = 0$$

$$i_2 R_2 + L_2 \frac{di_2}{dt} - M \frac{di_1}{dt} = 0$$


Energy Calculations?

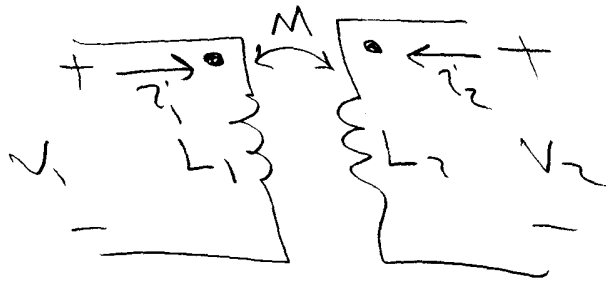

what is the total Energy stored in the magnetically coupled coils?

$$w(t) = \underbrace{\frac{1}{2} L_1 i_1^2}_{\text{coil 1}} + \underbrace{\frac{1}{2} L_2 i_2^2}_{\text{coil 2}} \pm \underbrace{M i_1 i_2}_{\text{Mutual Energy}}$$


How to decide on the sign, "+" or "-" ?

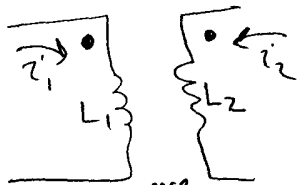

$i_1$  and  $i_2$  are same  
Both enter the  
Dot.

$\Rightarrow$  "+"
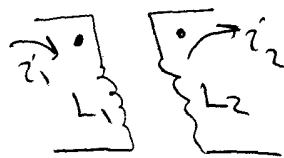
$$\Rightarrow w(t) = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 + M i_1 i_2$$



$i_1$  and  $i_2$  are opposite  
one current enters while  
the other leaves.

$\Rightarrow$  "-"

$$\Rightarrow w(t) = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 - M i_1 i_2$$