

EE 213 ELECTRIC CIRCUITS II

Resonance Circuits

Dr. Hakan Köroğlu



Recap: Sinusoidal Steady-State Analysis

- A sinusoidal voltage source is identified as:

$$v_s(t) = V_m \cos(\omega t + \phi)$$

where ω is the frequency, ϕ is the phase angle and V_m is the maximum amplitude.

- A sinusoidal current source is identified similarly as:

$$i_s(t) = I_m \cos(\omega t + \phi)$$

- The response of a **linear circuit** in steady-state in response to a sinusoidal source is also sinusoidal:
 - ❑ with the **same frequency** and
 - ❑ with possibly different amplitude and phase.

Recap: Phasor, Impedance & Admittance

- For linear circuits with sinusoidal sources, **phasor** transform leads to algebraic **frequency domain** analysis:

$$\mathcal{V} = \mathcal{V}_m e^{j\phi} = \mathcal{P}\{\mathcal{V}_m \cos(\omega t + \phi)\}$$

- The relation between voltage over an element and current through the element is expressed in the frequency domain as:

$$\mathcal{V} = ZI$$

- Z is referred to as the **impedance** and its reciprocal is called the **admittance**:

$$\mathcal{V} = I/Y$$

3

Recap: Impedance and Related Values

Element	Impedance (Z)	Reactance	Admittance (Y)	Susceptance
Resistor	R (resistance)	–	$1/R$ (conductance)	–
Inductor	$j\omega L$	ωL	$1/(j\omega L)$	$-1/(\omega L)$
Capacitor	$1/(j\omega C)$	$-1/(\omega C)$	$j\omega C$	ωC


- All circuit analysis techniques for resistive circuits are extended to sinusoidal steady-state analysis by using the frequency-dependent impedance expressions.

4

Frequency Response

- The impedance of an arbitrary RLC circuit is thus **frequency-dependent**.
- This dependence can be depicted graphically by magnitude and phase angle versus frequency, which constitute the frequency response of the impedance.
- Parallel RC impedance:

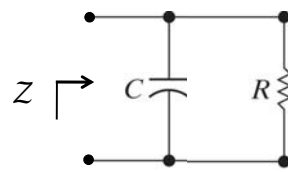
$$Z = \frac{\mathcal{R} \frac{1}{j\omega C}}{\mathcal{R} + \frac{1}{j\omega C}} = \frac{\mathcal{R}}{1 + j\omega RC}$$



5


Frequency Response: Parallel RC

$$|Z(j\omega)| = \frac{\mathcal{R}}{\sqrt{1 + (\omega RC)^2}}$$

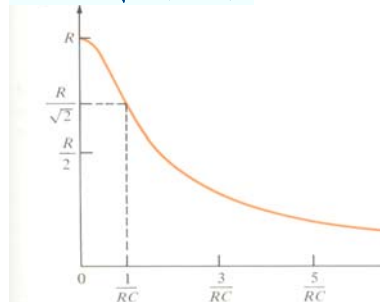

Amplitude response

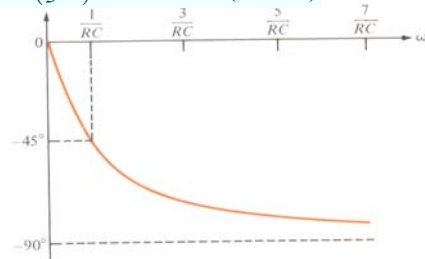
$$\angle Z(j\omega) = -\tan^{-1}(\omega RC)$$



Phase response

6

Half-Power or Cut-Off Frequency

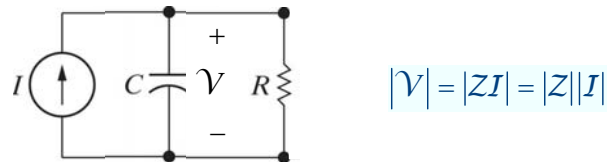

- Cut-off frequencies are those at which the average power is half of its maximum value.
- Maximum average power for the above circuit:


$$|Z| \text{ is max at } \omega = 0 \Rightarrow P_{max} = \frac{1}{2} \frac{|\mathcal{V}_0|^2}{\mathcal{R}} = \frac{1}{2} \frac{|Z(j0)|^2 |I|^2}{\mathcal{R}} = \frac{1}{2} \mathcal{R} |I|^2$$

- The power is halved at $\omega = \omega_c = 1/RC$:

$$P_c = \frac{1}{2} \frac{|\mathcal{V}_c|^2}{\mathcal{R}} = \frac{1}{2} \frac{|Z(j\omega_c)|^2 |I|^2}{\mathcal{R}} = \frac{1}{4} \mathcal{R} |I|^2 = \frac{1}{2} P_0$$

7

Resonance: Parallel RLC

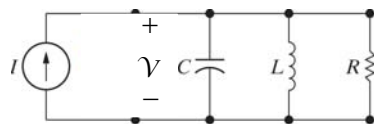

- A circuit is said to be **at resonance** if the imaginary part of its impedance or admittance is zero.
- For the parallel RLC circuit:


$$Y = \frac{I}{V} = \frac{1}{\mathcal{R}} + j \left(\omega C - \frac{1}{\omega L} \right)$$

- The imaginary part (susceptance) is zero at:

$$\omega_r = \frac{1}{\sqrt{LC}} \quad : \text{ Resonance frequency}$$

8

Example: Resonance Frequency

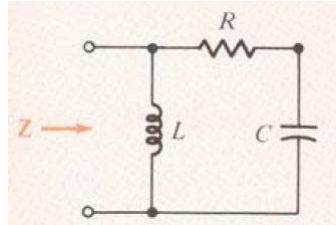

$$Z = \frac{V}{I} = \frac{j\omega L \left(R + \frac{1}{j\omega C} \right)}{j\omega L + R + \frac{1}{j\omega C}}$$


$$= \frac{j\omega L (1 + j\omega RC)}{1 - \omega^2 LC + j\omega RC}$$

- The resonance frequency for this circuit is:

$$\omega_r = \frac{1}{\sqrt{LC - R^2C^2}}$$

9

Parallel RLC: Magnitude Response

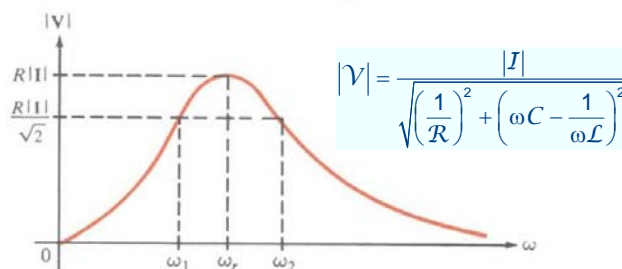

- **Bandwidth** is defined in terms of the half-power frequencies as:

$$BW \square \omega_2 - \omega_1$$

- The response gets sharper as the bandwidth gets smaller.

10

Quality Factor

- The **quality factor** is defined at the resonance as:

$$Q = 2\pi \left(\frac{\text{Maximum energy stored}}{\text{Total energy lost in a period}} \right)$$

- Since energy is stored by the capacitors/inductors and it is dissipated by the resistors, we have:

$$Q = \frac{2\pi \max_t [w_C(t) + w_L(t)]}{P_R T}$$

$$w_C(t) = \frac{1}{2} C v_C^2(t)$$

$$w_L(t) = \frac{1}{2} \mathcal{L} i_L^2(t)$$

$$P_R : \text{Resistive power}$$

11

Quality Factor: Parallel RLC

- Consider a source with current $i(t) = I \cos(\omega_r t)$

- At resonance, we have $Y = 1/R$. Hence:

$$v_C(t) = R i(t) = R I \cos(\omega_r t) \Rightarrow w_C(t) = \frac{1}{2} C R^2 I^2 \cos^2(\omega_r t)$$

- The inductor current is obtained via phasor analysis:

$$I_L = \frac{R I}{j\omega_r \mathcal{L}} = \frac{R I}{\omega_r \mathcal{L}} e^{-j90^\circ} \Rightarrow i_L(t) = \frac{R I}{\omega_r \mathcal{L}} \sin(\omega_r t)$$

- The energy stored in the inductor is then given by:

$$w_L(t) = \frac{1}{2} \frac{R^2 I^2}{\omega_r^2 \mathcal{L}} \sin^2(\omega_r t) = \frac{1}{2} C R^2 I^2 \sin^2(\omega_r t)$$

12

Quality Factor: Parallel RLC (ctd.)

- The total energy stored is thus a constant:

$$w_c(t) + w_L(t) = \frac{1}{2} CR^2 I^2$$

- The total energy dissipated by the resistor over a period is found as:

$$P_R = \frac{1}{2} I^2 R \Rightarrow P_R T = P_R \frac{2\pi}{\omega_r} = \frac{\pi I^2 R}{\omega_r}$$

- Hence the quality factor of a parallel RLC circuit is:

$$Q = \frac{\pi CR^2 I^2}{\frac{\pi I^2 R}{\omega_r}} = RC\omega_r = \frac{R}{L\omega_r} = R\sqrt{\frac{C}{L}}$$

13

Bandwidth for Parallel RLC

- Since $Q/R = \omega_r C = 1/\omega_r L$, the admittance satisfies:

$$Y = \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right) = \frac{1}{R} \left(1 + jQ \left(\frac{\omega}{\omega_r} - \frac{\omega_r}{\omega}\right)\right)$$

- At the half-power frequencies, we have:

$$|V| = \frac{R|I|}{\sqrt{2}} = \frac{|I|}{|Y|} \Rightarrow |Y| = \frac{\sqrt{2}}{R} \Rightarrow Q \left(\frac{\omega}{\omega_r} - \frac{\omega_r}{\omega}\right) = \pm 1$$

- We can obtain ω_1 , ω_2 and the bandwidth as:

$$\omega_{1,2} = \omega_r \left(\sqrt{1 + \left(\frac{1}{2Q}\right)^2} \pm \frac{1}{2Q} \right) \Rightarrow BW \square \omega_2 - \omega_1 = \frac{\omega_r}{Q} = \frac{1}{RC}$$

- The ratio $Q = \frac{\omega_r}{BW}$ is also called the **selectivity**.

14

Resonance: Series RLC



- Resonance frequency: $\omega_r = \frac{1}{\sqrt{LC}}$
- Quality factor: $Q = \frac{1}{R} \sqrt{\frac{L}{C}}$
- Half-power frequencies: $\omega_{1,2} = \omega_r \left(\sqrt{1 + \left(\frac{1}{2Q}\right)^2} \pm \frac{1}{2Q} \right)$
- Bandwidth: $BW = \frac{\omega_r}{Q} = \frac{R}{L}$


15

Resonance: Parallel and Series RLC

	Parallel RLC	Series RLC
Resonance frequency (ω_r)	$\frac{1}{\sqrt{LC}}$	$\frac{1}{\sqrt{LC}}$
Quality factor (Q)	$= \omega_r RC = R \sqrt{\frac{C}{L}}$	$= \omega_r \frac{L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$
Half-power frequencies	$\omega_r \left(\sqrt{1 + \left(\frac{1}{2Q}\right)^2} \pm \frac{1}{2Q} \right)$	$\omega_r \left(\sqrt{1 + \left(\frac{1}{2Q}\right)^2} \pm \frac{1}{2Q} \right)$
Bandwidth (BW)	$= \frac{\omega_r}{Q} = \frac{1}{RC}$	$= \frac{\omega_r}{Q} = \frac{R}{L}$

16

Series-Parallel RLC Circuit

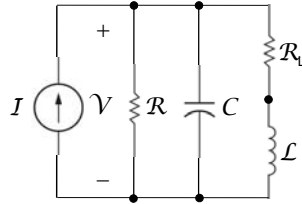

$$Y = \frac{I}{V} = \frac{1}{R} + j\omega C + \frac{1}{R_L + j\omega L} = \frac{1}{R} + \frac{R_L}{R_L^2 + \omega^2 L^2} + j\left(\omega C - \frac{\omega L}{R_L^2 + \omega^2 L^2}\right)$$

- Resonance frequency: $\omega_r = \sqrt{\frac{1}{LC} - \frac{R_L^2}{L^2}}$, for $R_L \leq \sqrt{\frac{L}{C}}$
- No resonance for larger R_L values !
- For the parallel (series) RLC the magnitude of the admittance (impedance) is minimum. Neither is the case for the series-parallel RLC circuit.

17

Series Inductive or Capacitive Reactance

$$Ie^{j\omega t} \rightarrow \begin{array}{c} R_s \\ \text{---} \bullet \text{---} \\ jX_s = j\omega L \end{array}$$

$$Ie^{j\omega t} \rightarrow \begin{array}{c} R_s \\ \text{---} \bullet \text{---} \\ jX_s = -j/(\omega C) \end{array}$$

- The quality factor is defined in a similar way. Consider the case of inductive reactance.
- The maximum total energy stored:

$$w(t) = \frac{1}{2} Li^2(t) = \frac{1}{2} LI^2 \cos^2(\omega t) \Rightarrow w_{max} = \frac{1}{2} LI^2 = \frac{X_s}{2\omega} I^2$$


- The energy dissipated per period:

$$P_s T = \frac{1}{2} I^2 R_s \left(\frac{2\pi}{\omega}\right) = \frac{\pi I^2 R_s X_s}{\omega}$$


- Quality factor: $Q = \frac{2\pi I^2 X_s / (2\omega)}{\pi I^2 R_s / \omega} = \frac{X_s}{R_s}$

18

Series versus Parallel Reactance

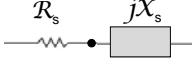- For a general **series** reactance: 

$$Q = \frac{|X_s|}{R_s}$$

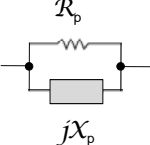- For a general **parallel** reactance: 


$$Q = \frac{R_p}{|X_p|}$$

- **Remark:** Note that the quality factor is frequency-dependent.

19

High-Q Resonant Circuit
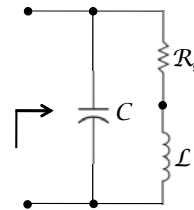
$$Y = j\omega C + \frac{1}{R_s + j\omega L}$$



- Suppose that the series reactance has a large (≥ 20) Q-factor (called a high-Q coil).

$$\frac{X_L}{R_s} \gg 1 \Rightarrow \frac{\omega L}{R_s} \gg 1 \Rightarrow \omega L \gg R_s$$


- The admittance can then be approximated by:

$$Y \approx j\omega C + \frac{1}{j\omega L}$$

- The resonance frequency is approximated as: $\omega_r \approx \frac{1}{\sqrt{LC}}$

20

Equivalent High-Q Resonant Circuit

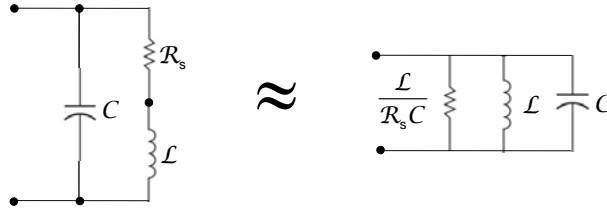

➤ Based on the impedance approximation


$$Z = \frac{(R_s + j\omega L) \frac{1}{j\omega C}}{R_s + j\omega L + \frac{1}{j\omega C}} \approx \frac{L/C}{R_s + j\omega L + \frac{1}{j\omega C}}$$

the admittance can be approximated as

$$Y \approx \frac{R_s C}{L} + j\omega C + \frac{1}{j\omega L}$$

21

Magnitude Scaling of a Circuit

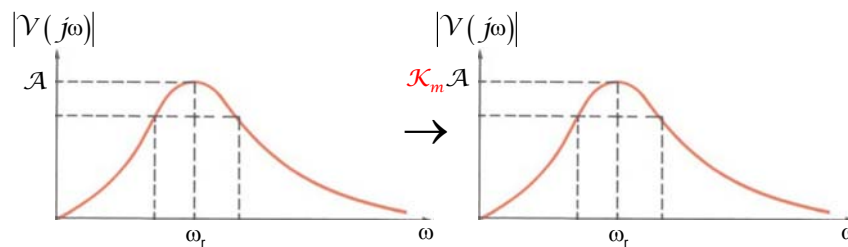


➤ **Magnitude (impedance) scaling:**

$$R \rightarrow K_m R \quad L \rightarrow K_m L \quad C \rightarrow \frac{C}{K_m}$$

Dependent sources with a unit of Ω (Siemens) are multiplied (divided) by K_m .

22

Frequency Scaling of a Circuit

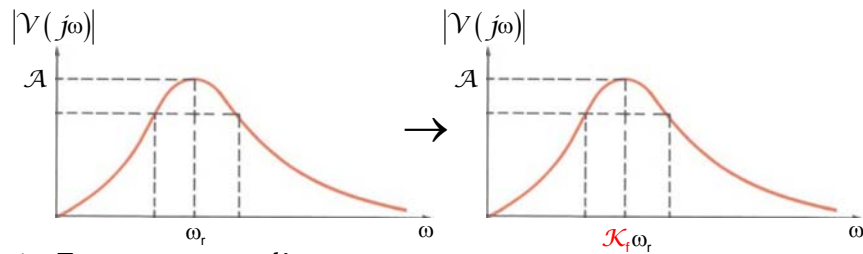

➤ **Frequency scaling:**

$$\mathcal{R} \rightarrow \mathcal{R} \quad \mathcal{L} \rightarrow \frac{\mathcal{L}}{K_f} \quad C \rightarrow \frac{C}{K_f}$$

- Magnitude scaling does not change the bandwidth.
- Frequency scaling scales the bandwidth too:

$$BW \rightarrow K_f BW$$