

EE 407  
Microwave Engineering


*Lecture 5 to 7*

Impedance Transformers  
and Smith chart

Dr. Sheikh Sharif Iqbal

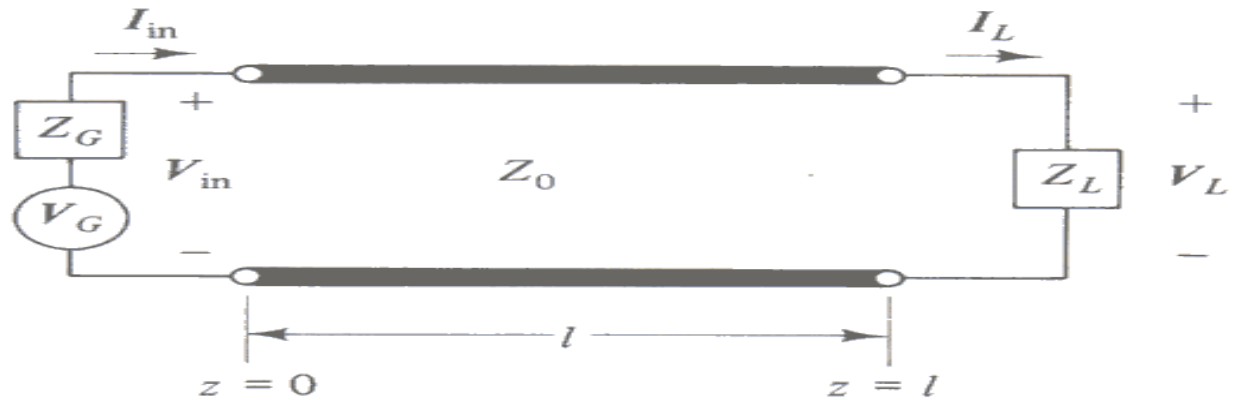**References: Text and reference books**

- Elec. length,  $\theta = \beta l$   
 where,  
 $l$  = physical length  
 $\beta$  = phase constant



## Impedance Transformers: (for $\alpha=0$ and $Z_0$ & $Z_L$ are real no's)

- For T.L. with  $l=\lambda/4$  has:  $\beta l = (2\pi/\lambda)(\lambda/2) = \pi/2$  &  $\tan \pi/2 = \infty$




$$Z_{in} = Z_0 \frac{Z_L + Z_0 \tan \beta l}{Z_0 + Z_L \tan \beta l} = Z_0 \frac{\frac{Z_L}{\tan \beta l} + Z_0}{\frac{Z_0}{\tan \beta l} + Z_L} = \frac{Z_0^2}{Z_L} \quad \text{Thus, } \begin{cases} Z_0 = \sqrt{Z_{in} Z_L} \\ \overline{Z_{in}} = \frac{1}{Z_L} \end{cases}$$

This transformer is used impedance inversion and matching purposes.


- For T.L. with  $l=\lambda/2$ :  $\beta l = (2\pi/\lambda)(\lambda/2) = \pi$ ;  $Z_{in} = Z_0 \frac{Z_L + Z_0 \tan \beta l}{Z_0 + Z_L \tan \beta l} = Z_L$

This transformer is used impedance point extension and matching.

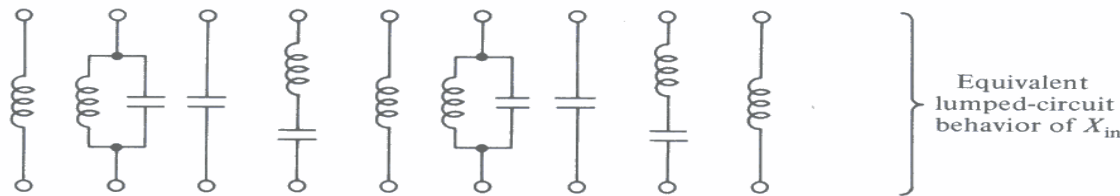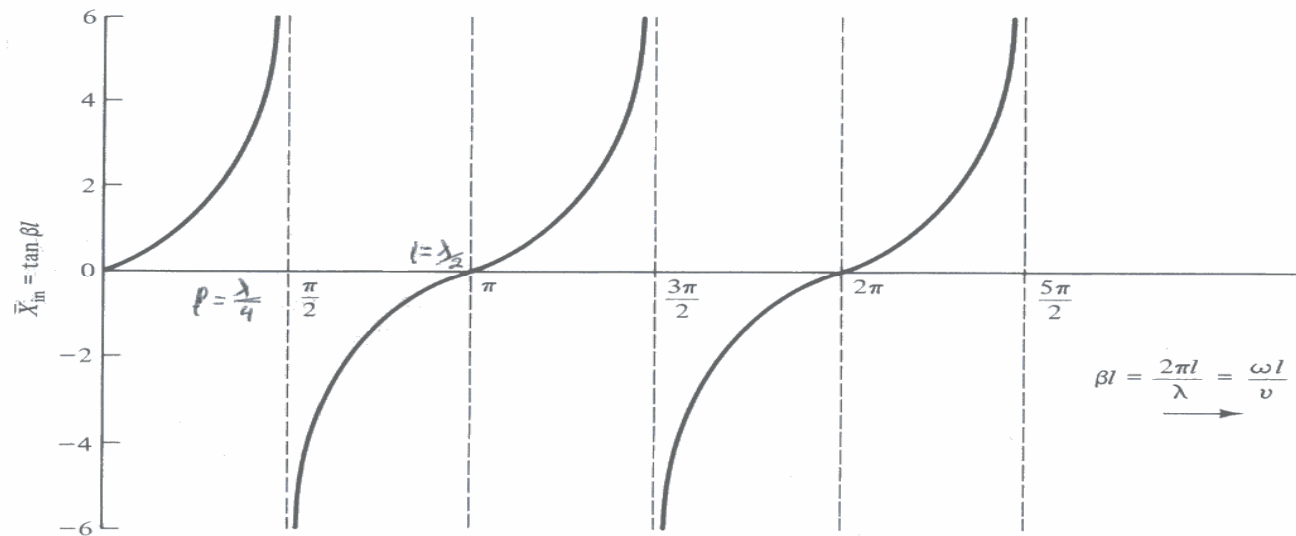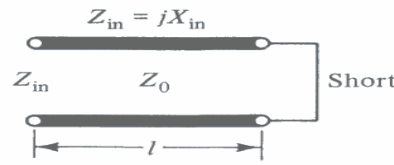- For T.L. with  $Z_L=0$  or S/C; we know that  $Z_{in} = jZ_0 \tan \beta l$  or  $\underline{X}_{in} = \tan \beta l$ ;
- Here if  $0 < l < \lambda/4$ ,  $\underline{X}_{in} \Rightarrow$  '+' and Input impedance ( $Z_{in}$ ) is Inductive
- But if  $\lambda/4 < l < \lambda/2$ ,  $\underline{X}_{in} \Rightarrow$  '-' and Input impedance ( $Z_{in}$ ) is Capacitive



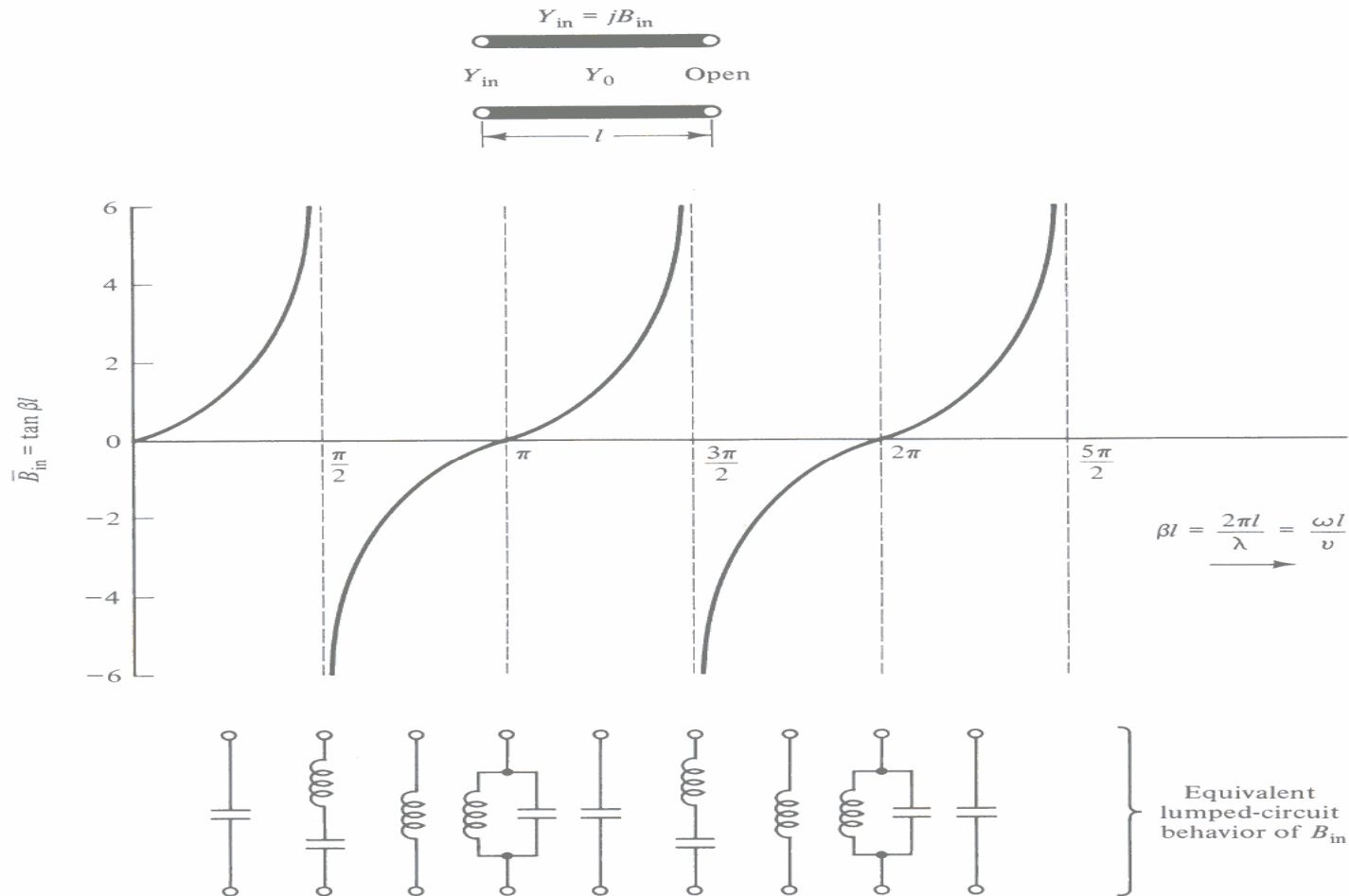- T.L. with  $Z_L = \infty$  or  $Y_L = 0$ ; we know that  $Y_{in} = jY_0 \tan \beta l$  or  $B_{in} = \tan \beta l$ ;
- Here if  $0 < l < \lambda/4$ ,  $B_{in} \Rightarrow$  '+' and Input impedance ( $Z_{in}$ ) is Capacitive
- But if  $\lambda/4 < l < \lambda/2$ ,  $B_{in} \Rightarrow$  '-' and Input impedance ( $Z_{in}$ ) is Inductive



- These O/C or S/C lines can be used as STUBS for matching TL's

# Smith Chart and its Applications: *(Invented by P.Smith in 1939)*

- ‘ $\Gamma$ ’ to ‘Z or Y’ converter; Simplifies analysis of complex TL or LE prob

$$\Gamma = \frac{Z - Z_0}{Z + Z_0} = \frac{\overline{Z_N} - 1}{\overline{Z_N} + 1} \quad \text{or} \quad U + jV = \frac{r + jx - 1}{r + jx + 1} \quad \text{as, } \begin{cases} \Gamma = U + jV \\ \overline{Z_N} = r + jx \end{cases}$$

$$U = \frac{r^2 - 1 + x^2}{(r + 1)^2 + x^2} \quad \text{and} \quad V = \frac{2x}{(r + 1)^2 + x^2}$$

- eq.1:eliminating  $x$ ;  $\left(U - \frac{r}{r + 1}\right)^2 + V^2 = \left(\frac{1}{r + 1}\right)^2$ 

$\begin{matrix} \nearrow \text{center} \\ \searrow \text{radius} \end{matrix}$

 $(U_0, V_0) = \left(\frac{r}{r + 1}, 0\right)$   
 $R = \left(\frac{1}{r + 1}\right)$

- eq.2:eliminating  $r$ ;  $(U - 1)^2 + \left(V - \frac{1}{x}\right)^2 = \left(\frac{1}{x}\right)^2 \rightarrow (U'_0, V'_0) = \left(1, \frac{1}{x}\right)$ ;  $R' = \left(\frac{1}{|x|}\right)$

- Eq.1  $\Rightarrow$  Resistance circles


{concentric at  $(U_0, V_0)$  & radius= $R$ }

(Note:  $\uparrow$  ‘r’  $\Leftrightarrow$   $\downarrow$  ‘circle size’)


- Eq.2  $\Rightarrow$  Reactance circles

{concentric at  $(U'_0, V'_0)$  & radius= $R'$ }

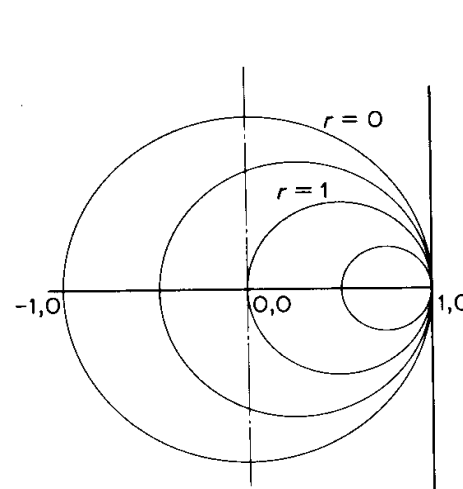(Note:  $\uparrow$  ‘x’  $\Leftrightarrow$   $\downarrow$  ‘circle size’)




RESISTANCE CIRCLES

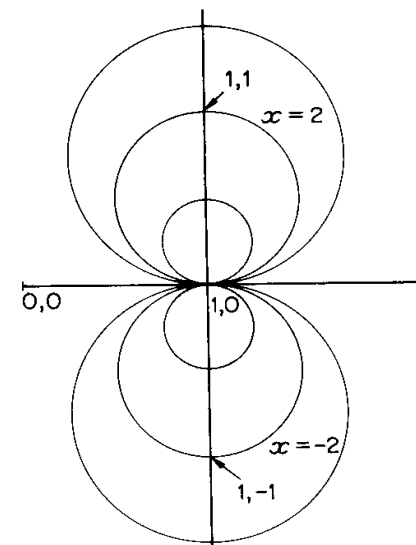

REACTANCE CIRCLES

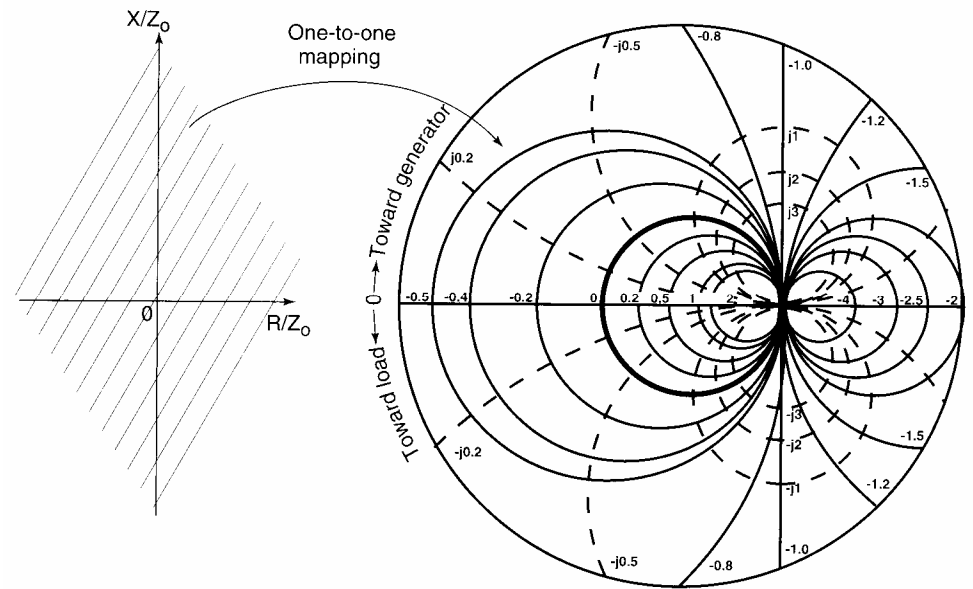
## Compressed Smith Chart :

- Plotting two families of circles for all values for  $(r,x)$  creates the entire smithchart: “Compressed”
- Applies to active & passive ckts
- Impractical and seldom used




## Standard Smith Chart :

- If two families of circles are plotted only for  $r \geq 0$ : “Standard”
- If ‘ $x \geq 0$ ’  $\Rightarrow$  Positive reactance
- If ‘ $x \leq 0$ ’  $\Rightarrow$  Negative reactance
- Heavily used for Passive ckts.
- Ref. Corff. Plane with ‘ $|\Gamma| \leq 1$ ’

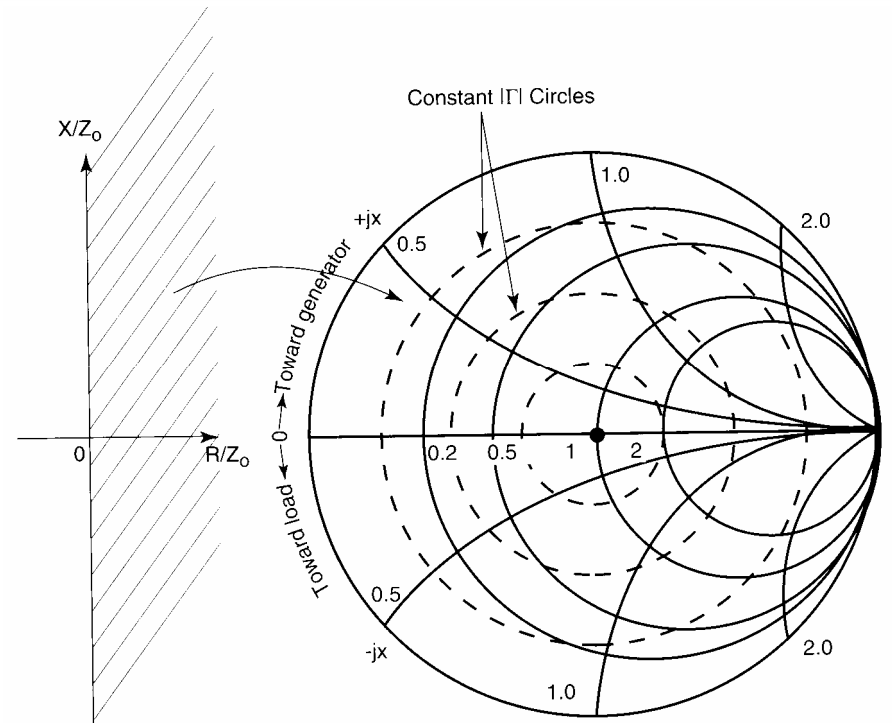


## Determine VSWR from known $Z_L$ :

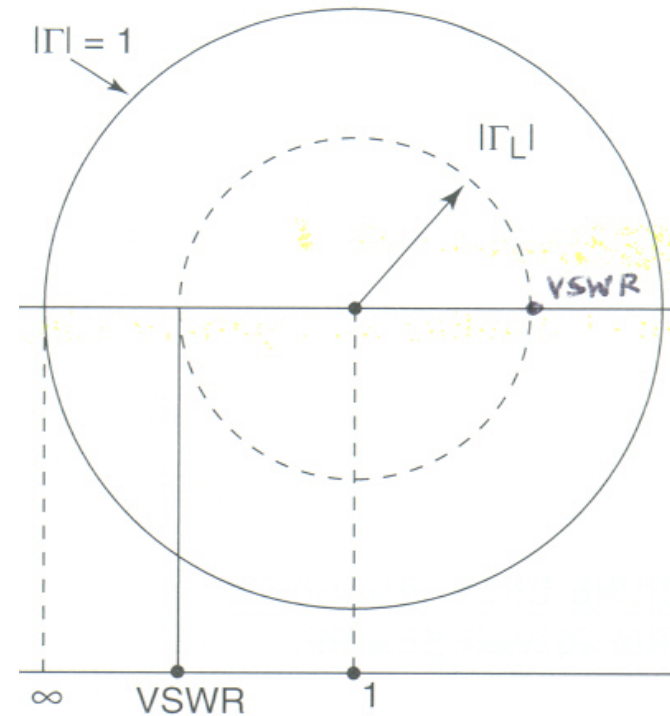1. Plot the normalized impedance  $(Z_L)_N$
2. Draw constant VSWR circle through  $(Z_L)_N$ 
  - From the intersection of circle and left-hand horizontal axis, drop a line on the bottom scale to read VSWR value
  - Or use intersection of the circle &  $\theta=0$  axis




## Determine $Y_N$ from known $Z_N$ : (vice versa)

1. Plot the normalized impedance  $[(Z)_N = Z/Z_0]$  on the standard Smith chart.
  2. Draw constant VSWR circle through  $(Z)_N$
  3. Draw a line from  $(Z)_N$  via the center of the of constant VSWR circle
  4.  $(Y)_N$  is the intersection of the line and circle
- \* Prove this using relation between  $(Z)_N$  &  $|\Gamma_N|$

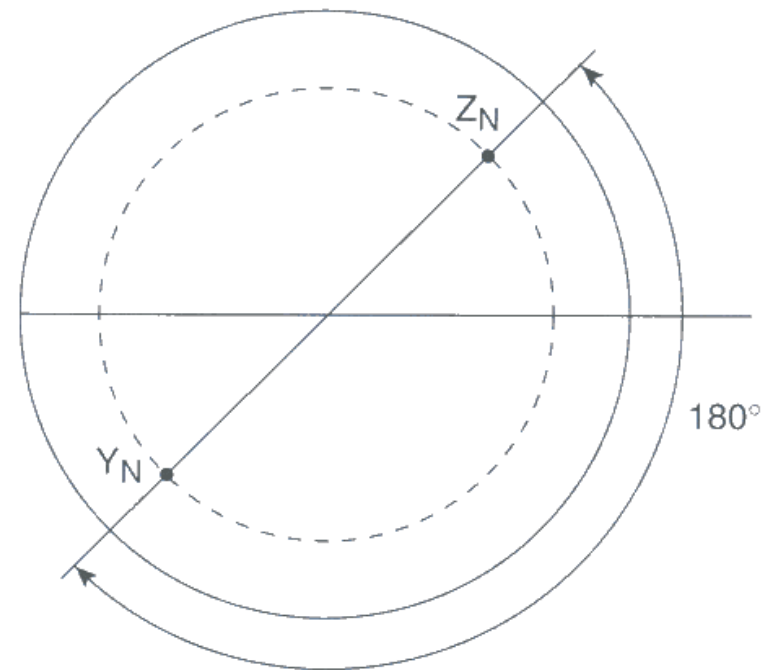


Determine  $Z_{IN}$  from known  $Z_L$ : (or vice versa)

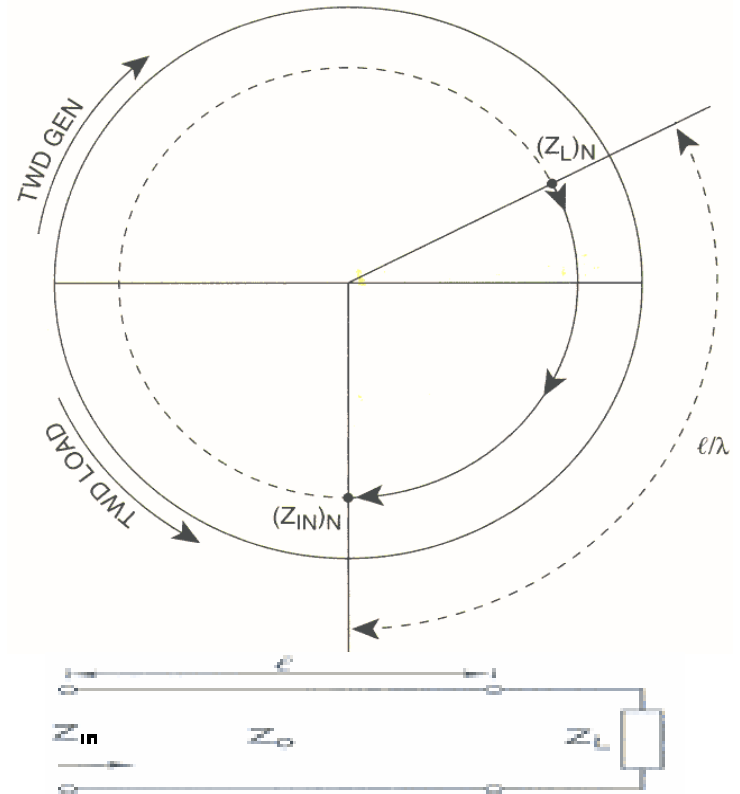1. Plot the normalized load impedance  $[(Z_L)_N = Z_L/Z_0]$  on the standard Smith chart.
2. Draw constant  $VSWR$  circle through  $(Z_L)_N$
3. From  $(Z_L)_N$ , move to a distance “ $l/\lambda$ ” ‘toward generator’ on constant  $VSWR$  circle
4. Read the normalized input impedance value  $[(Z_{IN})_N = Z_{IN}/Z_0]$  from the smith chart.



Determine  $Z_{IN}$  from known  $\Gamma$ : (for  $|\Gamma_{IN}| \leq 1$ )

1. For any point of TL. plot  $\Gamma_{IN} = |\Gamma_{IN}| e^{j\theta}$ ,
  - Use the bottom scale to plot  $|\Gamma_{IN}|$  value
  - Use circular scale to pot the angle ‘ $\theta$ ’.
2. Read the normalized input impedance value  $(Z_{IN})_N$  from the smith chart.

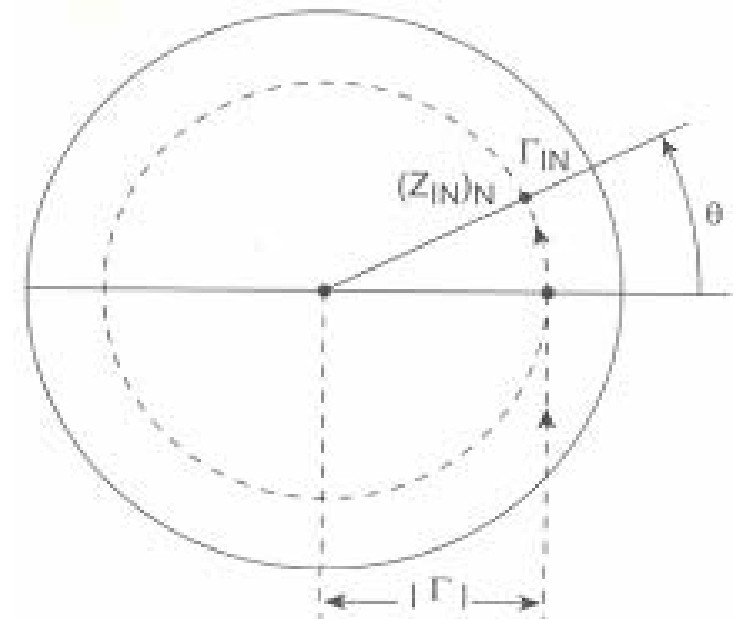

\* Conversely find ‘ $\Gamma$ ’ from known ‘ $Z_{IN}$ ’



## Examples of how to use the smith chart: (assume $Z_0=50 \Omega$ )

### **To plot the known impedance of the load:** (say, $Z_0= 50 \Omega$ , $Z_L= 50+j100 \Omega$ )

1. Normalizing the load impedance yields  $(Z_L)_N = 1+j2.0 \Omega$ .
2. Set chart with the central diameter horizontal & point zero on the left. Start from 'r = 0' on the central diameter & move to point 'r= 1.0' on the right.
3. Follow (r= 1.0) resistance circle upward and locate its intersection with reactance circle 'j2.0'. Point of intersection is  $(Z_L)_N = 1+j2.0 \Omega$ .

### **To find the VSWR of the transmission line:** (assume $Z_0=50 \Omega$ , $Z_L=100-j50 \Omega$ )

1. Plot  $(Z_L)_N$ . Draw VSWR circle, with center at point (1,0), through the point  $(Z_L)_N$ . Read point of intersection of the circle with the horizontal diameter ( $\theta=0$  axis) on the right of the Chart center. This gives the VSWR as 2.6

### **To find the admittance ( $Y_L$ ) of the load:** (assume $Z_0=50 \Omega$ , $Z_L=150-j75 \Omega$ )

1. Plot  $(Z_L)_N$ . Draw the VSWR circle. From point  $(Z_L)_N$ , draw a diameter through the center of the chart to intersect with the circle again.
2. Point of intersection is  $(Y_L)_N = 0.27+j0.14 \Omega = 1/(Z_L)_N$ . Now  $Y_L = (Y_L)_N / Z_0$

**To find the load Reflection coefficient ( $\Gamma_L$ ):** (assume  $Z_0=50 \Omega$ ,  $Z_L=100+j75 \Omega$ )

1. Plot  $(Z_L)_N$ . Draw the VSWR circle. Also draw a radial line through  $(Z_L)_N$ .
2. Use the scale below the smith chart (for Ref. Coeff. E or I) to read the value of the intersection of the circle and central diameter. Thus,  $|\Gamma| = 0.535$
3. The intersection of the radial line & phase angle circle, gives;  $\theta = 30^\circ$

**To find input impedance ( $Z_{IN}$ ), if  $l=0.25\lambda$  of T.L.:** ( $Z_0=50 \Omega$ ,  $Z_L=150-j75 \Omega$ )

1. Plot  $(Z_L)_N$ . Draw VSWR circle. From point  $(Z_L)_N$  move along the VSWR circle by a distance of '0.25', using wavelength circle of 'towards generator'
2. From the arrived point, draw a radial line towards the center. Intersection of this radial line and the VSWR circle gives,  $(Z_{IN})_N = 0.27+j0.14 \Omega$  ?.

**Problem:** A  $600 \Omega$  loss-free transmission line is 105 ft long & used to connect a 200 MHz transmitter, having an output impedance of  $600 \angle 0^\circ \Omega$ , to an antenna with a terminal impedance of  $700 \angle -72^\circ$ . Using smith chart determine;

- (a) the VSWR on the antenna feeder.
- (b) the voltage reflection coefficient at the antenna terminal.
- (c) the impedance presented at the transmitter terminal