

Date: May 29, 2007

Term: 062

Quiz # 8

SR # _____

ID # _____

Name: _____

Sec # 4

For the circuit shown below, **calculate** $i(t)$ & $v_L(t)$ and for V_2 find the **powers** P_{avg} , Q & $|S|$.

