

Date: December 02, 2007

Term: 071

Quiz # 5

SR # \_\_\_\_\_

ID # \_\_\_\_\_

Name: \_\_\_\_\_

Sec # 1

Knowing that  $V_c(t) = 24 \sin(2t)$  [V] in the circuit below, find the energy stored in the 4F capacitor.

