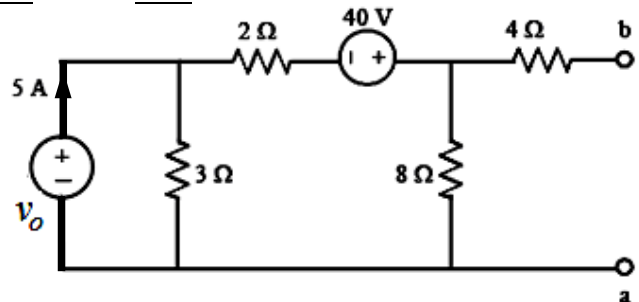


Question # 1

- If a **1.5** battery uses **15 J** to move a charge Q in **5 S**, find **Q in coulombs** & the used **power**.
- How long** must a **1200-W** toaster work to use **6 kWh** of energy?
- A current source of **6A** supplies power to an element for **20 min** at a constant voltage V . If **0.1 kWh** is delivered, **find V**.
- If a device operates at **6 V** & absorbs **12 μ W**, **how many electrons** will pass through the device in **one hour**?
- Find the **power** of a **10- Ω** resistor that carries a **2A** current. What would be its **power** if the current were **doubled**?
- If your room **AC** operates at **220 rms** volts & uses **15 A**, what will be its **annual cost**? (Assuming it works for 24 hours a day & the rate is 5 Halalas)


Question # 2

For the circuit shown below, find the **power** of the **two sources**.




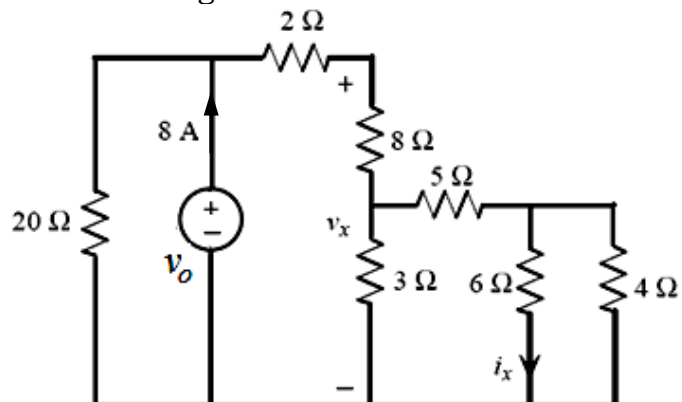
Question # 3

Find the **voltage** v_x and the **current** i_x for the following circuit.



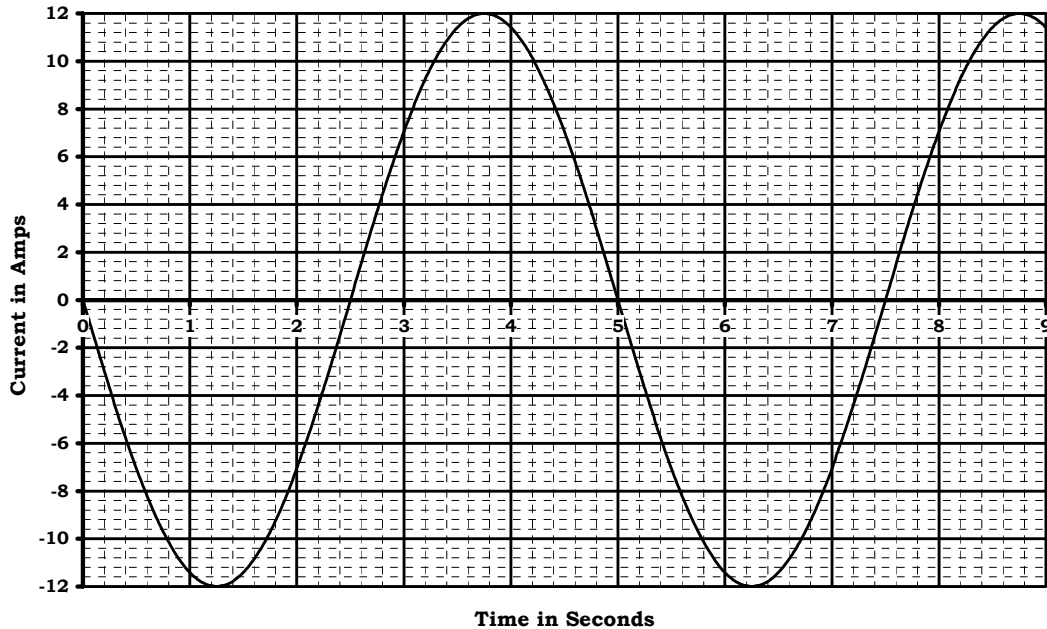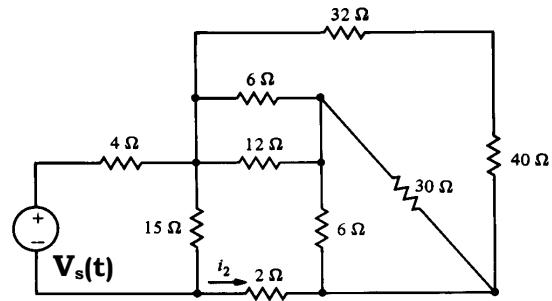Question # 4

If the figure given below represents the **current** $i_2(t)$ of the circuit, **complete** the **table** given below.



1. Frequency of the current $i_2(t)$ =	
2. Instantaneous value of the current $i_2(4.4)$ =	
3. Half cycle average value of the current $i_2(t)$ =	
4. Period of the current $i_2(t)$ =	
5. RMS value of the current $i_2(t)$ =	
6. Phase shift of the current $i_2(t)$ =	
7. RMS value of the voltage $V_s(t)$ =	
8. Peak to peak value of the voltage $V_s(t)$ =	
9. Frequency of the voltage $V_s(t)$ =	