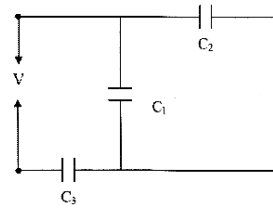


PHYS102.10
Quiz # 9-Chapter 25

Name: Key Id#: _____

In the figure, find the total energy stored by the three capacitors if the potential difference V is 10 V. Assume $C_1 = 10 \mu\text{F}$, $C_2 = 5 \mu\text{F}$ and $C_3 = 4 \mu\text{F}$.



C_1 and C_2 are parallel

$$C_{12} = C_1 + C_2 = 15 \mu\text{F}$$

C_{12} and C_3 are in series

$$C_{123} = \frac{C_{12} C_3}{C_{12} + C_3} = 3.15 \mu\text{F}$$

$$U = \frac{1}{2} C_{123} V^2 = \frac{1}{2} 3.15 \times 10^{-6} \times (10)^2$$
$$= \boxed{1.58 \times 10^{-4} \text{ J}}$$

PHYS102.11
Quiz # 9 - Chapter 25

Name:

Key

Id#:

An air filled parallel plate capacitor has a capacitance of 2.5 nF. The plate area is doubled and paper is inserted between the plates. The new capacitance is 15 nF. Find the dielectric constant of the paper.

$$C_0 = \epsilon_0 \frac{A}{d} = 2.5 \text{ nF}$$

double the area \Rightarrow $C_1 = \frac{6.2 \epsilon_0 A}{d} = 2 \times 2.5 \text{ nF} = 5 \text{ nF}$

$$C_2 = \kappa C_1$$

$$15 \text{ nF} = \kappa 5 \text{ nF}$$

$$\kappa = \frac{15 \text{ nF}}{5 \text{ nF}} = \underline{\underline{3}}$$

PHYS102.12
Quiz # 9 - Chapter 25

Name: Key Id#: _____

(a) If the potential difference between points a and b is 100 V. Find the charge stored in the equivalent capacitor.

$$q_{eq} = C_{eq} V$$

$$= 1 \mu F \times 100 V$$

$$q_{eq} = 100 \mu C$$

