

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS  
 PHYSICS DEPARTMENT  
 QUIZ #9- CHAPTER 27

NAME: Key ID# \_\_\_\_\_ SECTION# \_\_\_\_\_


Consider a series RC circuit as shown in the figure, where  $R = 1.0 \text{ M}\Omega$ ,  $C = 5.0 \text{ }\mu\text{F}$  and  $\mathcal{E} = 30 \text{ V}$ . If the switch is closed at  $t = 0$ ,

- (a) What is the current in resistance  $R$  at time  $10 \text{ s}$  after the switch is closed? What is its direction in the figure?

$$i = \frac{dq}{dt} = \frac{\mathcal{E}}{R} e^{-t/RC} = \frac{30}{1 \times 10^6} e^{-\frac{10}{5 \times 10^{-6} \times 1 \times 10^6}}$$

$$i = 30 \times 10^{-6} e^{-2} =$$
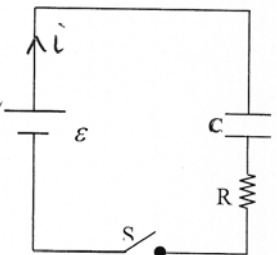
$$\boxed{i = 4.1 \times 10^{-6} \text{ A}}$$



- (b) What is the charge on the capacitor plates at  $t = 10 \text{ s}$ ?

$$q = C\mathcal{E}(1 - e^{-t/RC}) = 5 \times 10^{-6} \times 30 (1 - e^{-2})$$

$$\boxed{q = 1.3 \times 10^{-4} \text{ C}}$$


- (c) What is the potential difference across the capacitor at  $t = 10 \text{ s}$ ?

$$V_c = \frac{q}{C} = \frac{1.3 \times 10^{-4} \text{ C}}{5 \times 10^{-6} \text{ F}} = \boxed{25.9 \text{ V}}$$


KING FAHD UNIVERSITY OF PETROLEUM & MINERALS  
 PHYSICS DEPARTMENT  
 QUIZ #9- CHAPTER 27

NAME: Key ID# \_\_\_\_\_ SECTION# \_\_\_\_\_

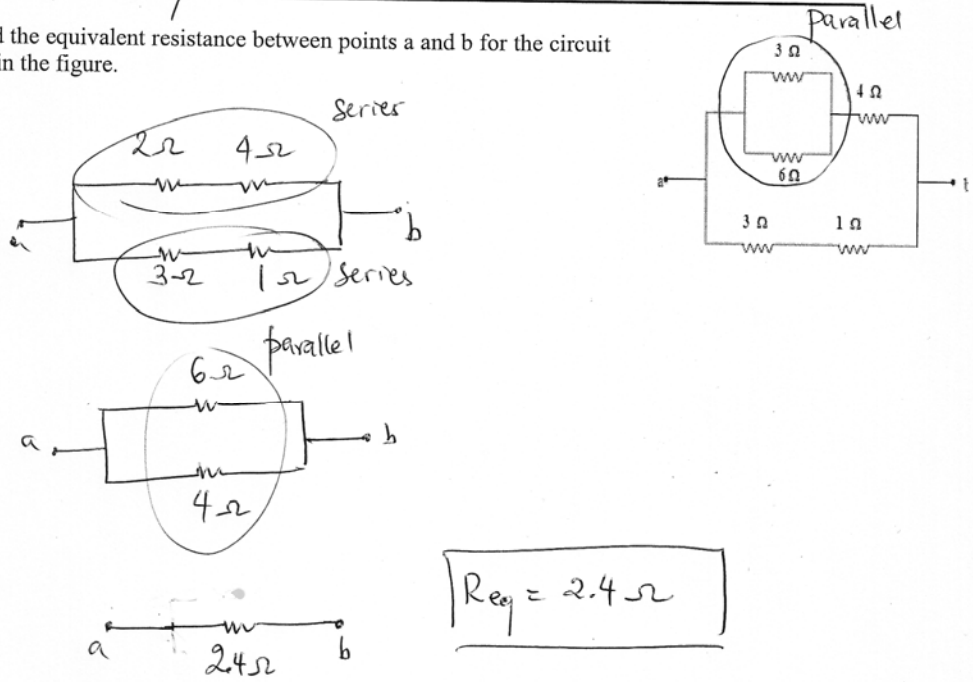(a) Find the equivalent resistance between points a and b for the circuit shown in the figure.



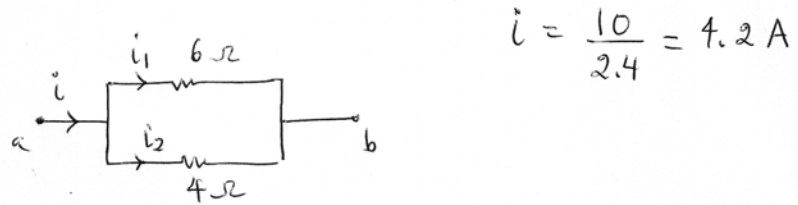(b) If the potential difference  $V_a - V_b = 10$  V, what is the current in the  $1 \Omega$  resistor?






$$V_a - V_b = i_2 \times 4 = i_1 \times 6$$

$$\left. \begin{aligned} i_2 &= \frac{10}{4} = 2.5 \text{ A} \\ i_1 &= \frac{10}{6} = 1.7 \text{ A} \end{aligned} \right\} \text{Sum} = 4.2 \text{ A}$$


KING FAHD UNIVERSITY OF PETROLEUM & MINERALS  
PHYSICS DEPARTMENT  
QUIZ #9- CHAPTER 27

NAME: Key ID# \_\_\_\_\_ SECTION# \_\_\_\_\_

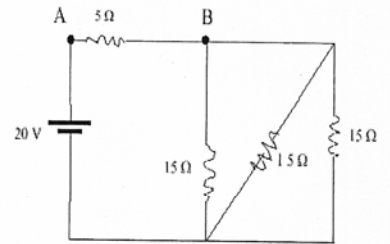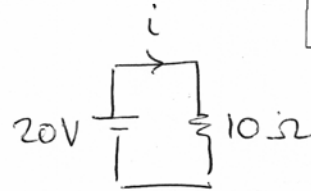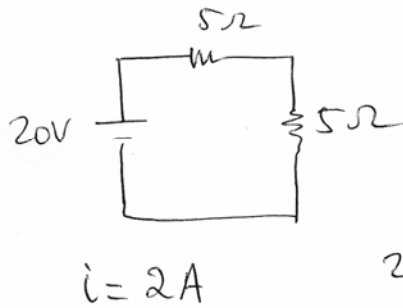(a) Find the equivalent resistor of the circuit shown in the figure.



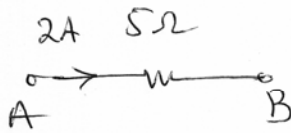(b) Find the potential difference ( $V_B - V_A$ ) between points B and A.



$$V_B - V_A = - 2 \times 5 = -10V$$

(c) What is the current in the  $15\ \Omega$  resistors on the right?

$$i = \frac{2}{3} A$$

