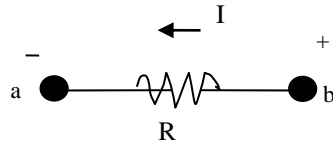


Kirchhoff's Laws


Junction rule: "The sum of the currents entering any junction must be equal to the sum of the current leaving that junction." In symbols $\sum I_{in} = \sum I_{out}$. It is a statement of conservation of charge.

Loop rule: "The algebraic sum of the changes in potential encountered in a complete traversal of any loop of a circuit must be zero." In symbols $\sum V_i = 0$. It is a statement of conservation of energy.




$$\Delta V = V_b - V_a = +iR$$

$$\Rightarrow V_b - iR = V_a$$

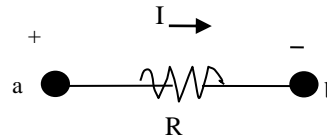


$$\Delta V = V_b - V_a = -iR$$

$$\Rightarrow V_b + iR = V_a$$

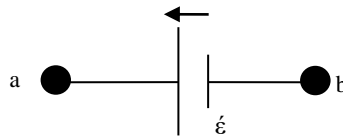

$$\Delta V = V_b - V_a = -\varepsilon$$


$$\Rightarrow V_b + \varepsilon = V_a$$

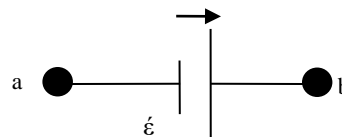

$$\Delta V = V_b - V_a = +\varepsilon$$

$$\Rightarrow V_b - \varepsilon = V_a$$

1- Find $V_a - V_b$.

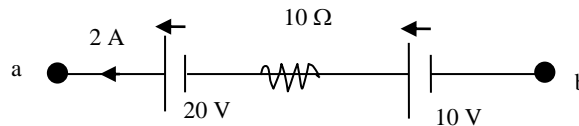

Start with point a and move to the right, one can have

$$V_a - 20 + 2 \times 10 - 10 = V_b \Rightarrow V_a - V_b = 10 \text{ volts}$$

2- A- Find the values of the currents in figure (3).

Ans: At the junction b

$$I_1 + I_2 + I_3 = 0$$

Loop I implies

$$+7I_1 - 10 - 4 = 0 \Rightarrow I_1 = 2A$$


Loop II implies

$$4 + 6 - 5I_2 = 0 \Rightarrow I_2 = 2A$$

from (2) and (3) in (1), one can find

$$I_3 = -I_1 - I_2 = -4A$$

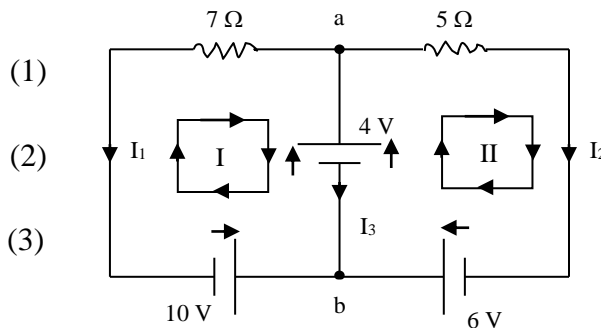So, the current I_3 will be in the opposite direction.



B- With three different methods, prove that $V_a - V_b = +4V$.

Through loop I, one finds $V_a - I_1(7) + 10 = V_b \Rightarrow V_a - V_b = 14 - 10 = 4$ Volts

Through loop II, one finds $V_a - I_2(5) + 6 = V_b \Rightarrow V_a - V_b = 10 - 6 = 4$ Volts

Through the middle connection, one finds $V_a - 4 = V_b \Rightarrow V_a - V_b = 4$ Volts

3- The two branch currents in the circuit shown in figure are $I_1 = \frac{1}{3}A$ and $I_2 = \frac{1}{2}A$.

A- Determine the emfs, E_1 and E_2 .

B- With three different methods, prove that

$$V_a - V_b = 3 \text{ volts.}$$

Ans: At the junction c


$$I_1 + I_2 = I_3 \Rightarrow I_3 = \frac{5}{6}A \quad (1)$$

Loop I implies

$$E_1 - I_1(1+2) - 6I_3 = 0 \Rightarrow E_1 = 6 \text{ volts} \quad (2)$$

Loop II implies
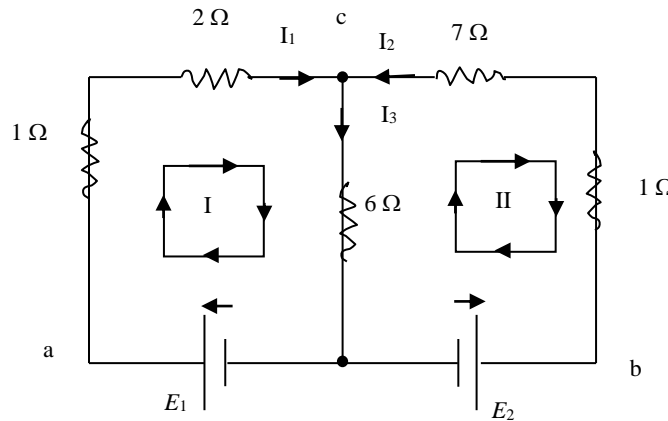
$$-E_2 + I_2(1+7) + 6I_3 = 0 \Rightarrow E_2 = 9 \text{ volts} \quad (3)$$



- If the current I in figure (5) is equal to 4.0 A, then the potential difference between point 1 and 2, i.e. ($V_2 - V_1$), is:

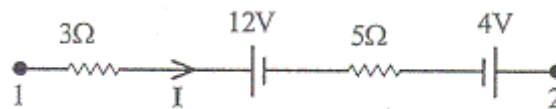


Figure (5)

$$V_1 - 3I - 12 - 5I + 4 = V_2$$

$$\Rightarrow V_2 - V_1 = -40 \text{ Volts}$$

- How long will it take a charged capacitor of 50.0×10^{-6} F to loss 30% of its initial energy if allowed to discharge through a 40 Ohm resistor?

$$\begin{aligned} \because U_i &= \frac{1}{2} \frac{q_i^2}{C}, \quad \therefore U_f = \frac{1}{2} \frac{q_f^2}{C} = 0.7U_i = 0.7 \frac{1}{2} \frac{q_i^2}{C} \\ \Rightarrow Q_f &= \sqrt{0.7}Q_i \\ \therefore Q_f &= Q_i e^{-t/RC} \Rightarrow \sqrt{0.7}Q_i = Q_i e^{-t/RC} \\ \Rightarrow t &= -RC \ln \sqrt{0.7} = \underline{0.36 \times 10^{-3} \text{ s}} \end{aligned}$$

- The capacitor in figure (1) is initially charged to 50 V and then the switch is closed. What charge flows out of the capacitor during the first minute after the switch was closed?

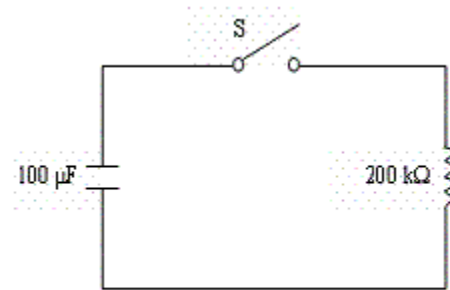



Figure 1

$$\begin{aligned} \because Q &= Q_o(1 - e^{-t/RC}), \\ Q_o &= \varepsilon C = 50 \times 1.0 \times 10^{-4} = 5.0 \text{ mC}, \\ \tau &= RC = 2.0 \times 10^5 \times 1.0 \times 10^{-4} = 20.0 \text{ s} \\ \therefore Q &= 5 \text{ mC}(1 - e^{-60/20}) = \underline{4.75 \text{ mC}} \end{aligned}$$

- At $t=0$, a 2.0×10^{-6} Farad capacitor is connected in series to a 20-V battery and a 2.0×10^6 Ohm resistor. How long does it take for the potential difference across the capacitor to be 12 V?

$$\begin{aligned} \because V &= V_{\max}(1 - e^{-t/RC}) \\ \therefore 12 &= 20(1 - e^{-t/4}) \\ \Rightarrow t &= RC = 2.0 \times 10^5 \times 1.0 \times 10^{-4} = \underline{3.66 \text{ s}} \end{aligned}$$

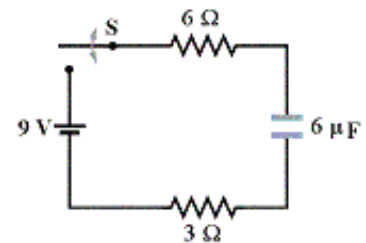- In the circuit shown in the following figure, the capacitor was initially uncharged. At time $t = 0$, switch S is closed. If τ denotes the time constant, the current through the 3-ohm resistor at $t = \tau/10$ is



$$I = \frac{\varepsilon}{R} e^{-t/\tau} = \frac{9}{9} e^{-1/10} = 0.90 \text{ A}$$

- A capacitor, initially uncharged in a single-loop RC circuit, is charged to 85% of its final potential difference in 2.4 s. What is its time constant in seconds?

$$\begin{aligned} \therefore V &= V_{\max}(1 - e^{-t/RC}) \\ \therefore 0.85 &= (1 - e^{-t/\tau}) \Rightarrow 0.85 = (1 - e^{-t/\tau}) \\ \therefore \ln 0.15 &= -\frac{t}{\tau} \Rightarrow \tau = -\frac{2.4}{\ln 0.15} = 1.27 = \underline{1.3 \text{ s}} \end{aligned}$$


- A 1.0 μF uncharged capacitor and a 3.0 $\text{k}\Omega$ resistor are connected in series, and then (at time $t = 0$) a 6-V potential difference is applied across them. Find the time at which the voltage on the capacitor is 3.8 V.

$$\begin{aligned} C &= 1.0 \mu\text{F}, R = 3.0 \text{ k}\Omega \Rightarrow \tau = 3.0 \text{ ms} \\ \therefore V &= \varepsilon(1 - e^{-t/\tau}) \Rightarrow e^{-t/\tau} = 1 - \frac{V}{\varepsilon} = 0.367 \\ \therefore t &= -\tau \ln(0.367) = \underline{3.0 \text{ ms}}. \end{aligned}$$

- Q16. A capacitor of capacitance C takes 2 s to reach 63 % of its maximum charge when connected in series to a resistance R and a battery of emf ε . How long does it take for this capacitor to reach 95 % of its maximum charge (from zero initial charge)? (Ans: 6s)

$$\begin{aligned} 1 - q(t) &= q_0(1 - e^{-t/\tau}) \Rightarrow e^{-t/\tau} = 1 - 0.63 = 0.37 \\ \Rightarrow \tau &= -t / \ln(0.37) \approx 2 \text{ s} \\ 0.95q_0 &= q_0(1 - e^{-t/2}) \Rightarrow e^{-t/2} = 1 - 0.95 = 0.05 \\ \Rightarrow t &= -2 \ln(0.05) \approx \underline{6 \text{ s}} \end{aligned}$$

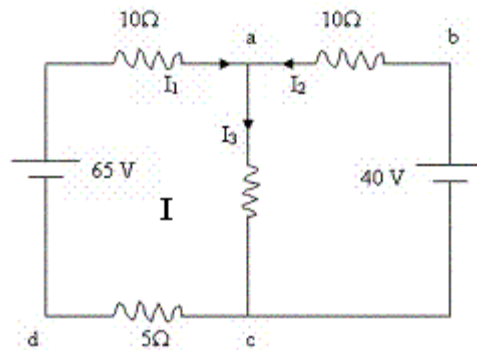Example: For the circuit shown in figure (4), if $V_a - V_c = 20$ Volts , what is the potential difference $V_b - V_d$?



- (a) -55 Volts.
- (b) 25 Volts.
- (c) -25 Volts.

$$\begin{aligned} \text{In Loop I, } 65 - 15I_1 - 20 &= 0 \Rightarrow I_1 = 3\text{A} \\ \therefore V_b - V_d &= V_b - V_c + V_c - V_d = 40 + 3 \times 5 = \underline{55 \text{ V}} \end{aligned}$$

- (d) 35 Volts.
 (e) 55 Volts.


Example: A capacitor of capacitance C is discharging through a resistor of resistance R . In terms of RC , when will the energy stored in the capacitor reduces to one fifth of its initial value?

$$\therefore U = U_0 e^{-2t/\tau}$$

$$\therefore \frac{1}{5} U_0 = U_0 e^{-2t/\tau} \Rightarrow t = \left(\frac{\ln 5}{2}\right) \tau = 0.80 RC$$

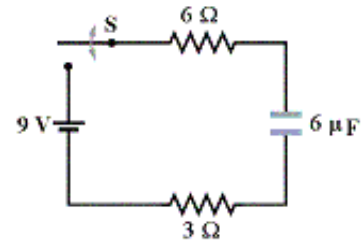Example: In the circuit shown in the following figure, the capacitor was initially uncharged. At time $t = 0$, switch S is closed. If τ denotes the time constant, the current through the 3-ohm resistor at $t = \tau/10$ is

$$I = \frac{\mathcal{E}}{R} e^{-t/\tau} = \frac{9}{9} e^{-1/10} = 0.90 \text{ A}$$



- A fully charged $6.0 \mu\text{F}$ capacitor is connected in series with a $1.5 \times 10^5 \Omega$ resistor. What percentage of the original charge is left on the capacitor after 1.8 s of discharging?

Solve: The time constant for this circuit is $\tau = RC = (1.5 \times 10^5 \Omega)(6.0 \times 10^{-6} \text{ F}) = 0.90 \text{ s}$. At $t = 1.8 \text{ s}$, which is 2τ , the fractional charge remaining is $\frac{q}{Q_0} = e^{-t/\tau} = e^{-(1.8 \text{ s})/(0.90 \text{ s})} = e^{-2} = 0.14$ or 14%.

- When a capacitor is being charged up, (a) how many time constants are required for it to receive 95% of its maximum charge, and (b) what is the current in the circuit at that time?


19.68. Set Up: The time constant is $\tau = RC$, so $q = Q_{\text{final}}(1 - e^{-t/RC})$ and $i = I_0 e^{-t/RC}$.

Solve: (a) $q = 0.95 Q_{\text{final}}$ gives $0.95 = 1 - e^{-t/RC}$. $e^{-t/\tau} = 0.05$. $-\frac{t}{\tau} = \ln(0.05)$. $\frac{t}{\tau} = 3.0$. Three time constants are required.

(b) $e^{-t/\tau} = 0.05$ so $i = 0.05 I_0$.

In **Figure 6**, $R_1 = 100 \Omega$, $R_2 = R_3 = R_4 = 75 \Omega$, and the ideal battery has emf $\mathcal{E} = 6.0 \text{ V}$. What is the current in R_1 ?

Figure 6

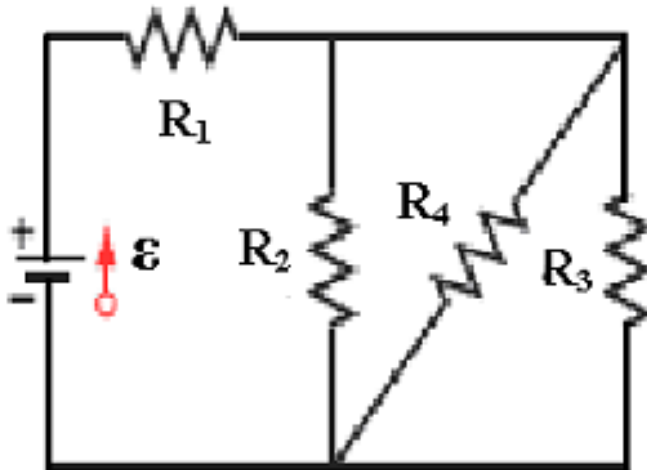

R_2, R_3 and R_4 are in parallel


$$\therefore R_{\text{eq}} = \frac{75}{3} = 25 \Omega$$

R_1 is in series with R_{eq}

$$\therefore R'_{\text{eq}} = R_{\text{eq}} + R_1 = 125 \Omega$$

$$\therefore i = \frac{\mathcal{E}}{R'_{\text{eq}}} = 48 \text{ mA}$$

In the circuit shown in **Figure 7**, the 33Ω resistor dissipates 0.50 W . What is the emf of the ideal battery?

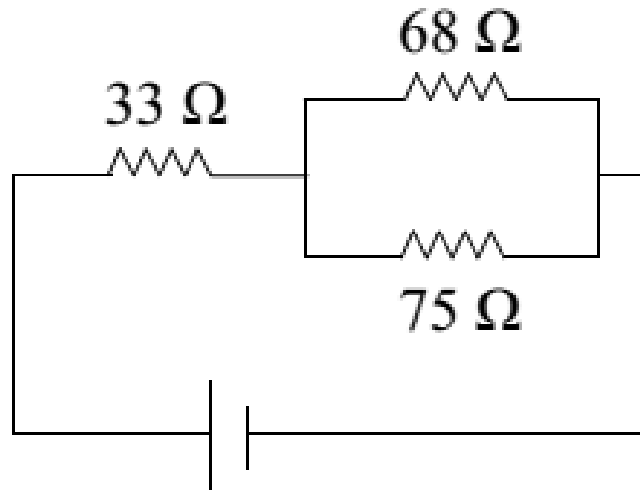Figure 7

$$P = I^2 R \rightarrow I = \sqrt{\frac{P_{33}}{R_{33}}} = 0.123 A, R_{eq} = 33 + \left(\frac{1}{68} + \frac{1}{75}\right)^{-1} = 68.88 \Omega,$$
$$V = IR_{eq} = 8.5 V$$