

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
ELECTRICAL ENGINEERING DEPARTMENT

Dr. Ibrahim O. Habiballah


EE-306

Key Solution

Quiz # 4 Sec.: 4 I.D.# Name:

Circle the correct answer.

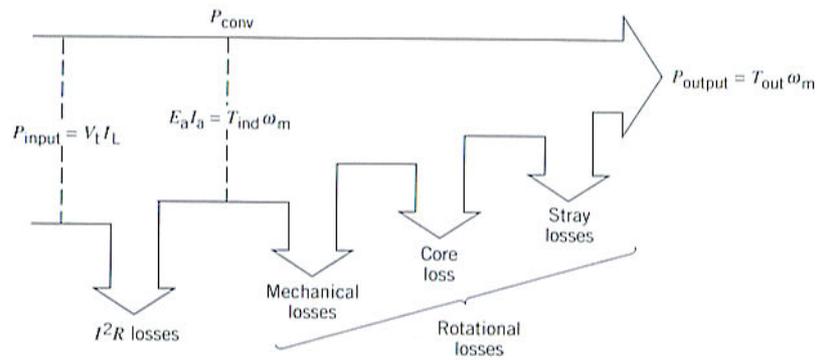The power flow daigram shown below is for a



- a- long-shunt compound DC generator.
- b- short-shunt compound DC motor.**
- c- shun DC gearator.
- d- none of the above.