KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

ELECTRICAL ENGINEERING DEPARTMENT


Dr. Ibrahim O. Habiballah

EE-306

Key Solution

Quiz 6	Sec.: 5	I.D.:	Ser#:	Name:	
Q.1 A 50	O-Hz polyphase indu	ction motor wi	th a full-load spee	d of 1450 rpm has 4- ₁	poles.
				□ True	e □ False
Q.2 The	pushover torque in t	hree-phase ind	uction machines o	occurs when the slip is	s positive.
_	-pole, 60-Hz, 3-phas synchronous speed is		notor has a full-lo	and speed of 3555 rpi	n. At half-
				□ True	e □ False
_	wn torque, its speed v rpm rpm		motor has a ful	ll-load speed of 174	0 rpm. At

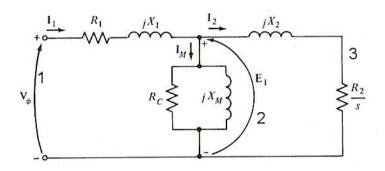Q.5 In the per-phase equivalent circuit of a polyphase induction motor shown below, number "1" is the (....) power, number "2" is the (.....) power, and number "3" is the (.....) power.



- a. electrical input; converted; mechanical output
- b. electrical input; air-gap; air-gap
- c. electrical input; air-gap; converted
- d. mechanical input; converted; electrical output.